


Microwave Filter Design

Chp4. Transmission Lines and Components

Prof. Tzong-Lin Wu



Department of Electrical Engineering
National Taiwan University

Prof. T. L. Wu

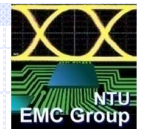

Microstrip Lines

Microstrip Structure

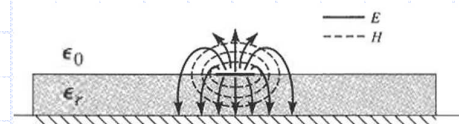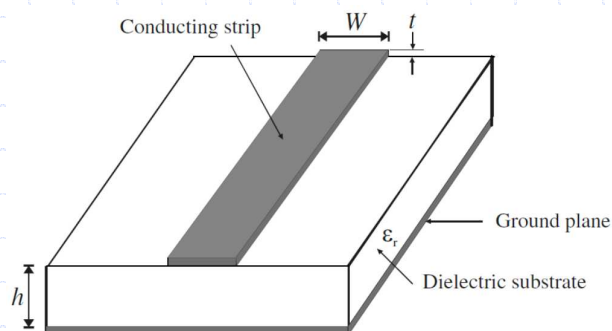


- Inhomogeneous structure:
Due to the fields within two guided-wave media, the microstrip does not support a pure TEM wave.
- When the longitudinal components of the fields for the dominant mode of a microstrip line is much smaller than the transverse components, the **quasi-TEM approximation** is applicable to facilitate design.

Prof. T. L. Wu

Microstrip Lines

- Transmission Line Parameters

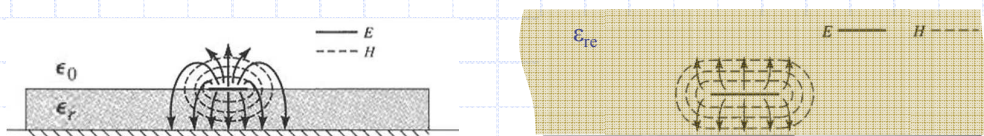Effective Dielectric Constant (ϵ_{re}) and Characteristic Impedance (Z_C)



➤ For thin conductors (i.e., $t \rightarrow 0$), closed-form expression (error $\leq 1\%$):

◆ $W/h \leq 1$:

$$\epsilon_{re} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left\{ \left(1 + 12 \frac{h}{W} \right)^{-0.5} + 0.04 \left(1 - \frac{W}{h} \right)^2 \right\}$$

$$Z_c = \frac{\eta}{2\pi\sqrt{\epsilon_{re}}} \ln \left(\frac{8h}{W} + 0.25 \frac{W}{h} \right)$$

◆ $W/h \geq 1$:

$$\epsilon_{re} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(1 + 12 \frac{h}{W} \right)^{-0.5}$$

$$Z_c = \frac{\eta}{\sqrt{\epsilon_{re}}} \left\{ \frac{W}{h} + 1.393 + 0.677 \ln \left(\frac{W}{h} + 1.444 \right) \right\}^{-1}$$

➤ For thin conductors (i.e., $t \rightarrow 0$), more accurate expressions:

◆ Effective dielectric constant (error $\leq 0.2\%$):

$$\epsilon_{re} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(1 + \frac{10}{u} \right)^{-ab}$$

$$a = 1 + \frac{1}{49} \ln \left(\frac{u^4 + \left(\frac{u}{52} \right)^2}{u^4 + 0.432} \right) + \frac{1}{18.7} \ln \left[1 + \left(\frac{u}{18.1} \right)^3 \right]$$

$$b = 0.564 \left(\frac{\epsilon_r - 0.9}{\epsilon_r + 3} \right)^{0.053}$$

◆ Characteristic impedance (error $\leq 0.03\%$):

$$Z_c = \frac{\eta}{2\pi\sqrt{\epsilon_{re}}} \ln \left[\frac{F}{u} + \sqrt{1 + \left(\frac{2}{u} \right)^2} \right]$$

$$F = 6 + (2\pi - 6) \exp \left[- \left(\frac{30.666}{u} \right)^{0.7528} \right]$$

Prof. T. L. Wu

Microstrip Lines

- Transmission Line Parameters

➤ Guided wavelength

$$\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_{re}}} \quad \text{or} \quad \lambda_g = \frac{300}{f(\text{GHz})\sqrt{\epsilon_{re}}} \text{ mm}$$

➤ Propagation constant


$$\beta = \frac{2\pi}{\lambda_g}$$

➤ Phase velocity

$$v_p = \frac{\omega}{\beta} = \frac{c}{\sqrt{\epsilon_{re}}}$$

➤ Electrical length

$$\theta = \beta \ell$$

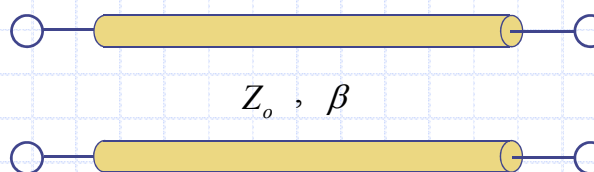

Prof. T. L. Wu

Microstrip Lines


- Transmission Line Parameters

➤ Losses

- ◆ Conductor loss
- ◆ Dielectric loss
- ◆ Radiation loss

➤ Dispersion

- ◆ $\epsilon_{re}(f)$
- ◆ $Z_o(f)$

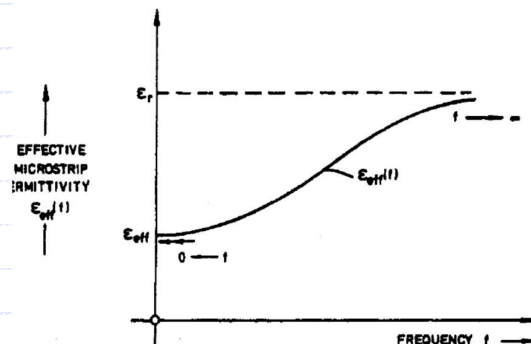

➤ Surface Waves and higher-order modes

- ◆ Coupling between the quasi-TEM mode and surface wave mode become significant when the frequency is above f_s

$$f_s = \frac{c \tan^{-1} \epsilon_r}{\sqrt{2\pi h} \sqrt{\epsilon_r - 1}}$$

- ◆ Cutoff frequency f_c of first higher-order modes in a microstrip

$$f_c = \frac{c}{\sqrt{\epsilon_r} (2W + 0.8h)}$$


- ◆ The operating frequency of a microstrip line $< \text{Min}(f_s, f_c)$

Prof. T. L. Wu

Microstrip Lines

- Tx-Line

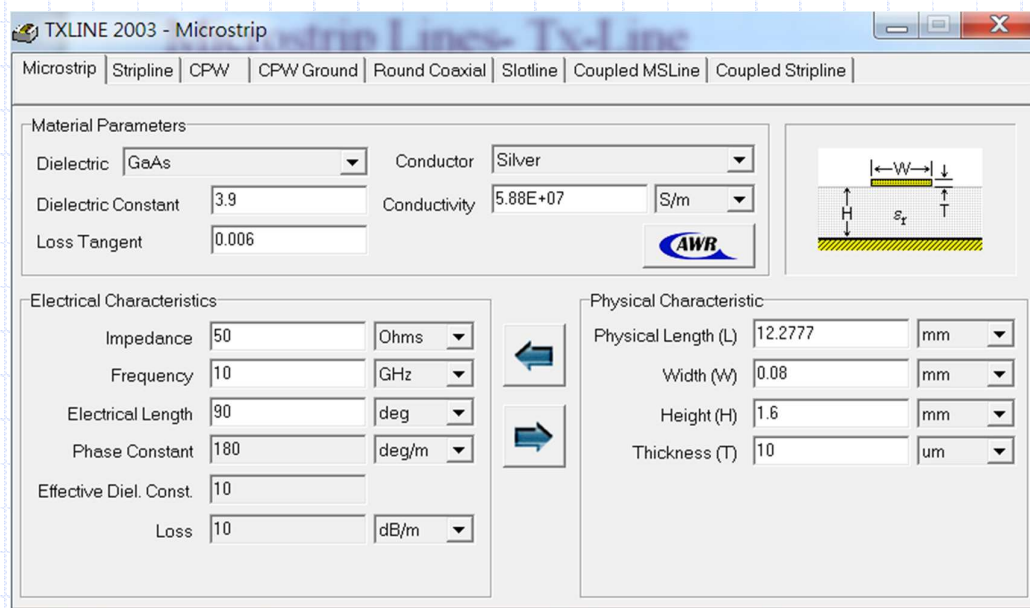➤ Synthesis of transmission line – electrical or physical parameters




Prof. T. L. Wu

Coupled Lines

Coupled line Structure

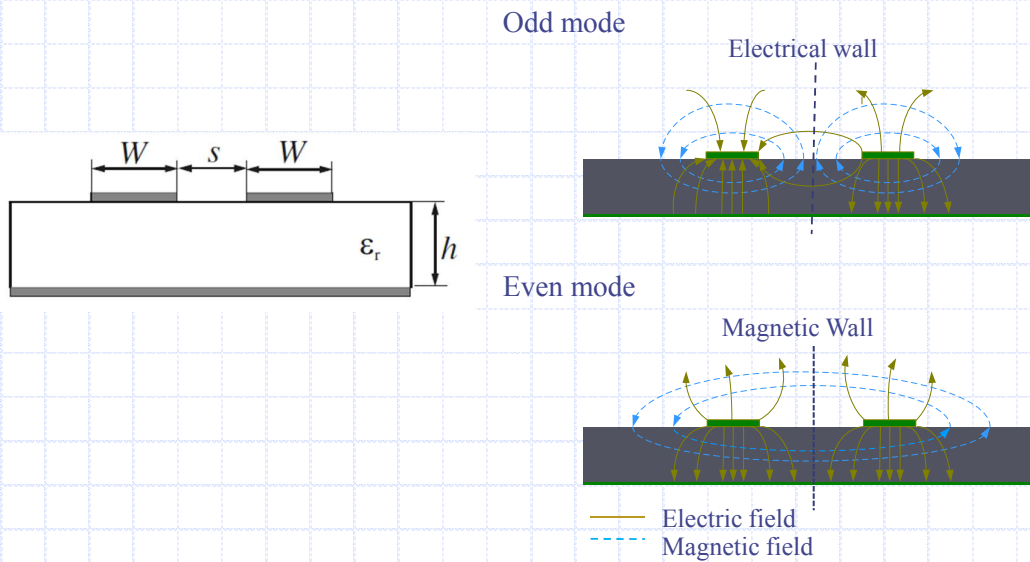- The coupled line structure supports two quasi-TEM modes: odd mode and even mode.




Prof. T. L. Wu


Coupled Lines – Odd- and Even- Mode

Effective Dielectric Constant (ϵ_{re}) and Characteristic Impedance (Z_C)

Odd mode

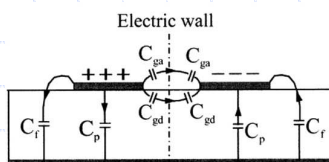

Even mode

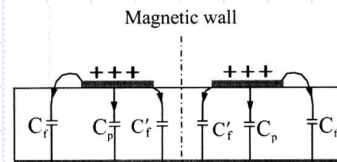

- Odd- and Even- Mode:

The characteristic impedances (Z_{co} and Z_{ce}) and effective dielectric constants (ϵ_{re}^o and ϵ_{re}^e) are obtained from the capacitances (C_o and C_e):

- ◆ Odd-Mode:

$$Z_{co} = (c\sqrt{C_o^a C_o})^{-1}$$

$$\epsilon_{re}^o = C_o / C_o^a$$

- ◆ Even-Mode:

$$Z_{ce} = (c\sqrt{C_e^a C_e})^{-1}$$

$$\epsilon_{re}^e = C_e / C_e^a$$

- C_o^a and C_e^a are even- and odd-mode capacitances for the coupled microstrip line configuration with air as dielectric.

Prof. T. L. Wu

Coupled Lines

– Odd- and Even- Mode

Effective Dielectric Constant (ϵ_{re}) and Characteristic Impedance (Z_c)

➤ Odd- and Even- Mode Capacitances:

◆ Odd-Mode:

$$C_o = C_p + C_f + C_{gd} + C_{ga}$$

◆ Even-Mode:

$$C_e = C_p + C_f + C_f'$$

□ C_p denotes the parallel plate capacitance between the strip and the ground plane:

$$C_p = \epsilon_o \epsilon_r W/h$$

□ C_f is the fringe capacitance as if for an uncoupled single microstrip line:

$$2C_f = \sqrt{\epsilon_{re}}/(cZ_c) - C_p$$

□ C_f' accounts for the modification of fringe capacitance C_f :

$$C_f' = \frac{C_f}{1 + A(h/s)\tanh(8s/h)}, \quad A = \exp[-0.1 \exp(2.33 - 2.53W/h)]$$


□ C_{gd} may be found from the corresponding coupled stripline geometry:

$$C_{gd} = \frac{\epsilon_o \epsilon_r}{\pi} \ln \left[\coth \left(\frac{\pi}{4} \frac{s}{h} \right) \right] + 0.65 C_f \left(\frac{0.02 \sqrt{\epsilon_r}}{s/h} + 1 - \frac{1}{\epsilon_r^2} \right)$$


□ C_{ga} can be modified from the capacitance of the corresponding coplanar strips:

$$C_{ga} = \epsilon_o \frac{K(k')}{K(k)}, \quad \frac{K(k')}{K(k)} = \begin{cases} \frac{1}{\pi} \ln \left(2 \frac{1 + \sqrt{k'}}{1 - \sqrt{k'}} \right) & \text{for } 0 \leq k^2 \leq 0.5 \\ \frac{\pi}{\ln \left(2 \frac{1 + \sqrt{k}}{1 - \sqrt{k}} \right)} & \text{for } 0.5 \leq k^2 \leq 1 \end{cases}, \quad k = \frac{s/h}{s/h + 2W/h}, \quad k' = \sqrt{1 - k^2} \quad \text{T. L. Wu}$$

Odd mode

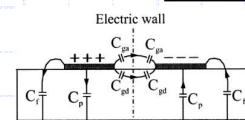

Even mode

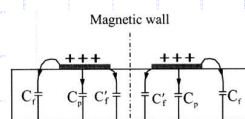


Discontinuities And Components

– Discontinuities

➤ Microstrip discontinuities commonly encountered in the layout of practical filters include steps, open-ends, bends, gaps, and junctions.

➤ The effects of discontinuities can be accurately modeled by full-wave EM simulator or closed-form expressions and taken into account in the filter designs.


◆ Steps in width:

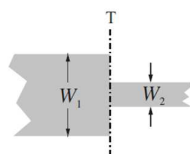


◆ Open ends:




◆ Gaps:

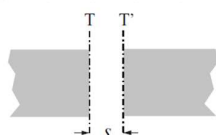

◆ Bends:

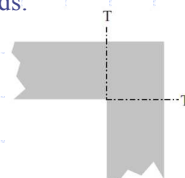

Discontinuities – Steps in width

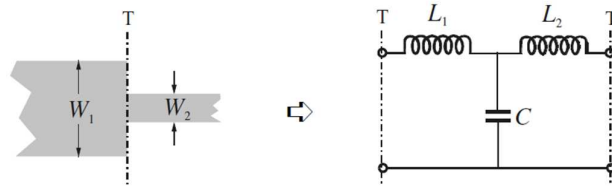

$$C = 0.00137h \frac{\sqrt{\epsilon_{re1}}}{Z_{c1}} \left(1 - \frac{W_2}{W_1}\right) \left(\frac{\epsilon_{re1} + 0.3}{\epsilon_{re1} - 0.258}\right) \left(\frac{W_1/h + 0.264}{W_1/h + 0.8}\right) \text{ (pF)}$$

$$L_1 = \frac{L_{w1}}{L_{w1} + L_{w2}} L$$

$$L_{wi} = Z_{ci} \sqrt{\epsilon_{rei}}/c$$

where

$$L_2 = \frac{L_{w2}}{L_{w1} + L_{w2}} L$$

$$L = 0.000987h \left(1 - \frac{Z_{c1}}{Z_{c2}} \sqrt{\frac{\epsilon_{re1}}{\epsilon_{re2}}}\right)^2$$


Note : L_{wi} for $i = 1, 2$ are the inductances per unit length of the appropriate microstrips, having widths W_1 and W_2 , respectively.

Z_{ci} and ϵ_{rei} denote the characteristic impedance and effective dielectric constant corresponding to width W_i , and h is the substrate thickness in micrometers.

Prof. T. L. Wu

Discontinuities – Open ends

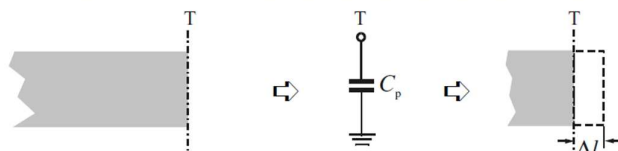- The fields do not stop abruptly but extend slightly further due to the effect of the fringing field.



$$\Delta l = \frac{cZ_c C_p}{\sqrt{\epsilon_{re}}}$$

◆ Closed-form expression:

$$\frac{\Delta l}{h} = \frac{\xi_1 \xi_3 \xi_5}{\xi_4}$$

where

$$\xi_1 = 0.434907 \frac{\epsilon_{re}^{0.81} + 0.26(W/h)^{0.8544} + 0.236}{\epsilon_{re}^{0.81} - 0.189(W/h)^{0.8544} + 0.87}$$

$$\xi_2 = 1 + \frac{(W/h)^{0.371}}{2.35\epsilon_r + 1}$$

$$\xi_3 = 1 + \frac{0.5274 \tan^{-1}[0.084(W/h)^{1.9413/\xi_2}]}{\epsilon_{re}^{0.9236}}$$

$$\xi_4 = 1 + 0.037 \tan^{-1}[0.067(W/h)^{1.456}] \cdot \{6 - 5 \exp[0.036(1 - \epsilon_r)]\}$$



$$\xi_5 = 1 - 0.218 \exp(-7.5W/h)$$

◆ The accuracy is better than 0.2 % for the range of $0.01 \leq W/h \leq 100$ and $\epsilon_r \leq 128$

Prof. T. L. Wu

Discontinuities

– Gaps

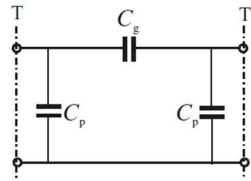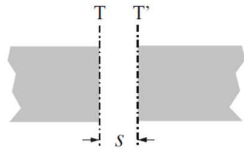

$$C_p = 0.5C_e$$

$$C_g = 0.5C_o - 0.25C_e$$

$$\frac{C_o}{W} (\text{pF/m}) = \left(\frac{\epsilon_r}{9.6} \right)^{0.8} \left(\frac{s}{W} \right)^{m_o} \exp(k_o)$$

$$m_o = \frac{W}{h} [0.619 \log(W/h) - 0.3853]$$

$$\text{for } 0.1 \leq s/W \leq 1.0$$

where

$$k_o = 4.26 - 1.453 \log(W/h)$$

$$m_e = 0.8675$$

$$\text{for } 0.1 \leq s/W \leq 0.3$$

$$k_e = 2.043 \left(\frac{W}{h} \right)^{0.12}$$

$$m_e = \frac{1.565}{(W/h)^{0.16}} - 1$$

$$\text{for } 0.3 \leq s/W \leq 1.0$$



$$k_e = 1.97 - \frac{0.03}{W/h}$$

- ◆ The accuracy is within 7 % for $0.5 \leq W/h \leq 2$ and $2.5 \leq \epsilon_r \leq 15$

Prof. T. L. Wu

Discontinuities

– Bends

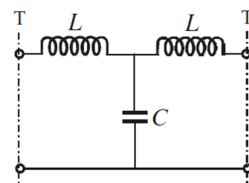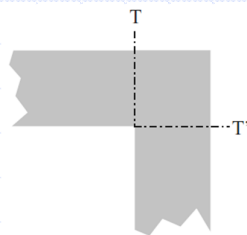

$$\frac{C}{W} (\text{pF/m}) = \begin{cases} \frac{(14\epsilon_r + 12.5)W/h - (1.83\epsilon_r - 2.25)}{\sqrt{W/h}} + \frac{0.02\epsilon_r}{W/h} & \text{for } W/h < 1 \\ (9.5\epsilon_r + 1.25)W/h + 5.2\epsilon_r + 7.0 & \text{for } W/h \geq 1 \end{cases}$$

$$\frac{L}{h} (\text{nH/m}) = 100 \left\{ 4 \sqrt{\frac{w}{h}} - 4.21 \right\}$$

- ◆ The accuracy on the capacitance is quoted as within 5% over the ranges of $2.5 \leq \epsilon_r \leq 15$ and $0.1 \leq W/h \leq 5$.
- ◆ The accuracy on the inductance is about 3 % for $0.5 \leq W/h \leq 2$.

Prof. T. L. Wu

Components


– lumped inductors and capacitors

➤ Lumped inductors and capacitors

The elements whose physical dimensions are much smaller than the free space wavelength λ_0 of the highest operating frequency (smaller than $0.1 \lambda_0$).

➤ Design of inductors


◆ High-impedance line

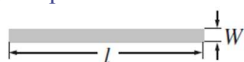

◆ Meander line




◆ Circular spiral

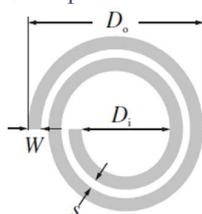

◆ Square spiral



◆ Circuit representation

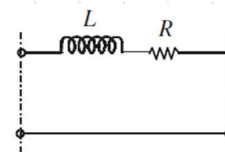

◆ Initial design formula for straight-line inductor

$$L(\text{nH}) = 2 \times 10^{-4} l \left[\ln \left(\frac{l}{W+t} \right) + 1.193 + 0.2235 \frac{W+t}{l} \right] K_g \quad \text{for } l \text{ in } \mu\text{m}$$

$$R = \frac{R_s l}{2(W+t)} \left[1.4 + 0.217 \ln \left(\frac{W}{5t} \right) \right] \quad \text{for } 5 < \frac{W}{t} < 100$$

Prof. T. L. Wu


Components

– lumped inductors and capacitors

➤ Design of capacitors

◆ Interdigital capacitor

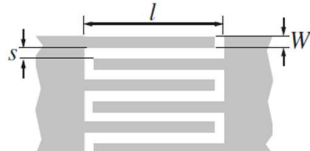Assuming the finger width W equals to the space and empirical formula for capacitance is shown as follow




$$C(\text{pF}) = 3.937 \times 10^{-5} l (\epsilon_r + 1) [0.11(n-3) + 0.252] \quad \text{for } l \text{ in } \mu\text{m}$$

$$R = \frac{4}{3} \frac{R_s l}{W n}$$

◆ Metal-insulator-metal (MIM) capacitor

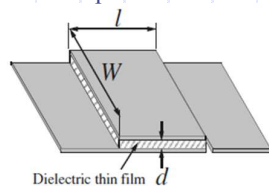
Estimation of capacitance and resistance is approximated by parallel-plate



$$C = \frac{\epsilon(W \times l)}{d}$$

$$R = \frac{R_s l}{W}$$

◆ Circuit representation

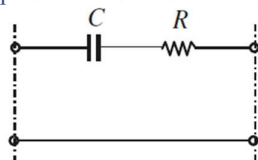

Prof. T. L. Wu



Components

- Quasilumped elements (1)

➤ Quasilumped elements

Physical lengths are smaller than a quarter of guided wavelength λ_g .

◆ High-impedance short line element

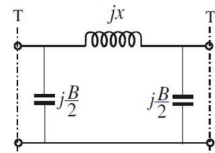
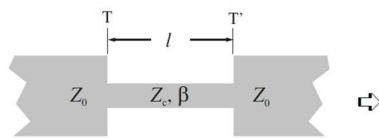


$$l < \frac{\lambda_g}{8}$$

$$x = Z_c \sin\left(\frac{2\pi}{\lambda_g} l\right) \approx Z_c \left(\frac{2\pi}{\lambda_g} l\right)$$

$$\frac{B}{2} = \frac{1}{Z_c} \tan\left(\frac{\pi}{\lambda_g} l\right) \approx \frac{1}{Z_c} \left(\frac{\pi}{\lambda_g} l\right)$$

□ Derivation

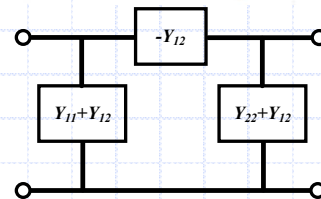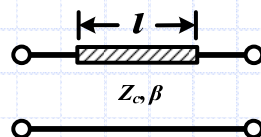

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta l & jZ_c \sin \beta l \\ j\frac{1}{Z_c} \sin \beta l & \cos \beta l \end{bmatrix}$$



$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{D}{B} & -\frac{(AD-BC)}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix} = \begin{bmatrix} \frac{\cos \beta l}{jZ_c \sin \beta l} & \frac{-1}{jZ_c \sin \beta l} \\ -1 & \cos \beta l \end{bmatrix}$$

inductive element: $-Y_{12} = \frac{1}{jZ_c \sin \beta l} = \frac{1}{jx}$



capacitive element: $Y_{11} + Y_{12} = \frac{\cos \beta l - 1}{jZ_c \sin \beta l} = \frac{\cos^2 \frac{\beta l}{2} - \sin^2 \frac{\beta l}{2} - \left(\cos^2 \frac{\beta l}{2} + \sin^2 \frac{\beta l}{2}\right)}{jZ_c 2 \sin \frac{\beta l}{2} \cos \frac{\beta l}{2}} = \frac{-2 \sin^2 \frac{\beta l}{2}}{jZ_c 2 \sin \frac{\beta l}{2} \cos \frac{\beta l}{2}} = j \frac{\tan \frac{\beta l}{2}}{Z_c} = j \frac{B}{2}$

Components

- Quasilumped elements (2)

➤ Quasilumped elements

◆ Low-impedance short line element

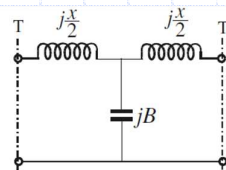
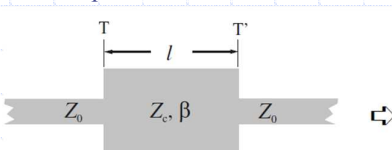


$$l < \frac{\lambda_g}{8}$$

$$B = \frac{1}{Z_c} \sin\left(\frac{2\pi}{\lambda_g} l\right) \approx \frac{1}{Z_c} \left(\frac{2\pi}{\lambda_g} l\right)$$

$$\frac{x}{2} = Z_c \tan\left(\frac{\pi}{\lambda_g} l\right) \approx Z_c \left(\frac{\pi}{\lambda_g} l\right)$$

□ Derivation

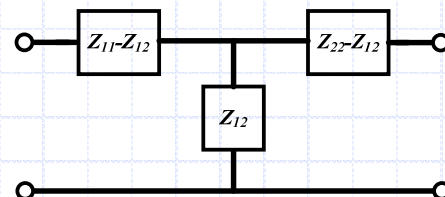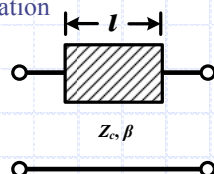

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta l & jZ_c \sin \beta l \\ j\frac{1}{Z_c} \sin \beta l & \cos \beta l \end{bmatrix}$$



$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{A}{C} & \frac{(AD-BC)}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix} = \begin{bmatrix} \frac{Z_c \cos \beta l}{j \sin \beta l} & \frac{Z_c}{j \sin \beta l} \\ \frac{Z_c}{j \sin \beta l} & \frac{Z_c \cos \beta l}{j \sin \beta l} \end{bmatrix}$$

capacitive element: $Z_{12} = \frac{Z_c}{j \sin \beta l} = \frac{1}{jB} \Rightarrow B = \frac{\sin \beta l}{Z_c}$


inductive element: $Z_{11} - Z_{12} = \frac{Z_c \cos \beta l - 1}{j \sin \beta l} = jZ_c \tan \frac{\beta l}{2} = j \frac{x}{2} \Rightarrow \frac{x}{2} = Z_c \tan \frac{\beta l}{2}$

Components

– Quasilumped elements (3)

➤ Quasilumped elements

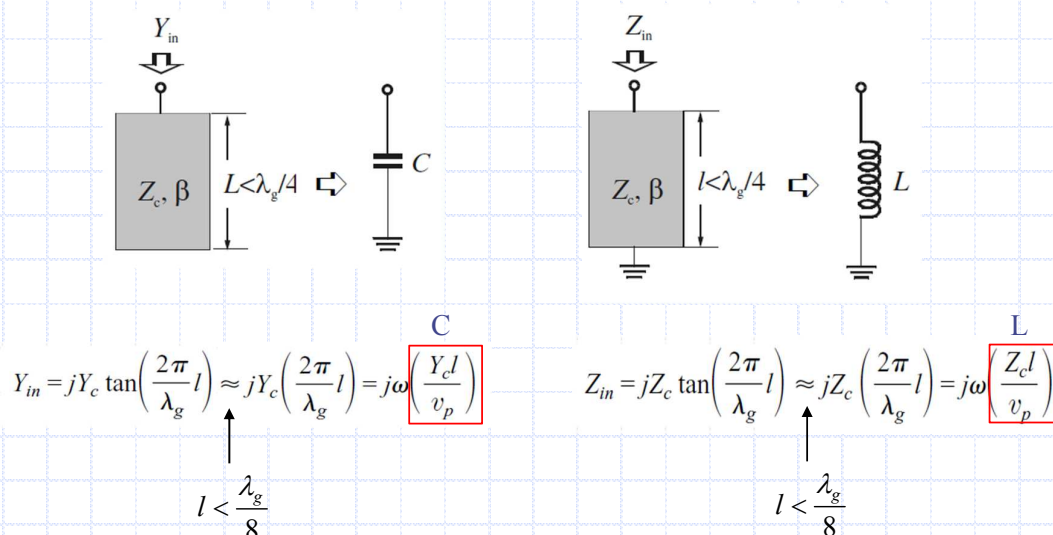- ◆ Open- and short-circuited stubs
(assuming the length L is smaller than a quarter of guided wavelength λ_g)



Prof. T. L. Wu

Components

– Resonators


➤ Lumped-element or quasilumped-element resonators

- ◆ Formed by the lumped or quasilumped inductors and capacitors
- ◆ Resonate at $\omega_0 = \frac{1}{\sqrt{LC}}$



➤ Distributed resonators

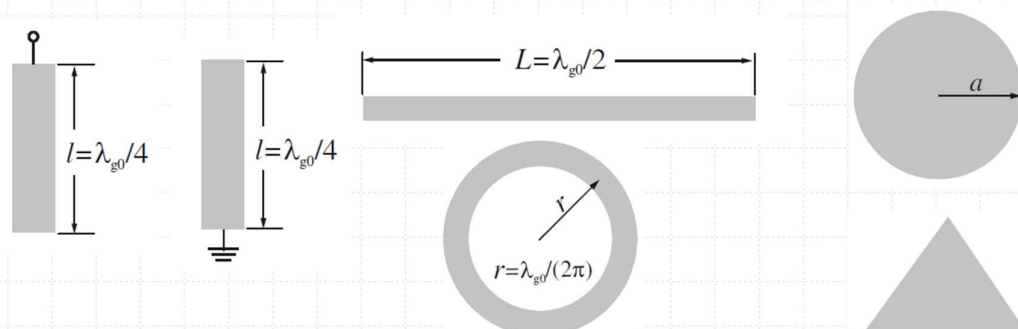- ◆ Quarter-wavelength resonators, half-wavelength resonators, and patch resonators.



L. Wu

Loss Considerations for Microstrip Resonators

- Unloaded quality factor Q_u is served as a justification for whether or not the required insertion loss of a bandpass filter can be met.

$$Q_u = \omega \frac{\text{Time-average energy stored in resonator}}{\text{Average power lost in resonator}}$$

- The total unloaded quality factor of a resonator can be found by adding conductor, dielectric, and radiation loss together.

$$\frac{1}{Q_u} = \frac{1}{Q_c} + \frac{1}{Q_d} + \frac{1}{Q_r}$$

EM simulator

- Quality factors Q_c and Q_d for a microstrip line

$$Q = \frac{\beta}{2\alpha} \Rightarrow Q_c = \frac{\pi}{\alpha_c \lambda_g}$$

$$Q_d \geq \frac{\epsilon'}{\epsilon''} = \frac{1}{\tan \delta} \quad \text{or} \quad Q_d = \frac{\pi}{\alpha_d \lambda_g}$$