



- What is the configuration of circuit. Suggest what used for?
- Configuration type? A, AB, B or C.? Explain
- What is voltage at collector transistor  $V_2$  under normal condition? Explain.
- What is voltage at collector transistor  $V_1$  ~~under~~ where  $R_4$  is open circuit.
- How to measure total (base and collector) at  $V_2$  without disconnecting any components
- State purpose of capacitor  $C_2$ ? What effect reducing from  $330\text{nF}$  to  $3.3\text{nF}$  have on operation of circuit?