

Thus:

$$\left| CMRR = \frac{(1+\beta) \pi_E}{(\pi_S + h_{ie})} \approx \frac{\pi_E}{\left(\frac{\pi_S}{\beta} + h_{ib}\right)} \right|$$

c) Differential Mode input resistance:

$$R_d = \frac{V_d}{(i_{S1} - i_{S2})} = \frac{V_{S1}}{i_{S1}} \bigg|_{\substack{V_{S2} = 0 \\ R_{S1} = R_{S2} = 0}}$$

Since $i_{S1} = i_{b1}$ we obtain from the SFG

$$R_d \approx h_{ie} \frac{\Delta}{[1 + (1+\beta) \frac{\pi_E}{h_{ie}}]} = h_{ie} \frac{[h_{ie} + 2(1+\beta)\pi_E]}{[h_{ie} + (1+\beta)\pi_E]}$$

$$\left| R_d \approx 2 h_{ie} \frac{\pi_E + \frac{1}{2} h_{ib}}{\pi_E + h_{ib}} \approx 2 h_{ie} \left(1 - \frac{1}{2} \frac{h_{ib}}{\pi_E}\right) \right|$$

d) Summary $\left(\frac{\pi_S}{\beta} \ll h_{ib}\right)$

$$A_{cm} \approx -\frac{1}{2} \frac{\pi_C}{\pi_E} \frac{1}{\left(1 + \frac{1}{2} \frac{h_{ib}}{\pi_E}\right)} \approx -\frac{1}{2} \frac{\pi_C}{\pi_E}$$

$$A_d \approx \frac{1}{2} \frac{\pi_C}{h_{ib}} \frac{1}{\left(1 + \frac{1}{2} \frac{h_{ib}}{\pi_E}\right)} = \frac{1}{2} \frac{\pi_C}{h_{ib}}$$

$$CMRR \approx \frac{\pi_E}{h_{ib}}$$

$$R_d \approx 2 h_{ie} \frac{1}{\left(1 + \frac{1}{2} \frac{h_{ib}}{\pi_E}\right)} \approx 2 h_{ie}$$

e.g. $\pi_C = \pi_E = 4.7 k\Omega$

$$h_{ib} \approx 30 \Omega$$

$$\beta = 100$$

↓

$$A_{cm} \approx -0.5$$


$$A_d \approx 78$$

$$CMRR = 157$$

$$R_d \approx 6 k\Omega$$

4.2 MOSFET Differential Amplifier

Basic Configuration

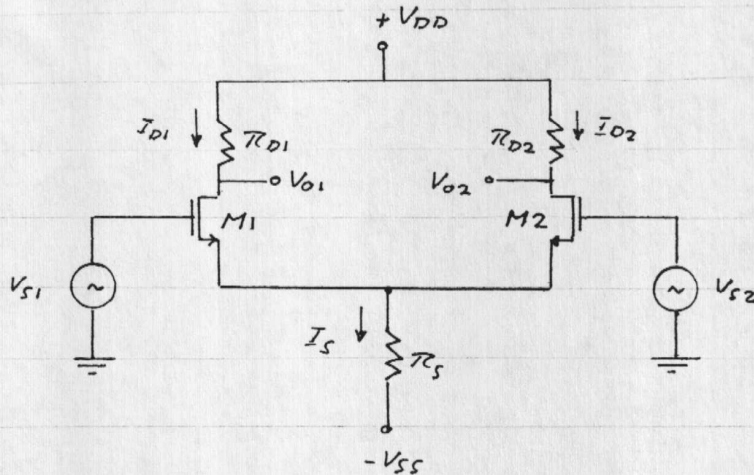

assumption:
M1 and M2
are matched

4.2.1 DC Considerations

Recall: MOSFET in saturation (forward active mode)

$$\left| I_D \approx \frac{1}{2} \underbrace{\frac{W}{L} \mu C_{ox}}_K (V_{GS} - V_t)^2 \right| \quad (V_{DS} > [V_{GS} - V_t] = V_{DSsat})$$

from differential amplifier:

$$\left| I_{D1} = I_{D2} = \frac{1}{2} I_S \right|$$

$$\left| V_{GS1} = V_{GS2} = V_{CM} + V_{SS} - I_S r_s \right|$$

Note: Transconductance parameter for ac model

$$\left| g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{W}{L} \mu C_{ox} (V_{GS} - V_t) = \sqrt{2 \frac{W}{L} \mu C_{ox} I_D} \right|$$