



- What is the configuration of circuit. Suggest what used for ?
- Configuration type ? A, AB, B or C. ? Explain
- What is voltage at collector transistor V_2 under normal condition ? Explain .
- What is voltage at collector transistor V_1 under where R_4 is open circuit .
- How to measure total (base and collector) η . without disconnecting any component