

## EXPERIMENT 9: LISSAJOUS FIGURES

### PREPARATION

Read the attached *Notes on Lissajous Figures*.

**EP-9:** Find the amplitude ratio and phase shift for each of the three Lissajous figures in Fig. E9-4.

### EXPERIMENT

#### Part A -- Phase-Shift Network

The  $RC$  phase-shift network in Fig. E9-1 is prewired in a box, with  $R = 1\text{ k}\Omega$  and  $C = 110\text{ nF}$ . Your task is to measure the amplitude and phase of  $v_B$  while simultaneously monitoring the amplitude and phase of  $v_A$  when terminal  $X$  is grounded with a jumper wire. Use the function generator to supply a sinusoidal input  $v_A$ . Do *not* connect the SYNC output to the scope. Make sure the “Probe attenuation factor” is set at 1 for both channels of the scope.

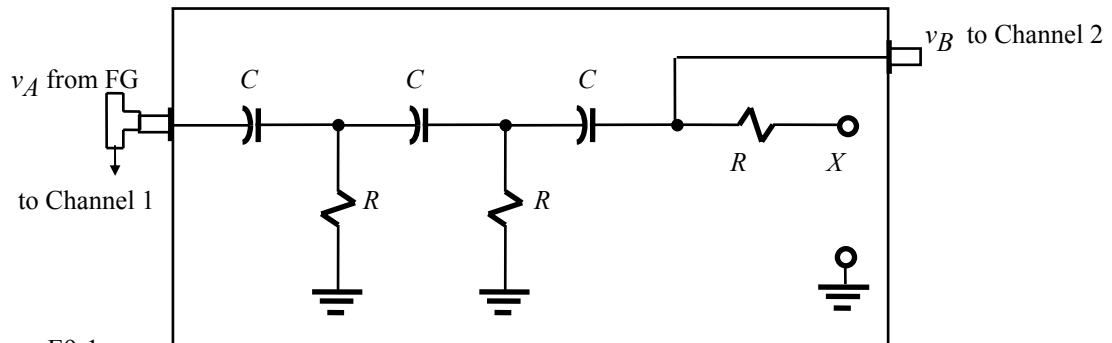


Figure E9-1

1. Keeping terminal  $X$  at ground with a jumper wire, set the FG frequency at  $f = 2\text{ kHz}$ . Apply  $v_A$  to Channel 1 of the scope and  $v_B$  to Channel 2. Set the scope for the XY mode (so  $v_A$  is the horizontal or X deflection). Adjust  $v_A$  for an amplitude of about 8 Vpp. Calculate the amplitude ratio and phase shift from cursor measurements of the resulting Lissajous figure.
2. Press **Autoscale** to switch the scope to dual-trace mode, displaying  $v_A$  and  $v_B$ . Use cursors to measure the time shift  $t_d$  of  $v_B$  by comparing like zero-crossings. Calculate the phase shift via
$$\theta(^{\circ}) = t_d \times f \times 360^{\circ}$$
3. Return to the XY mode, and decrease  $f$  until the Lissajous figure becomes a straight line corresponding to  $\theta = \pm 180^{\circ}$ . (This occurs when  $v_B$  has a much smaller amplitude than  $v_A$ , so you'll need to reduce the volts/div of Channel 2.) Record  $f$  and determine the amplitude ratio for this case.

## Part B -- Phase-Shift Oscillator

The circuit in Fig. E9-2 will spontaneously oscillate at a particular frequency  $f_{osc}$  if  $V_B/V_A \times V_{out}/V_B = 1$  so  $V_{out} = V_A$ . Since the inverting op-amp circuit has  $V_{out}/V_B = -R_F/R = (R_F/R) \angle \pm 180^\circ$ , the phase-shift network must have  $V_B/V_A = a \angle \pm 180^\circ$  at  $f_{osc}$  and oscillation requires  $R_F/R = a^{-1}$  or  $R_F = R/a$ .

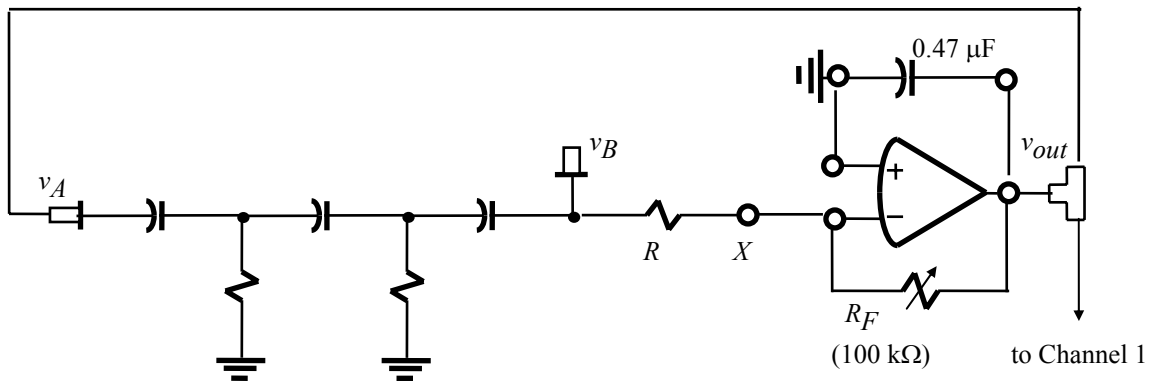


Figure E9-2

Build the circuit in Fig. E9-2 with an op-amp and the  $RC$  phase-shift network (from part A). Use a jumper wire (*not* a BNC cable) to connect  $X$  on the  $RC$  phase-shift network box directly to the op-amp's inverting input. Use a 100-k $\Omega$  digital pot for  $R_F$ , and apply  $v_{out}$  to Channel 1. Connect the  $\pm 5$  V supplies to the op-amp and turn the outputs off via the **Output On/Off** button. Also connect a 0.47- $\mu$ F capacitor between the op-amp's output and ground to prevent unwanted high-frequency oscillation.

1. Set  $R_F = R/a$ , where  $R = 1$  k $\Omega$  and  $a$  is the amplitude ratio found in part A.3. Turn on the power supply outputs (providing  $\pm 5$  V supplies for  $\pm V_{cc}$ ) and the circuit should oscillate. (If not, then increase  $R_F$  until oscillation occurs.) Measure  $f_{osc}$  on the scope and compare it with the value found in part A.3.
2. Increase  $R_F$  and note any changes in the shape or frequency of  $v_{out}$ . Then decrease  $R_F$  until oscillation stops. What is the minimum value of  $R_F$  required to sustain oscillation? How/Why does it differ from the value required to start oscillation?

### POST-LAB:

1. Try to find the transfer functions  $V_B/V_A$  (you may want to use a math modeling tool – e.g. Maple, MathCAD) and  $V_{out}/V_B$  for the circuit shown in Figure E9-2.
2. How could you use these transfer functions to predict what frequency the circuit will oscillate at?
3. How would you design a circuit to produce a square wave oscillator (with an output frequency of 440 Hz) – using (at most) the above circuits, another op-amp and a few more passive components?

## NOTES ON LISSAJOUS FIGURES

Consider any two branch variables in a circuit under ac steady-state conditions, which can be written in general as

$$x(t) = X_m \cos(\omega t + \phi_x) \quad y(t) = Y_m \cos(\omega t + \phi_y)$$

The corresponding phasor ratio is  $\underline{Y}/\underline{X} = (Y_m \angle \phi_y)/(X_m \angle \phi_x) = a \angle \theta$ , where

$$a = Y_m/X_m \quad \theta = \phi_y - \phi_x$$

which are the amplitude ratio and phase shift, respectively.

One way of measuring these quantities involves the elliptical Lissajous figure produced by applying  $x(t)$  to the horizontal input of a scope and  $y(t)$  to the vertical input. As illustrated in Fig. E9-3,  $y_{max}$  appears in the first quadrant when  $-90^\circ < \theta < 90^\circ$  and in the second quadrant when  $90^\circ < \theta < 270^\circ$ .

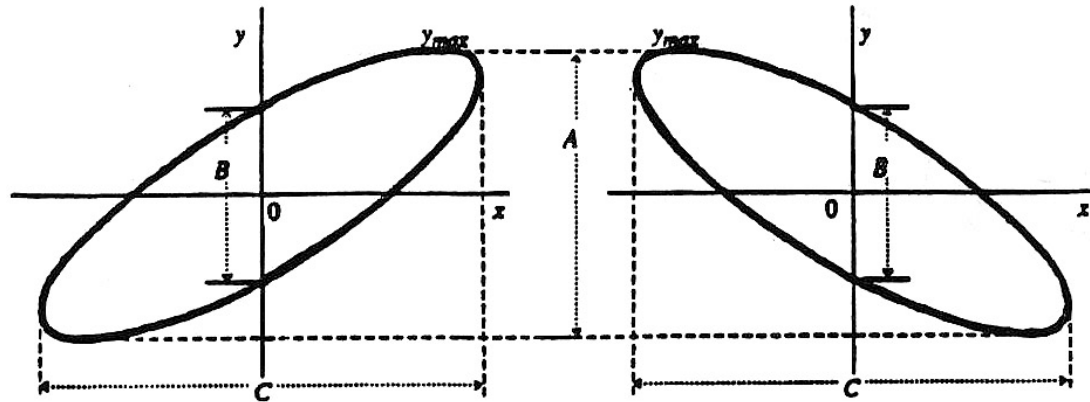


Figure E9-3 (a)  $-90^\circ < \theta < 90^\circ$

(b)  $90^\circ < \theta < 270^\circ$

The peak-to-peak vertical excursion is  $A = 2Y_m$ , and the peak-to-peak horizontal excursion is  $C = 2X_m$ . Hence, we can calculate the amplitude ratio via

$$a = Y_m/X_m = A/C$$

To find the phase shift, we note that  $x(t) = 0$  when  $\omega t + \phi_x = \pm 90^\circ$ , so  $\omega t = -\phi_x \pm 90^\circ$ . Correspondingly, we have  $y(t) = Y_m \cos(\phi_y - \phi_x \pm 90^\circ) = Y_m \cos(\theta \pm 90^\circ) = \pm Y_m \sin \theta$ , so  $B = 2Y_m |\sin \theta| = A |\sin \theta|$ . Hence, we can calculate the phase shift via

$$\begin{aligned} \theta &= \pm \sin^{-1}(B/A) & -90^\circ < \theta < 90^\circ \\ &= 180^\circ \pm \sin^{-1}(B/A) & 90^\circ < \theta < 270^\circ \end{aligned}$$

The quadrant of  $\theta$  must be determined by a dual-trace display or other means.

Figure E9-4 shows Lissajous figures for various values of amplitude ratio and phase shift.

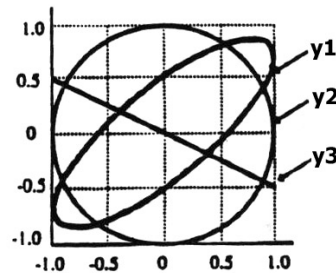


Figure E9-4