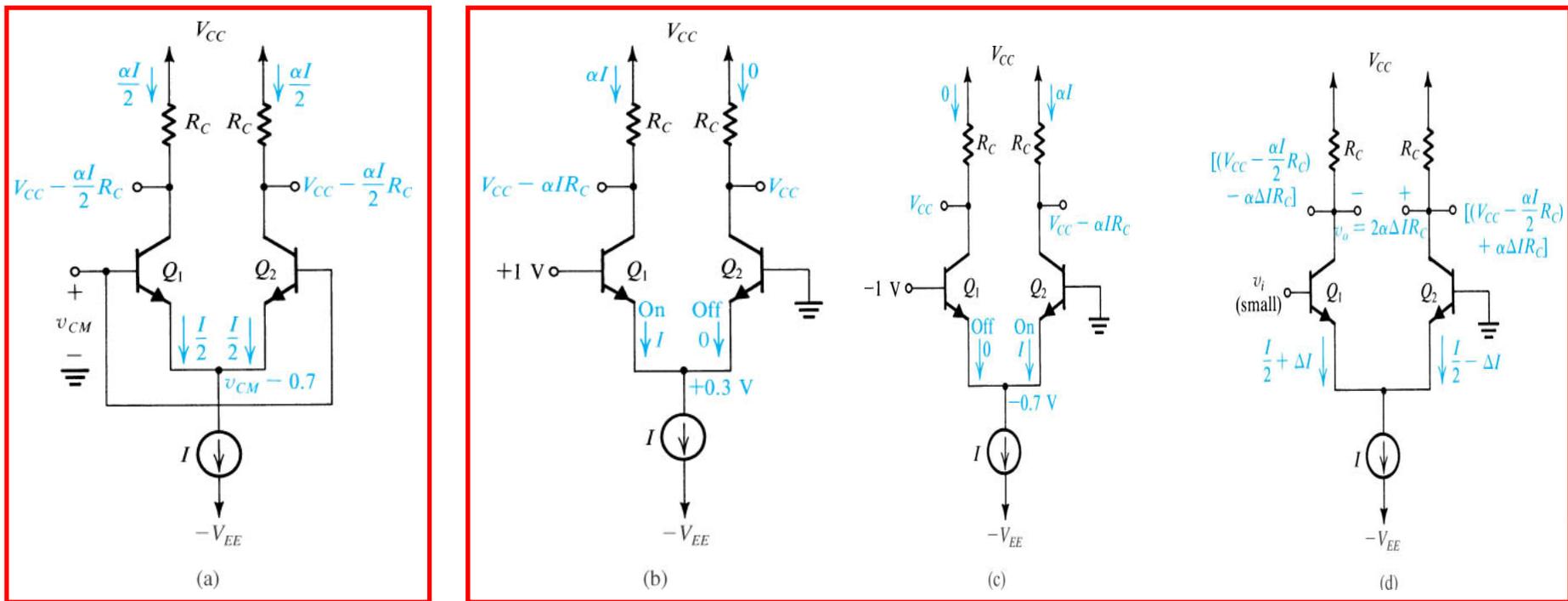


Bipolar Differential Amplifiers: Qualitative Analysis



Common Mode

Differential Mode

Different modes of operation of the BJT differential pair: **(a)** The differential pair with a common-mode input signal v_{CM} . **(b)** The differential pair with a “large” differential input signal. **(c)** The differential pair with a large differential input signal of polarity opposite to that in (b). **(d)** The differential pair with a small differential input signal v_i . Note that we have assumed the bias current source I to be ideal (i.e., it has an infinite output resistance) and thus I remains constant with the change in v_{CM} .

Bipolar Differential Amplifiers: Large Signal Analysis

The exponential relationship applied to each of the two transistors may be written as:

$$i_{E1} = \frac{I_S}{\alpha} e^{(v_{B1}-v_E)/V_T} \quad \text{and} \quad i_{E2} = \frac{I_S}{\alpha} e^{(v_{B2}-v_E)/V_T}$$

These two equations can be combined to obtain

$$\frac{i_{E1}}{i_{E2}} = e^{(v_{B1}-v_{B2})/V_T}$$

which can be manipulated to yield

$$\frac{i_{E1}}{i_{E1} + i_{E2}} = \frac{1}{1 + e^{(v_{B2}-v_{B1})/V_T}} \quad \text{and} \quad \frac{i_{E2}}{i_{E1} + i_{E2}} = \frac{1}{1 + e^{(v_{B1}-v_{B2})/V_T}}$$


From the circuit we have

$$i_{E1} + i_{E2} = I$$


Which may be used to obtain the following expressions for i_{E1} and i_{E2}

$$i_{E1} = \frac{I}{1 + e^{(v_{B2}-v_{B1})/V_T}} \quad \text{and} \quad i_{E2} = \frac{I}{1 + e^{(v_{B1}-v_{B2})/V_T}}$$

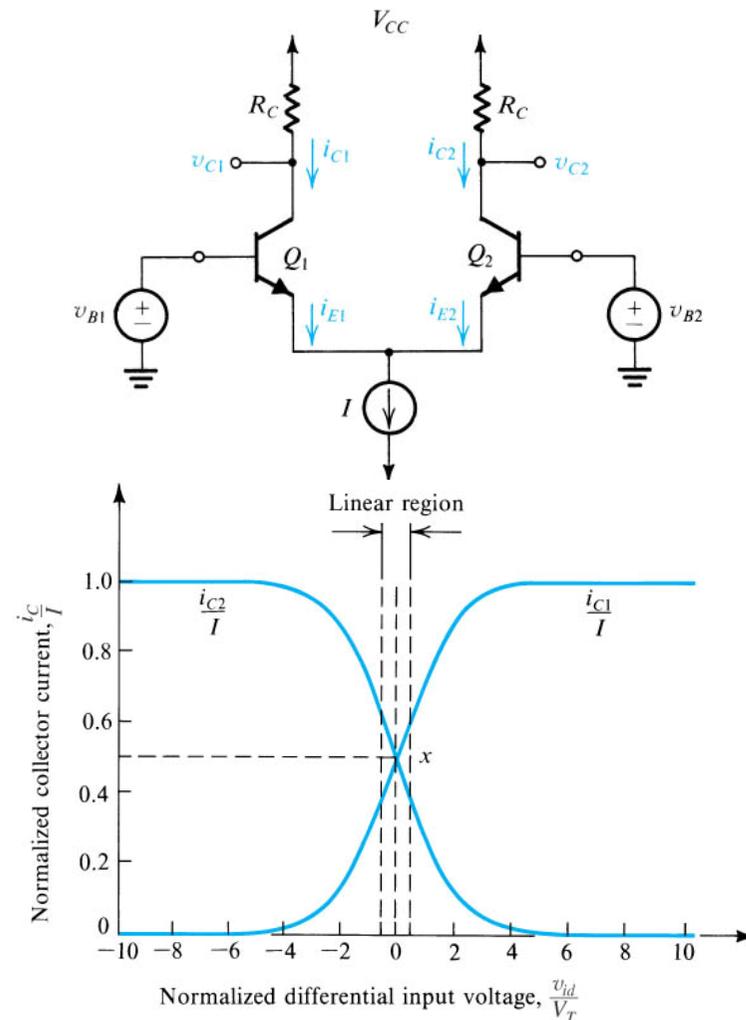
i_{C1} and i_{C2} may be obtained by multiplying i_{E1} and i_{E2} by α which is almost unity and plotted as shown in the figure



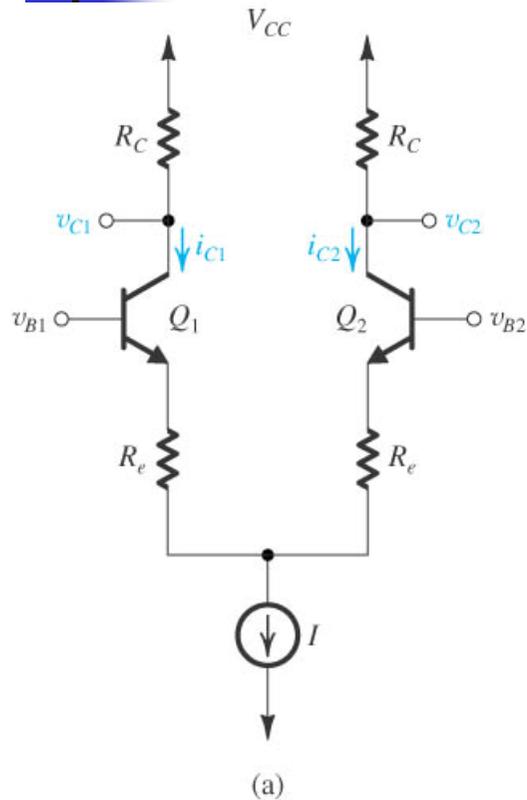Bipolar Differential Amplifiers: Linearization For Your Information



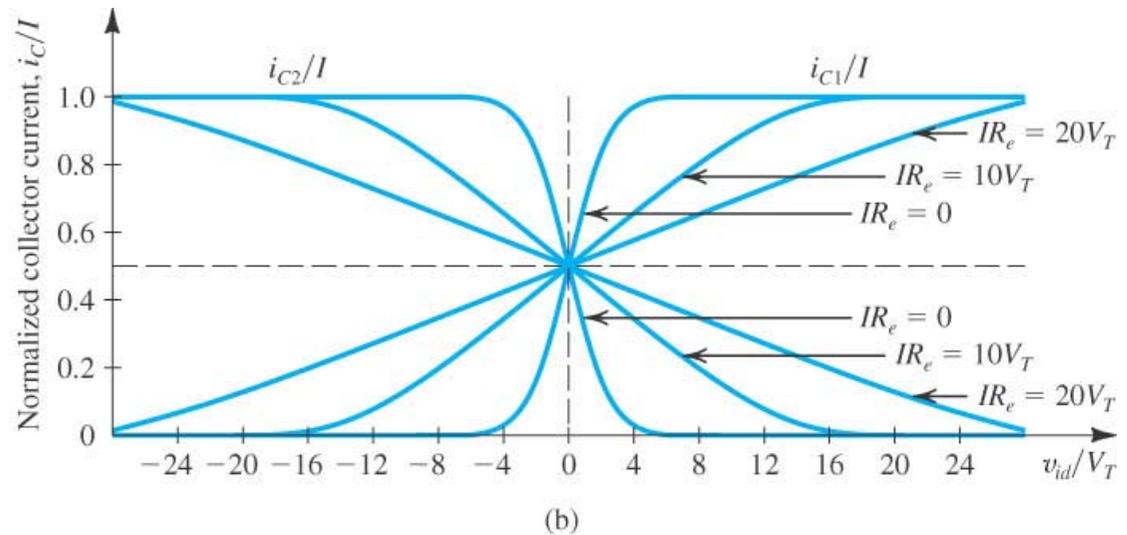What is the role of the degeneration resistance (R_e)?



The transfer characteristics of the BJT differential pair (a) can be linearized (b) (i.e., the linear range of operation can be extended) by including resistances in the emitters.

Bipolar Differential Amplifiers: DC Analysis (Example 1)

- **Problem:** Find the Q-points of transistors in the shown differential amplifier.
- **Given data:** $V_{CC} = V_{EE} = 15\text{ V}$, $R_{EE} = R_C = 75\text{ k}\Omega$, $\beta = 100$
- **Analysis:**


$$I_E = \frac{V_{EE} - V_{BE}}{2R_{EE}} = \frac{(15 - 0.7)\text{ V}}{2(75 \times 10^3)\Omega} = 95.3\mu\text{ A}$$

$$I_C = \alpha I_E = \frac{100}{101} I_E = 94.4\mu\text{ A}$$

$$I_B = \frac{I_C}{\beta} = \frac{94.4\mu\text{ A}}{100} = 0.944\mu\text{ A}$$

$$V_C = 15 - I_C R_C = 7.92\text{ V}$$
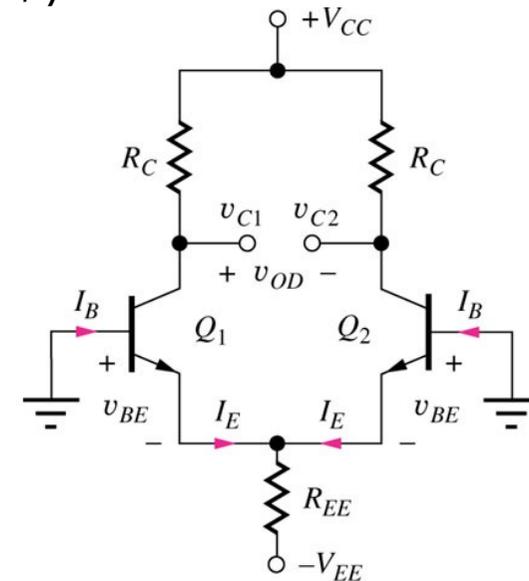
$$V_{CE} = V_C - V_E = 7.92\text{ V} - (-0.7\text{ V}) = 8.62\text{ V}$$



Due to symmetry, both transistors are biased at Q-point ($94.4\mu\text{ A}$, 8.62 V)

Bipolar Common-mode Input Voltage Range


- **Problem:** Find the max. V_{IC} before saturation in the shown differential amplifier.
- **Given data:** $V_{CC} = V_{EE} = 15\text{ V}$, $R_{EE} = R_C = 75\text{ k}\Omega$, $\beta = 100$
- **Analysis:**

We want to find max. V_{IC} while the C-B junction is reverse biased.

$$V_{CB} = V_{CC} - I_C R_C - V_{IC} \geq 0$$

$$I_C = \alpha \frac{V_{IC} - V_{BE} + V_{EE}}{2R_{EE}}$$
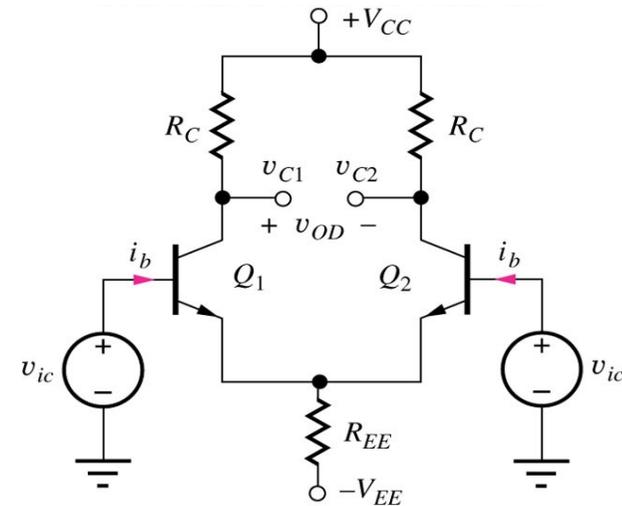
$$\therefore V_{IC} \leq V_{CC} \frac{1 - \alpha \frac{R_C}{2R_{EE}} \frac{(V_{EE} - V_{BE})}{V_{CC}}}{1 + \alpha \frac{R_C}{2R_{EE}}}$$



For symmetrical power supplies ($V_{EE} = V_{CC}$), $V_{EE} \gg V_{BE}$, and $R_C = R_{EE}$,

$$V_{IC} \leq \frac{V_{CC}}{3} = 5\text{ V}$$

Bipolar Differential Amplifiers: DC Analysis (Example 2)

- **Problem:** Find v_E , v_{C1} , and v_{C2} in the shown differential amplifier.
- **Given data:** $V_{CC} = V_{EE} = 5 \text{ V}$, $R_{EE} = R_C = 1 \text{ k}\Omega$, $\alpha \approx 1$, $|V_{BE}| = 0.7 \text{ V}$
- **Analysis:**

We can assume Q1 to be off and Q2 on


$$v_E = +0.7 \text{ V}$$

$$v_{C1} = -5 + R_C * I_{C1} = -5 + 0 = -5 \text{ V}$$


$$I_{E2} = I_E = (5 - 0.7) / 1 = 4.3 \text{ mA}$$

$$I_{C2} = \alpha I_{E2} = 4.3 \text{ mA}$$
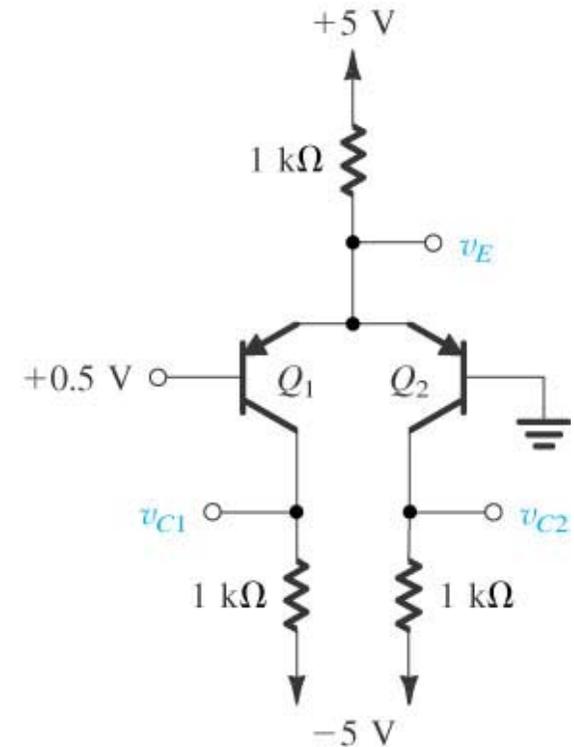
$$v_{C2} = -5 + R_C * I_{C2} = -5 + 4.3 = -0.7 \text{ V}$$



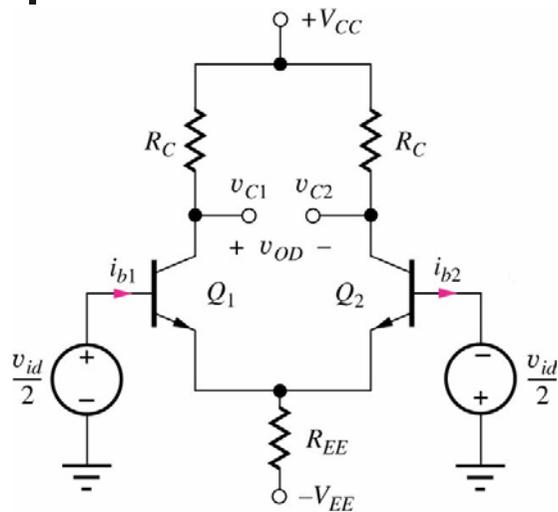Differential-mode Gain and Input Resistance



$$v_3 = \frac{v_{id}}{2} - v_e \quad v_4 = -\frac{v_{id}}{2} - v_e$$


$$(g_m + 1/r_\pi)(v_3 + v_4) = 1/R_{EE} v_e$$

$$\therefore v_e (1/R_{EE} + 2/r_\pi + 2g_m) = 0 \rightarrow v_e = 0$$

Emitter node in differential amplifier represents virtual ground for differential-mode input signals.

$$\therefore v_3 = \frac{v_{id}}{2} \quad v_4 = -\frac{v_{id}}{2}$$

Output signal voltages are:

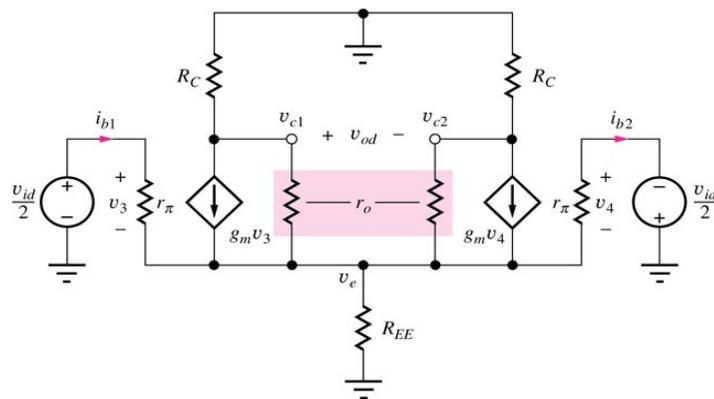

$$v_{c1} = -g_m R_C \frac{v_{id}}{2} \quad v_{c2} = +g_m R_C \frac{v_{id}}{2}$$

$$\therefore v_{od} = -g_m R_C v_{id}$$

Differential-mode Gain and Input Resistance (contd.)

Differential-mode gain for balanced output, $v_{od} = v_{c1} - v_{c2}$ is:

$$A_{dd} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic} = 0} = -g_m R_C$$

If either v_{c1} or v_{c2} is used alone as output, output is said to be single-ended.


$$A_{dd1} = \left. \frac{v_{c1}}{v_{id}} \right|_{v_{ic} = 0} = -\frac{g_m R_C}{2} = \frac{A_{dd}}{2} \quad A_{dd2} = \left. \frac{v_{c2}}{v_{id}} \right|_{v_{ic} = 0} = \frac{g_m R_C}{2} = -\frac{A_{dd}}{2}$$

Differential-mode input resistance is small-signal resistance presented to differential-mode input voltage between the two transistor bases.

$$i_{b1} = \frac{(v_{id}/2)}{r_\pi} \quad \therefore R_{id} = v_{id}/i_{b1} = 2r_\pi$$

If $v_{id} = 0$, $R_{od} = 2(R_C \parallel r_o) \cong 2R_C$. For single-ended outputs, $R_{od} \cong R_C$

Common-mode Gain and Input Resistance

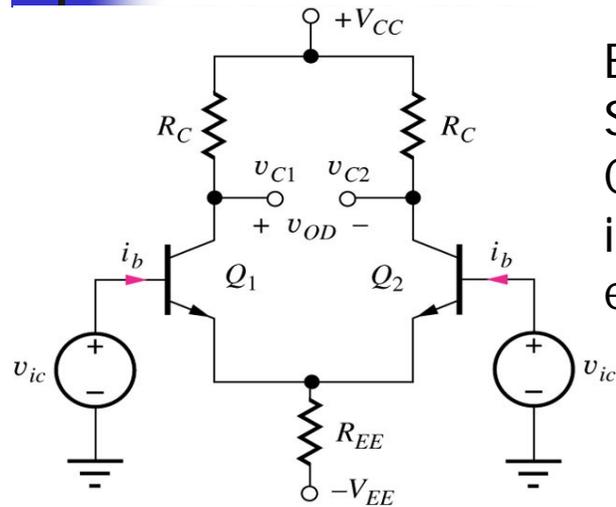


Both arms of differential amplifier are symmetrical. So terminal currents and collector voltages are equal. Characteristics of differential pair with common-mode input are similar to those of a C-E amplifier with large emitter resistor.

$$i_b = \frac{v_{ic}}{r_{\pi} + 2(\beta + 1)R_{EE}}$$


Output voltages are:
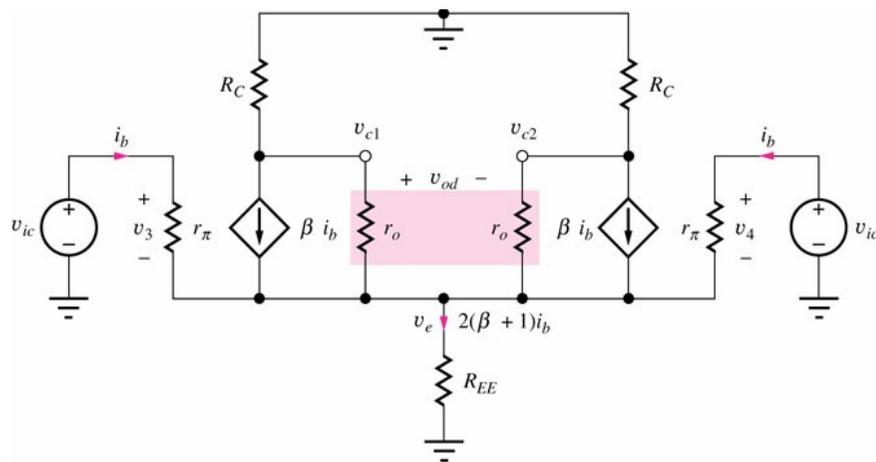
$$v_{c1} = v_{c2} = -\beta i_b R_C = \frac{-\beta R_C}{r_{\pi} + 2(\beta + 1)R_{EE}} v_{ic}$$



$$v_e = 2(\beta + 1)i_b R_{EE}$$
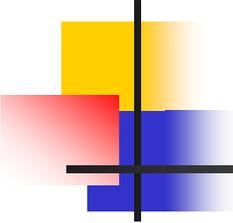
$$= \frac{2(\beta + 1)R_{EE}}{r_{\pi} + 2(\beta + 1)R_{EE}} v_{ic} \cong v_{ic}$$



Common-mode Gain and Input Resistance (contd.)

Common-mode gain is given by:


$$A_{cc} = \left. \frac{v_{oc}}{v_{ic}} \right|_{v_{id}=0} = -\frac{\beta R_C}{r_\pi + 2(\beta + 1)R_{EE}} \cong -\frac{R_C}{2R_{EE}}$$

For $R_C = R_{EE}$, common-mode gain = 0.5. Thus, common-mode output voltage and A_{cc} is 0 if R_{EE} is infinite. This result is obtained since output resistances of transistors are neglected. A more accurate expression is:

$$A_{cc} \cong R_C \left(\frac{1}{\beta r_o} - \frac{1}{2R_{EE}} \right)$$

$v_{od} = v_{c1} - v_{c2} = 0$ Therefore, common-mode conversion gain is found to be 0.
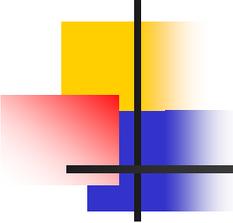
$$R_{ic} = \frac{v_{ic}}{2i_b} = \frac{r_\pi + 2(\beta + 1)R_{EE}}{2} = \frac{r_\pi}{2} + (\beta + 1)R_{EE}$$




Common-Mode Rejection ratio (CMRR)

- Represents ability of amplifier to amplify desired differential-mode input signal and reject undesired common-mode input signal.
- For differential output, common-mode gain of balanced amplifier is zero, CMRR is infinite. For single-ended output,


$$\text{CMRR} = \left| \frac{A_{dm}}{A_{cm}} \right| = \left| \frac{A_{dd} / 2}{A_{cc}} \right| = \frac{1}{2 \left(\frac{1}{\beta r_o g_m} - \frac{1}{2 g_m R_{EE}} \right)} \cong g_m R_{EE}$$

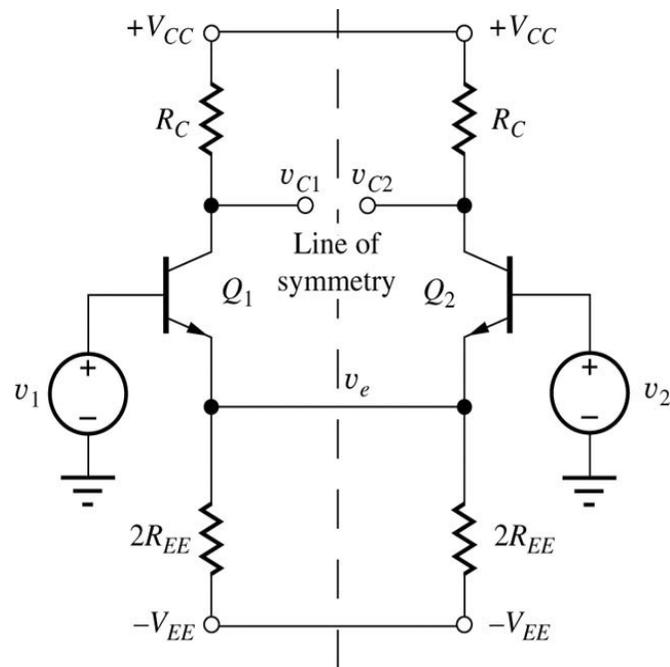Analysis of Differential Amplifiers Using Half-Circuits



- Half-circuits are constructed by first drawing the differential amplifier in a fully symmetrical form- power supplies are split into two equal halves in parallel, emitter resistor is separated into two equal resistors in parallel.
- None of the currents or voltages in the circuit are changed.
- For differential mode signals, points on the line of symmetry are virtual grounds connected to ground for ac analysis
- For common-mode signals, points on line of symmetry are replaced by open circuits.

Bipolar Differential-mode Half-circuits

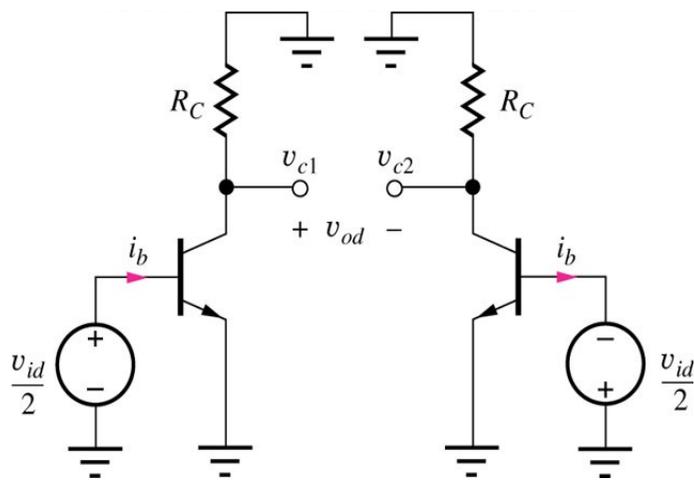

Applying rules for drawing half-circuits, the two power supply lines and emitter become ac grounds. The half-circuit represents a C-E amplifier stage.

Direct analysis of the half-circuits yield:

$$v_{c1} = -g_m R_C \frac{v_{id}}{2} \quad v_{c2} = +g_m R_C \frac{v_{id}}{2}$$


$$v_{od} = v_{c1} - v_{c2} = -g_m R_C v_{id}$$

$$A_{dd} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic}=0} = -g_m R_C$$

$$A_{dd1} = \left. \frac{v_{c1}}{v_{id}} \right|_{v_{ic}=0} = -\frac{g_m R_C}{2} = \frac{A_{dd}}{2}$$

$$R_{id} = v_{id} / i_{b1} = 2r_{\pi} \quad R_{od} = 2(R_C \parallel r_o)$$

Bipolar Common-mode Half-circuits

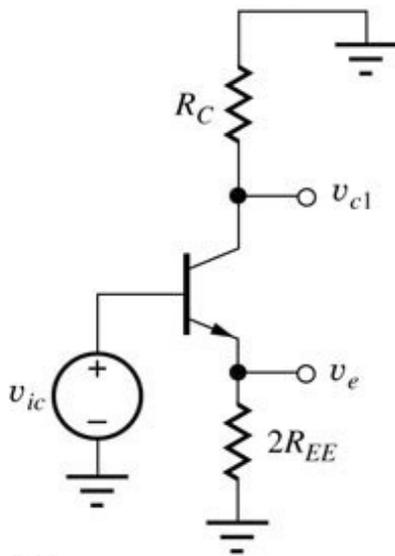

Applying rules for drawing half-circuits, the points at the line of symmetry are open circuited. The half-circuit represents a C-E amplifier stage with an emitter resistance.

Direct analysis of the half-circuits yield:

$$v_{c1} = v_{c2} = -\beta i_b R_C = \frac{-\beta R_C}{r_\pi + 2(\beta + 1)R_{EE}} v_{ic}$$


$$A_{cc} = \left. \frac{v_{oc}}{v_{ic}} \right|_{v_{id}=0} = -\frac{\beta R_C}{r_\pi + 2(\beta + 1)R_{EE}} \cong -\frac{R_C}{2R_{EE}}$$

$$v_{od} = v_{c1} - v_{c2} = 0$$




$$R_{ic} = \frac{v_{ic}}{2i_b} = \frac{r_\pi + 2(\beta + 1)R_{EE}}{2} = \frac{r_\pi}{2} + (\beta + 1)R_{EE}$$

$$\text{CMRR} = \left| \frac{A_{dm}}{A_{cm}} \right| = \left| \frac{A_{dd}/2}{A_{cc}} \right| \cong g_m R_{EE}$$

Biasing with Electronic Current Sources

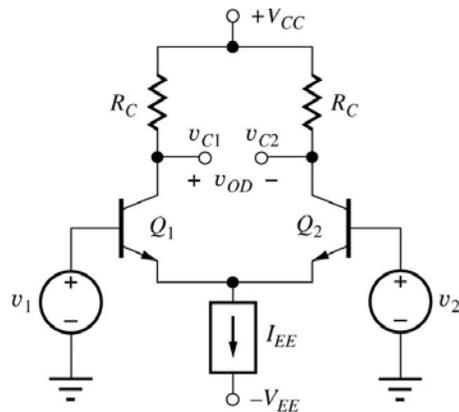

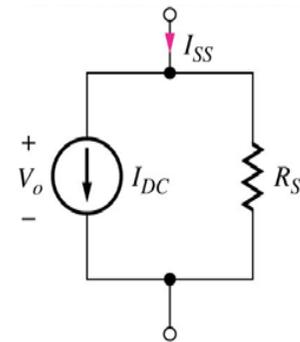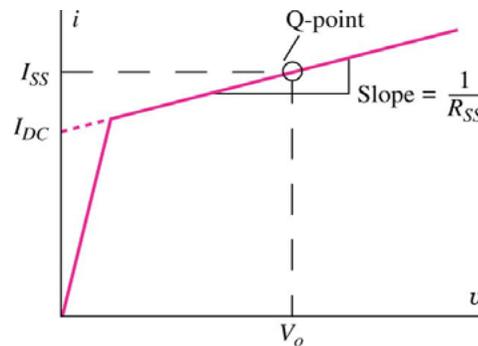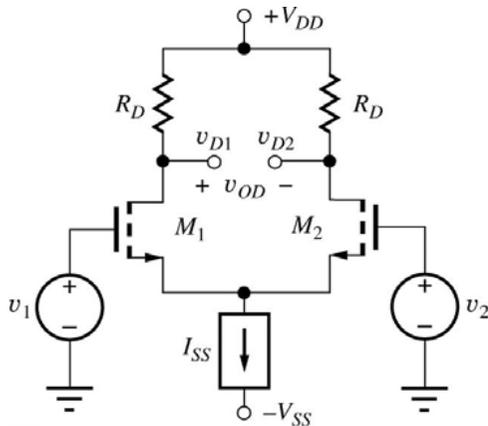- Differential amplifiers are biased using electronic current sources to stabilize the operating point and increase effective value of R_{EE} to improve CMRR
- Electronic current source has a Q-point current of I_{SS} and an output resistance of R_{SS} as shown.
- DC model of the electronic current source is a dc current source, I_{SS} while ac model is a resistance R_{SS} .



$$I_{DC} = I_{SS} - \frac{V_o}{R_{SS}}$$