

E2.2. An amplifier has been connected as shown below, with a signal source and a load connected. In addition, a dc voltage source (V_F) and a resistor (R_F) have been attached to provide feedback. Find the input resistance seen by the signal source with the feedback in place.

