 


S	R	Q	Q'	Remarks
0	0	NC	NC	No Change
0	1	0	1	Reset
1	0	1	0	Set
1	1	Illegal	Illegal	Illegal



Characteristic Table for RS Latch



A Basic SR Latch



<http://elprojects.blogspot.com>

  S-R Latch:
 When $Q=0$ & $Q'=1$ latch is in reset state
 When $Q=1$ & $Q'=0$ latch is in set state
 This is bistable 2 stable states




E	S	R	Q	Q'
0	0	0	Latch	
0	0	1	Latch	
0	1	0	Latch	
0	1	1	Latch	
1	0	0	Latch	
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

  
Gated S-R Latch
 When enabled input is low the S & R inputs are ignored.
 When enabled input is high the output is controlled by S & R inputs.



Inputs			Outputs		Comments
S	R	C	Q	Q'	
0	0	X	Q ₀	Q' ₀	No Change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	?	?	Invalid

 The edge triggered s-r flipflop. The inputs s & r are called synchronous inputs. The data on these inputs are only transferred to the outputs on the triggering edge of the clock pulse.





 

E	D	Q	\bar{Q}
0	0	latch	latch
0	1	latch	latch
1	0	0	1
1	1	1	0

When D is HIGH and E is HIGH the latch is set
When D is LOW and E is HIGH the latch is reset


Regular D-latch response

  

if D is HIGH when clock is applied it is in set state
if D is LOW when clock is applied it is in reset state

Function Table

INPUTS		OUTPUTS
CLK	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

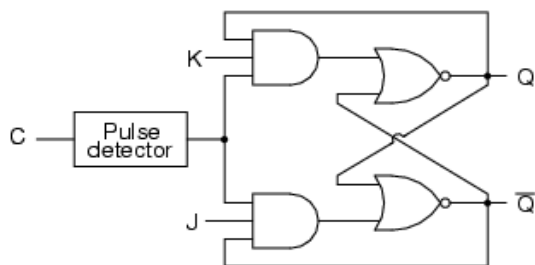

C	J	K	Q	\bar{Q}
0	0	0	latch	latch
0	0	1	0	1
0	1	0	1	0
0	1	1	toggle	toggle
x	0	0	latch	latch
x	0	1	latch	latch
x	1	0	latch	latch
x	1	1	latch	latch

J-K has no invalid state

