



*Fig. 6. A solid-state circuit is the most versatile method of building a negative-ion generator. By adjusting the frequency of IC1 with R3, you can tune the circuit to the resonance of T1 for greatest efficiency. Any 12-volt automobile ignition coil will do for T1.*