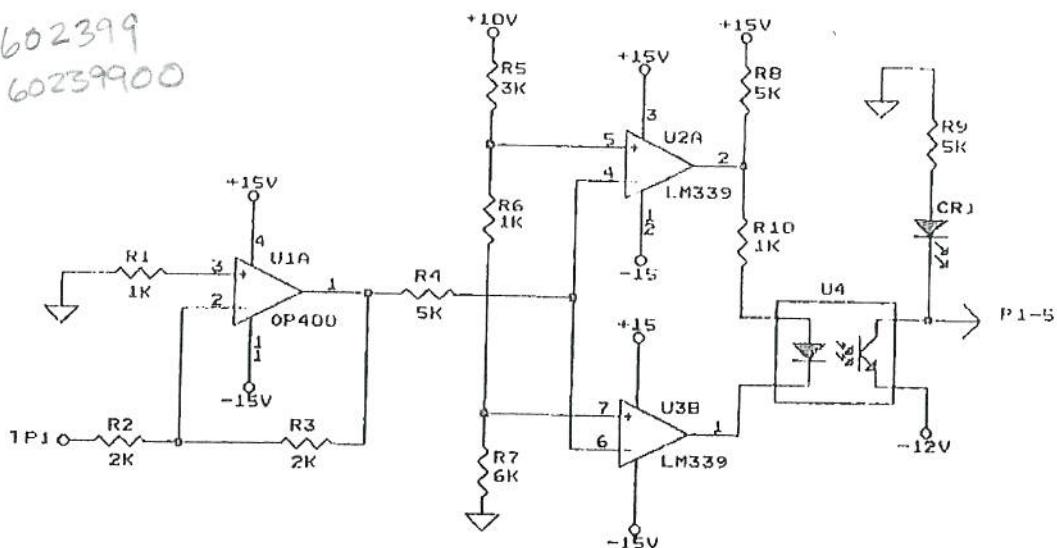


13. What range of voltage at TPI will result in CR1 being on?

OP400

62-602399
62-60239900



A component has failed in the preceding circuit. If the voltage at TPI is too negative, CR1 turns off as designed. The problem is that CR1 is on when TPI is at 0 volts. Which component has failed?