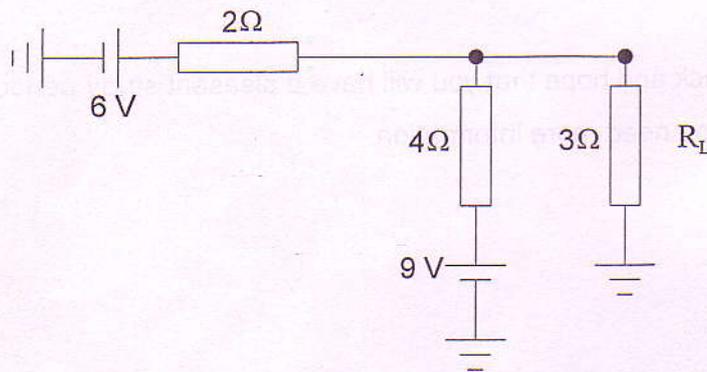


ASSIGNMENT 1

INDUSTRIAL ELECTRONICS N4

QUESTION 1


Determine the value of the current through R_L in the following diagram using Kirchoff's laws (only).



[10]

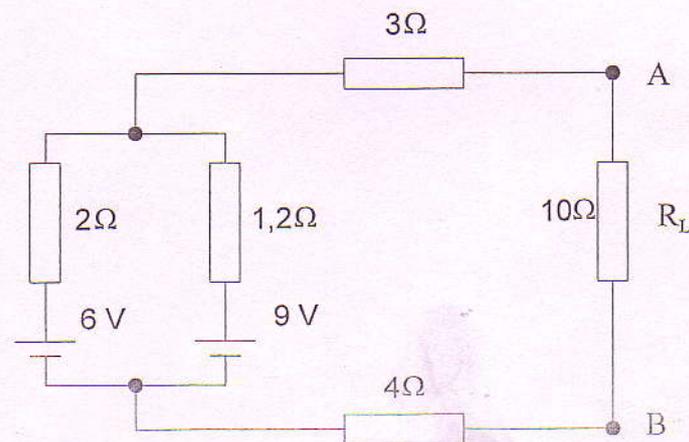QUESTION 2


Use Thevenin's method to calculate the potential difference across R_L in the following figure.



[10]

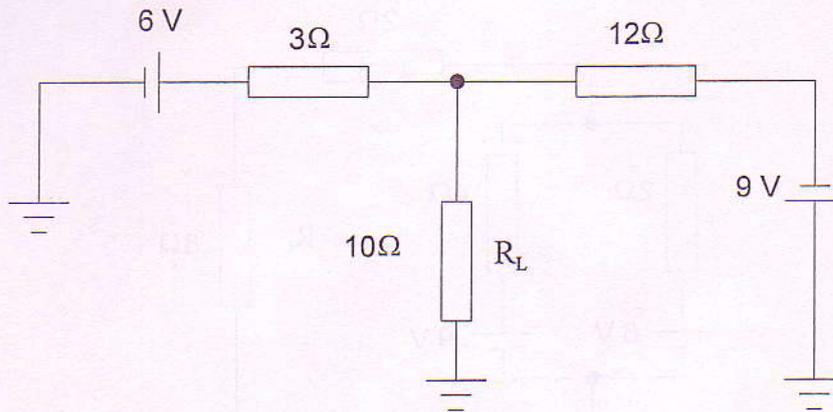QUESTION 3


Use the superposition method to calculate the current flow through R_L in the following figure.



[10]

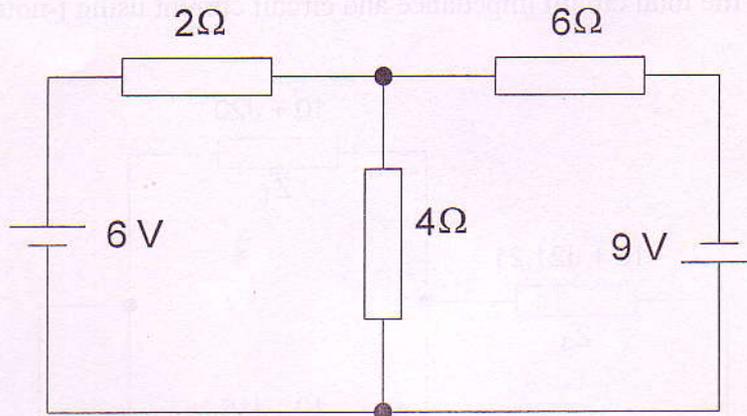QUESTION 4


Use Thevenin's theorem to calculate the current through the $4\ \Omega$ resistor in the following diagram.



[10]

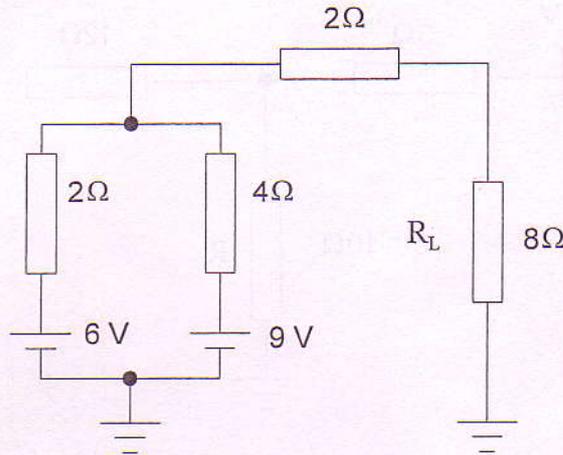QUESTION 5


Use Thevenin's method to calculate the current flow through R_L in the following figure.



[10]

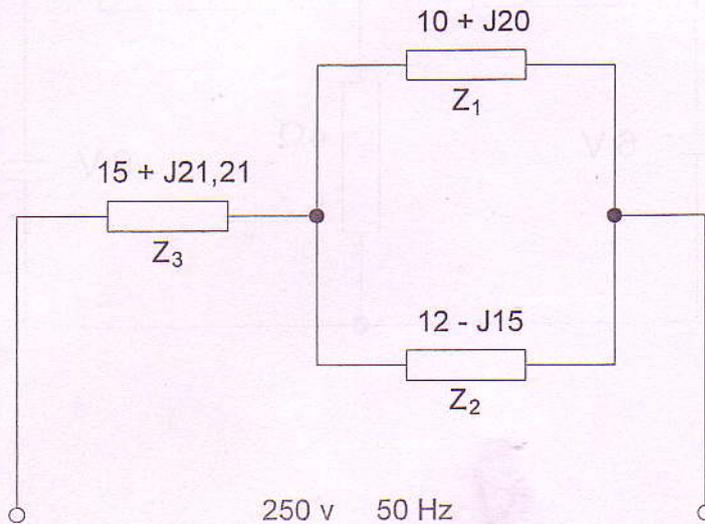QUESTION 6

Calculate the total circuit impedance and circuit current using j-notation only.




[10]

QUESTION 7

If the following circuit is resonant, calculate the following:-

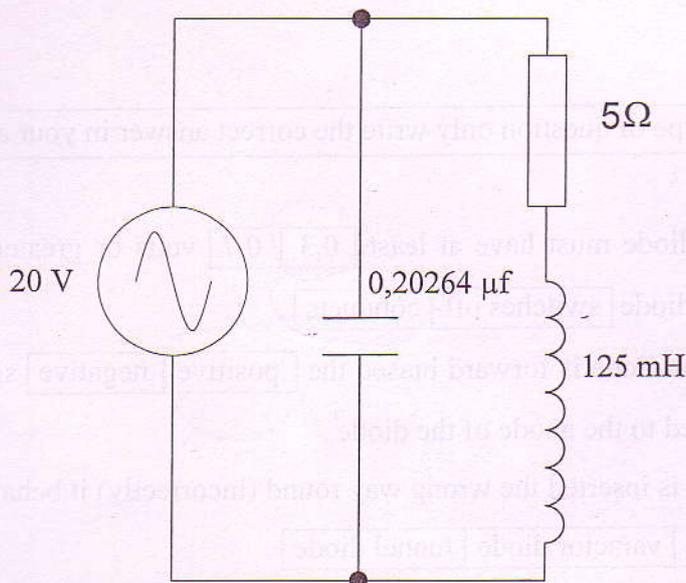- 1) The resonant frequency.
- 2) The current through the coil.
- 3) The current through the capacitor.
- 4) The dynamic impedance.
- 5) The total current from the supply.
- 6) Draw the phasor diagram.




[10]

QUESTION 8

- (a) From the following circuit diagram what power is dissipated in R_L when VR_1 is set to 0Ω ?

{1}

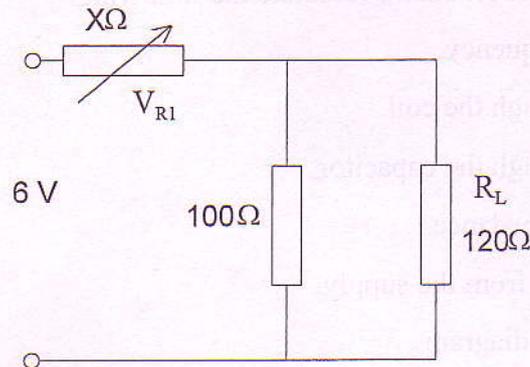- (b) From the circuit diagram what power is dissipated in R_L when V_{R_1} is set to 50Ω ? {1}



(For the following type of question only write the correct answer in your assignment)

- (c) A germanium diode must have at least 0,3 / 0,7 volts or greater forward bias before the diode switches off / conducts. {1}
- (d) When a junction diode is forward biased the positive / negative side of the supply is coupled to the anode of the diode. {1}
- (e) If a zener diode is inserted the wrong way round (incorrectly) it behaves like a junction diode / varactor diode / tunnel diode. {1}
- (f) What is the expected output voltage of a zener diode, specified as $9 \text{ V} \pm 10\%$? {1}
- (g) In a series RLC circuit at resonance the impedance is at minimum / maximum and is equal to R / X_L / X_C . {2}
- (h) In a series RLC circuit at resonance the supply voltage is equal to V_R / V_L / V_C and the circuit current is at a minimum / maximum. {2}

[10]

QUESTION 9

- (a) Define impedance. {2}
 - (b) Define or describe Q factor. {2}
 - (c) In a parallel resonant circuit at resonance the impedance is minimum maximum and the circuit current is at minimum maximum. {2}
 - (d) At resonance $X_L = X_C$ in a series a parallel both series and parallel circuit/s. {1}
 - (e) A series resonant circuit is also known as an acceptor rejector. {1}
 - (f) A parallel resonant circuit is also known as an acceptor rejector. {1}
 - (g) At resonance the power factor of a circuit is 1 0°. {1}
- [10]

QUESTION 10

Explain with the aid of a neat, labelled circuit diagram, how a unijunction transistor can be used to trigger a silicon controlled rectifier (SCR).

[10]

TOTAL [100]

ASSIGNMENT 2


INDUSTRIAL ELECTRONICS N4

QUESTION 1

- (a) A 9 volt regulator uses a 0,5 W zener diode to supply a constant voltage of 9 volts from a 12 volt supply. Calculate a suitable value for the series resistor if the load current is 15 mA. {4}
- (b) A power supply delivers a no-load voltage of 22 volts. At full load the voltage drops to 18 volts. Calculate the percentage voltage regulation. {2}
- [6]

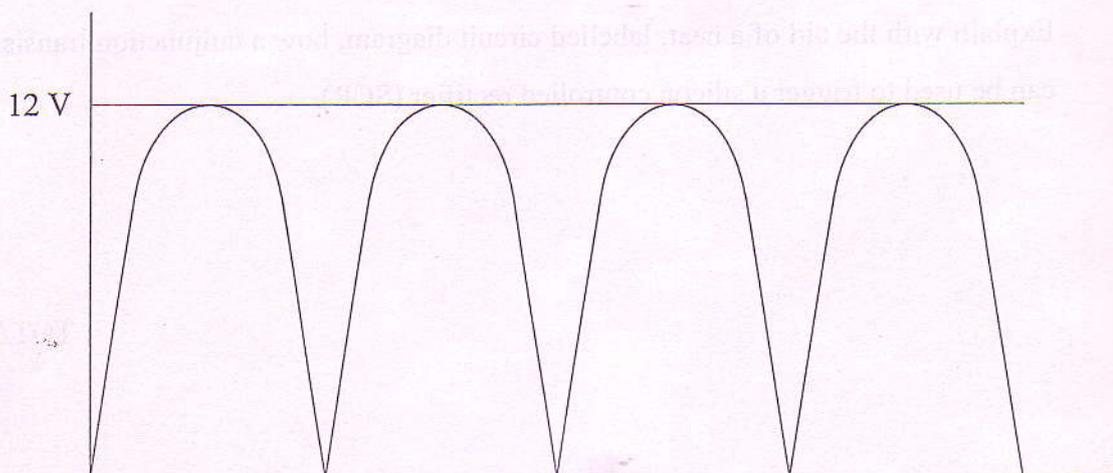QUESTION 2

The following diagram is of the waveform obtained from a full wave bridge rectifier.




Calculate:-

- (1) The average DC voltage. {2}

- (2) The pulsating DC voltage when no filter circuit is used. {1}
 - (3) The transformer's secondary RMS voltage. {1}
 - (4) The output ripple voltage. {2}
 - (5) The ripple factor when no filter is used. {1}
 - (6) The transformer's secondary peak voltage. {1}
 - (7) The transformer's average DC voltage. {1}
 - (8) The peak inverse voltage (PIV). {1}
- [10]

QUESTION 3

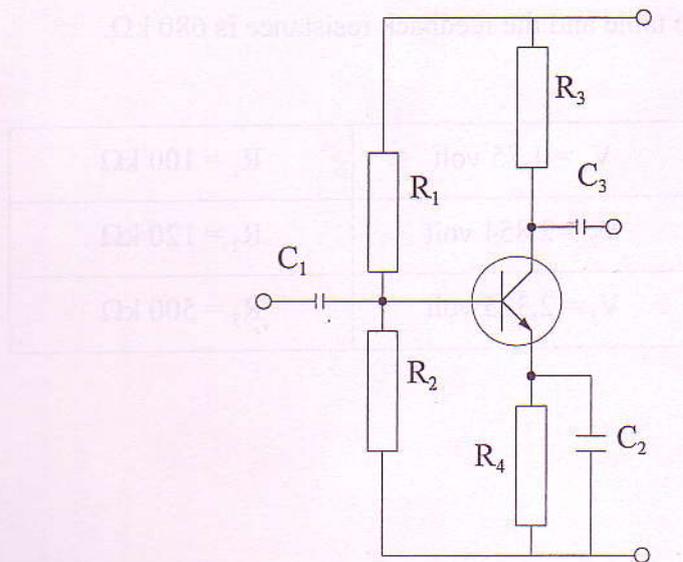- (a) In a CE transistor circuit if the emitter current is 40 mA and the base current is 75 μ A, what is the collector current? {2}
- (b) What is the function of each numbered component in the following diagram? {3}



What is the affect on the amplifier if C2 is removed? Gain will

. {1}

- (c) Draw a neat, fully labelled characteristic curve of a unijunction transistor. {3}
 - (d) A FET is a current voltage controlled device. {1}
 - (e) Draw a neat, fully labelled characteristic curve of a tunnel diode. {4}
- [14]

QUESTION 4

- (a) Draw a neat, fully labelled circuit diagram to show how a triac can be used to control the speed of a small AC motor. The following voltage waveforms must be shown:- i) Input voltage. ii) Voltage across the motor. iii) Voltage across the triac. {6}
- (b) Draw the circuit diagram and calculate the output voltage of a voltage summing op-amp. The values of the input voltages and resistances are given in the table and the feedback resistance is 680 kΩ.

| | |
|--------------------|----------------|
| $V_1 = 1,75$ volt | $R_1 = 100$ kΩ |
| $V_2 = 2,854$ volt | $R_2 = 120$ kΩ |
| $V_3 = 2,325$ volt | $R_3 = 500$ kΩ |

{4}
[10]

QUESTION 5

- (a) Define a transducer. {2}
- (b) What is the basic function of a potentiometer as a transducer? {2}
- (c) Give four requirements of a transducer. {4}

- (d) Give two physical quantities that are converted to electrical output values by transducers. {2}
- [10]

QUESTION 6

- (a) What is a function generator? {2}
- (b) Can a function generator supply different output waveforms simultaneously? Motivate your answer. {2}
- (c) Draw a block diagram of a basic function generator; your drawing must be fully labelled. {4}
- (d) Draw a neat square wave with a mark to space ratio of one. Clearly label the mark, space, a leading edge and a trailing edge. {2}
- [10]

QUESTION 7 (Miscellaneous questions)

- (a) A sine wave is displayed on a CRO screen (oscilloscope). The peak-to-peak distance is 5 cm and the distance between cycles is 4 cm. The volts/cm dial is set to 10v/cm and the time/div is set at 100 μsec/cm. From the following list of possible answers, choose the correct answer for each of the questions.

| | | | | |
|---------|--------|----------|-----------|-----------|
| 25 volt | 5 volt | 0,4 ms | 35,4 volt | 4 ms |
| 50 volt | 250 Hz | 2,5 volt | 2,5 kHz | 17,7 volt |

- (i) Determine the peak-to-peak voltage.
- (ii) Determine the periodic time of the waveform.
- (iii) Determine the maximum value of the voltage.
- (iv) Determine the frequency of the waveform.