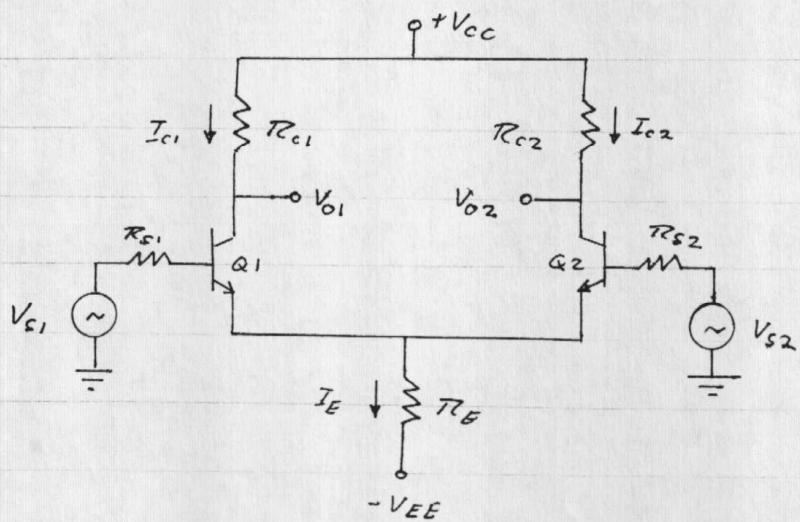


IV-1

IV Operational Amplifier Circuits

4.1 The Differential Amplifier

Basic Configuration



assumption:

Q_1 and Q_2 are
a matched pair

Def Common Mode input voltage:

$$V_{cm} = \frac{V_{S1} + V_{S2}}{2}$$

Common Mode voltage gain:

$$A_{cm} = \frac{V_o}{V_{cm}} = \frac{V_o}{V_{S1}} \Big|_{V_{S2}=V_{S1}}$$

where: $V_o = V_{O2}$ (single ended output)

$V_o = V_{O2} - V_{O1}$ (differential output)

Differential Mode input voltage

$$V_d = (V_{S1} - V_{S2})$$

Differential Mode voltage gain:

$$A_d = \frac{V_o}{V_d} = \frac{V_o}{V_{S1}} \Big|_{V_{S2}=0}$$

Differential Mode input resistance:

$$R_d = \frac{V_d}{(i_{S1} - i_{S2})} = \frac{V_{S1}}{i_{S1}} \Big|_{V_{S2}=0}$$

4.1.1 DC Considerations

$$\bar{I}_{C1} = \bar{I}_{C2} = \frac{1}{2} \bar{I}_E$$

assumption:

$$\bar{I}_E = \frac{(V_{EE} + V_{CM} - V_{BE})}{(\frac{R_E}{\beta} + R_E)} \approx \frac{(V_{EE} + V_{CM} - V_{BE})}{R_E}$$

both Transistors are
operated in forward
active region!

Thus:

$$\bar{I}_{C1} = \bar{I}_{C2} \approx \frac{(V_{EE} + V_{CM} - V_{BE})}{2R_E}$$

$$V_{CE1} = V_{CE2} \approx (V_{cc} + V_{EE}) - (V_{EE} + V_{CM} - V_{BE})(1 + \frac{R_E}{2R_E})$$

Note: $V_{E1} - V_{E2} = V_{CM} - V_{BE}$