

Numerical Example

$$V_{CC} = V_{EE} = 10 \text{ V}$$

$$R_C = R_E = 4.7 \text{ k}\Omega$$

$$V_{BE} = 0.7 \text{ V}$$

Transistors are matched

Case A

$$V_{CM} = 0 \text{ V}$$

$$I_{C1} = I_{C2} \approx 1 \text{ mA}$$

$$V_{CE1} = V_{CE2} \approx 6 \text{ V}$$

$$h_{i1} = h_{i2} \approx 30 \Omega$$

Case B

$$V_{CM} = -2 \text{ V}$$

$$I_{C1} = I_{C2} \approx 0.78 \text{ mA}$$

$$V_{CE1} = V_{CE2} \approx 9 \text{ V}$$

$$h_{i1} = h_{i2} \approx 38 \Omega$$

Case C

$$V_{CM} = +2 \text{ V}$$

$$I_{C1} = I_{C2} \approx 1.2 \text{ mA}$$

$$V_{CE1} = V_{CE2} \approx 3 \text{ V}$$


$$h_{i1} = h_{i2} \approx 25 \Omega$$

Conclusion:

Operating point and thus ac performance of the differential amplifier depends on the applied common mode voltage V_{CM} !

Solution for this problem:

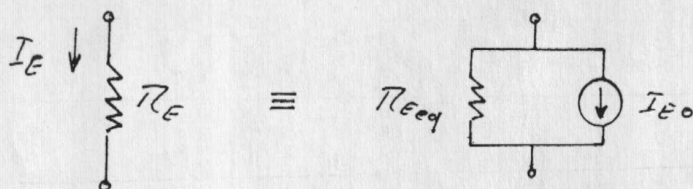
Replace the emitter resistance by a current source!
The bias current is then no longer a function of the applied common mode voltage V_{CM} but depends entirely on the current source circuitry.



Typically:

$$R_{Eeq} \gg R_E$$

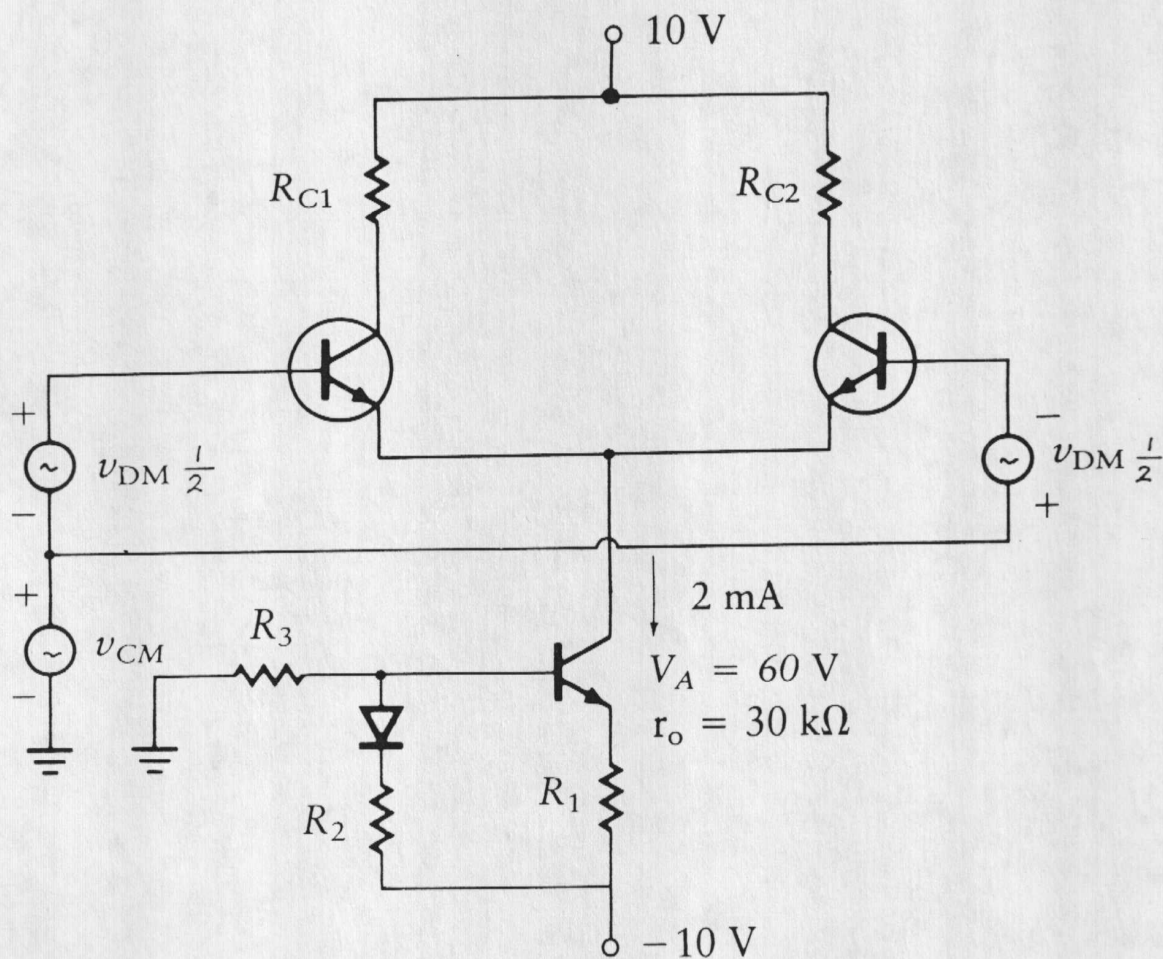Differential Amplifier with Current Source Biasing



Equivalent Emitter Resistance of Current Source

$$\left| r_{Eeq} \approx \frac{1}{h_{oe}} \left(1 + \frac{r_{\pi}}{\left[\frac{r_1 + r_2}{\beta} + h_{ib} \right]} \right) \right| \quad \text{where } \frac{1}{h_{oe}} \approx \frac{V_A}{I_E}$$

$$h_{ib} \approx \frac{V_T}{I_E}$$