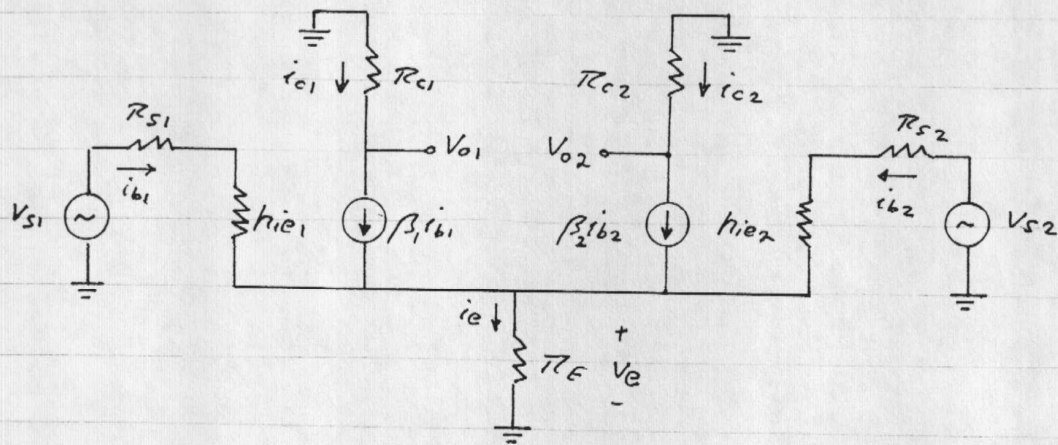
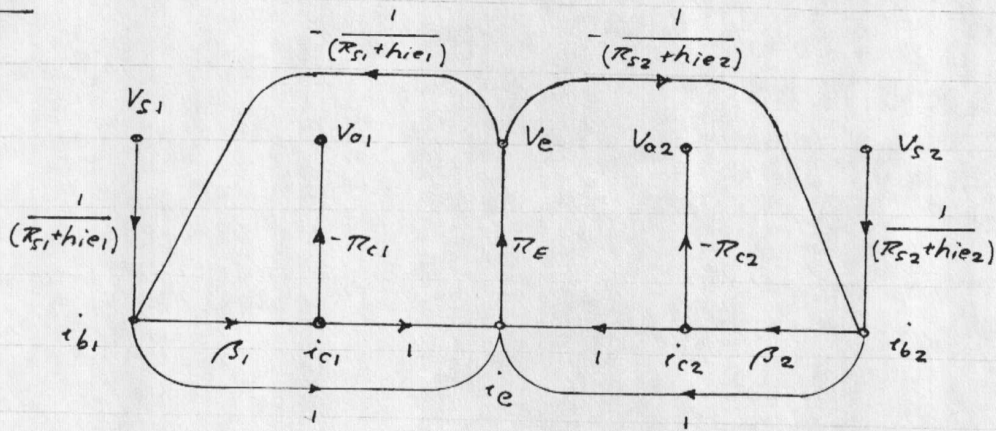


4.1.2 AC Considerations

linear equivalent circuit (h-Parameter model)



SFG



$$\Delta = 1 + (1 + \beta_1) \frac{R_E}{(R_{S1} + h_{ie1})} + (1 + \beta_2) \frac{R_E}{(R_{S2} + h_{ie2})}$$

If Transistors are matched then

$$\Delta = 1 + 2(1 + \beta) \frac{R_E}{(R_S + h_{ie})}$$

2) Common Mode voltage gain: (single-ended)

$$A_{cm} = \frac{V_o}{V_{cm}} = \frac{V_o}{V_{s1}} \Big|_{V_{s2}=V_{s1}} \quad \text{where } \underline{V_o = V_{o2}}$$

Thus:

$$A_{cm} = - \frac{\beta_2 R_{c2}}{(R_{s2} + h_{ie2})} \left[1 + \frac{(1+\beta_1) \pi E}{(R_{s1} + h_{ie1})} - \frac{(1+\beta_1) \pi E}{(R_{s1} + h_{ie1})} \right] \frac{1}{\Delta}$$

If transistors are matched and $R_{s1} = R_{s2} = R_s$, $R_{c1} = R_{c2} = R_c$ we can rewrite the common mode voltage gain as

$$\left\| A_{cm} = - \frac{\beta R_c}{(R_s + h_{ie} + 2[(1+\beta)\pi E])} \approx - \frac{1}{2} \frac{R_c}{(\pi E + \frac{1}{2}[\frac{R_s}{\beta} + h_{ib}])} \right\|$$

b) Differential Mode voltage gain: (single-ended)

$$A_d = \frac{V_o}{V_d} = \frac{V_o}{V_{s1}} \Big|_{V_{s2}=0} \quad \text{where } \underline{V_o = V_{o2}}$$

Thus:

$$A_d = \frac{\beta_2 R_{c2}}{(R_{s2} + h_{ie2})} \frac{(1+\beta_1) \pi E}{(R_{s1} + h_{ie1})} \frac{1}{\Delta}$$

If both branches of the diff. amplifier are identical we obtain:

$$\left\| A_d = \frac{\beta R_c}{(R_s + h_{ie})} \frac{(1+\beta) \pi E}{[\pi E + h_{ie} + 2(1+\beta) \pi E]} \approx \frac{1}{2} \frac{R_c}{(\frac{R_s}{\beta} + h_{ib})} \frac{\pi E}{(\pi E + \frac{1}{2}[\frac{R_s}{\beta} + h_{ib}])} \right\|$$

Def Common Mode Rejection Ratio

$$\left\| CMRR = \frac{|A_d|}{|A_{cm}|} \right\|$$