



Wentworth Institute of Technology

Department of Electrical Engineering and Technology


Review of Digital Circuits

(Chapter 2)


Introduction

- Digital circuits are the essential parts of a microcontroller.
- Although the end users never see them, all operations are performed using digital circuits.
- We begin the review the basics of digital circuits with MOSFET transistors.
- Step by step, we will look at more complex circuitry.

Transistor as a Switch

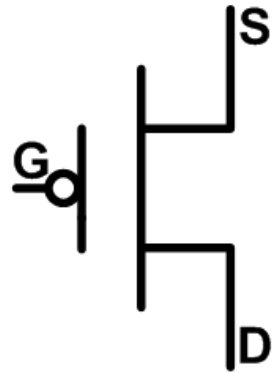

PMOS

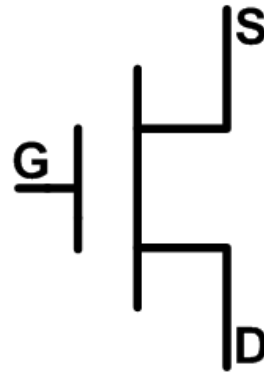

NMOS

NMOS and PMOS MOSFET transistors can be used as a switch.



Logic 0 corresponds to 0 V.

Logic 1 corresponds to V_{cc} .


Logic Gates from Transistors:

NOT Gate


NOT gate

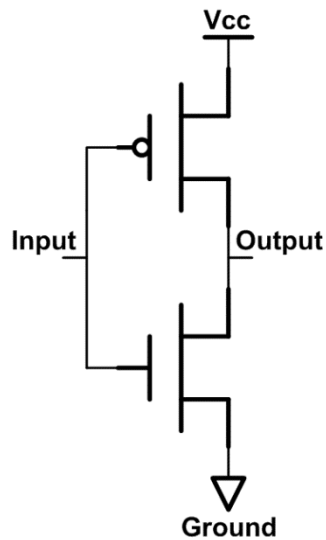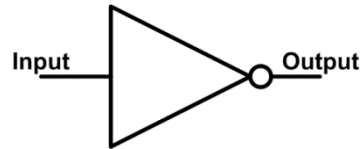

The circuitry

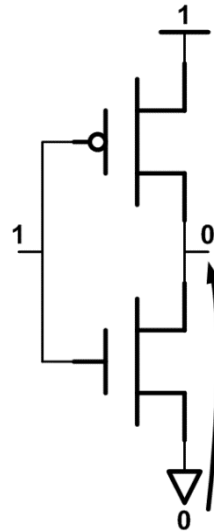

Input is 1


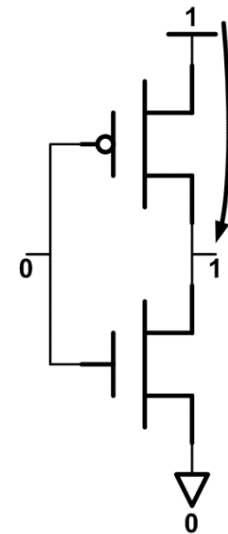


Input is 0

The NOT gate is a simple logic level inverter.



Logic Gates from Transistors: NOR/OR Gates

NOR gate

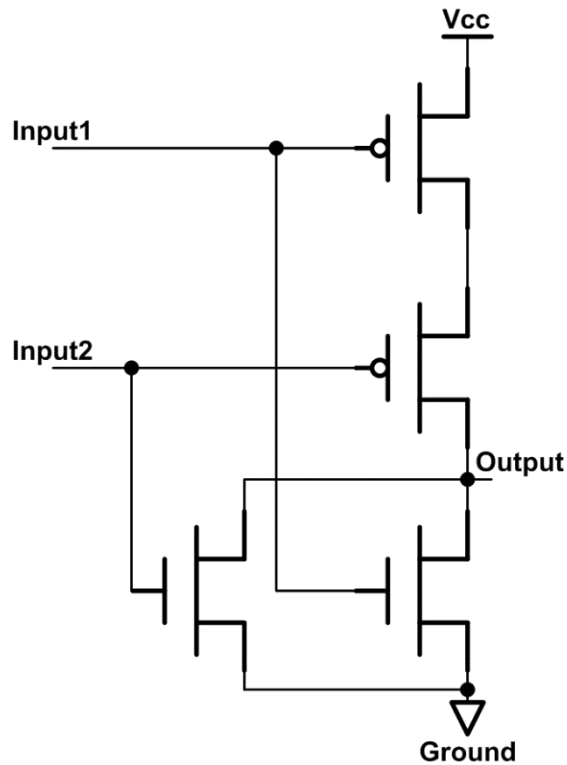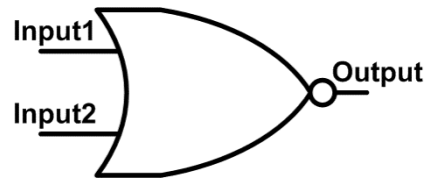

The circuitry

OR gate

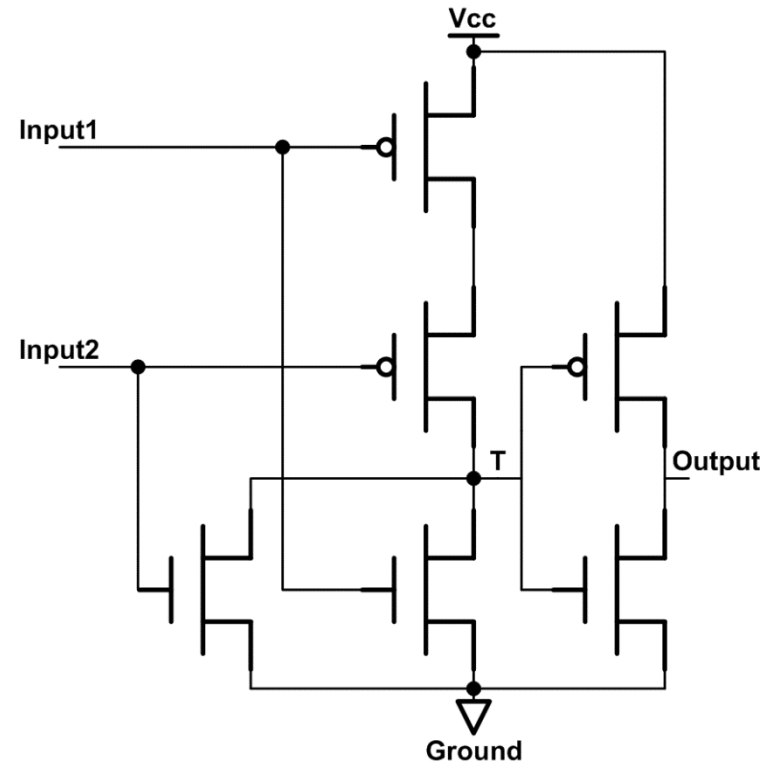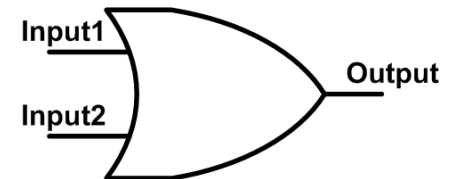


The circuitry

Logic Gates from Transistors:

NOR/OR Gates


NOR gate

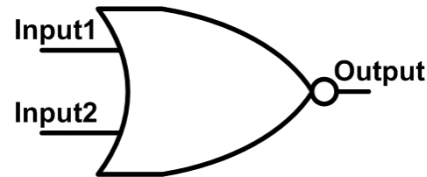

The truth table

Input1	Input2	Output
0	0	1
0	1	0
1	0	0
1	1	0

OR gate

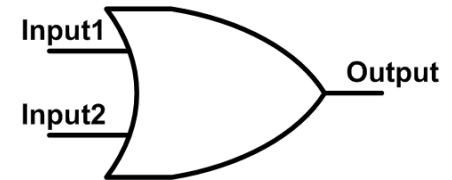



The truth table

Input1	Input2	Output
0	0	0
0	1	1
1	0	1
1	1	1

Logic Gates from Transistors:



NAND/AND Gates

NAND gate

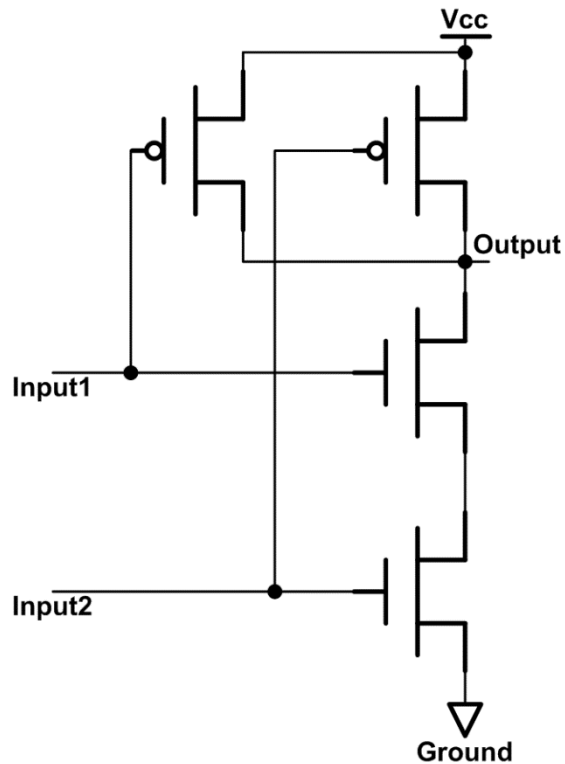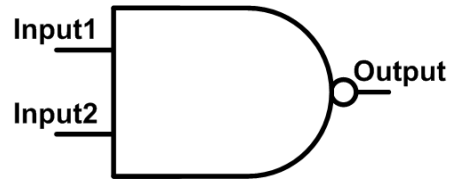

The circuitry

AND gate

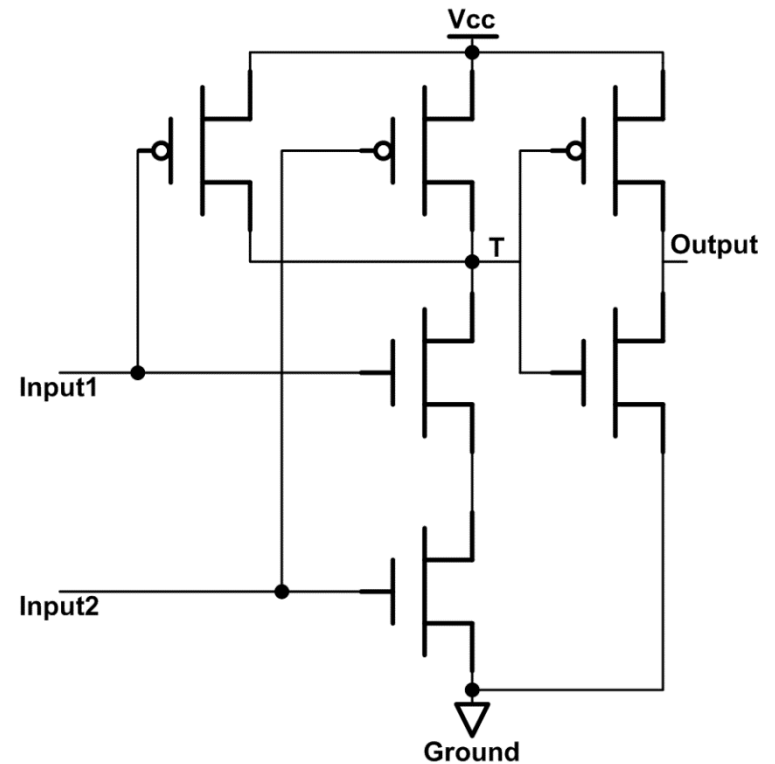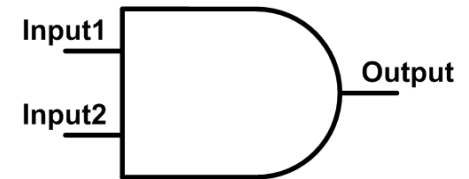


The circuitry


Logic Gates from Transistors:

NAND/AND Gates

NAND gate

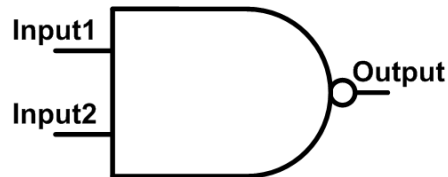

AND gate

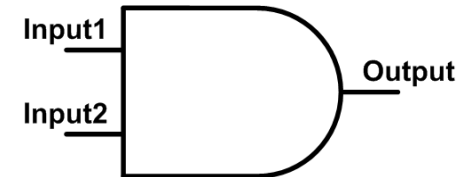

The truth table


Input1	Input2	Output
0	0	1
0	1	1
1	0	1
1	1	0

The truth table

Input1	Input2	Output
0	0	0
0	1	0
1	0	0
1	1	1


Logic Gates from Transistors

XOR gate

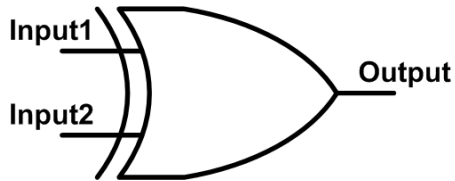

The truth table

Input1	Input2	Output
0	0	0
0	1	1
1	0	1
1	1	0


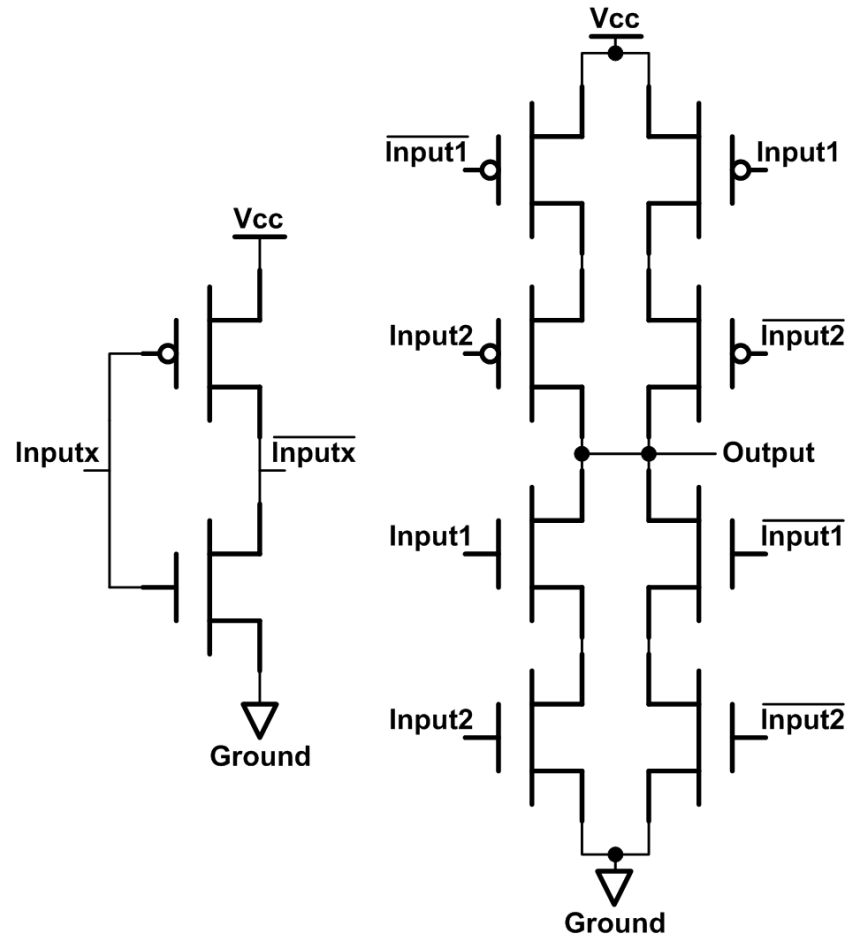


The circuitry

Logic Gates from Transistors:

Transmission gate

Transmission gate

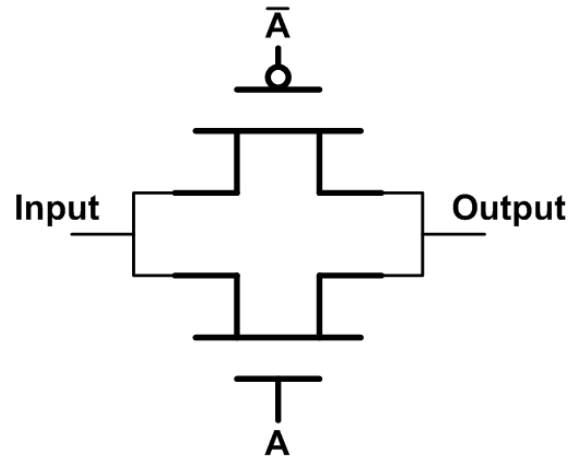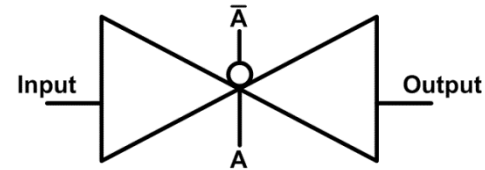


The circuitry

Combinational Circuits from Gates:


Decoder

Two to four decoder

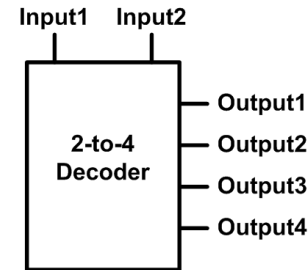

The truth table


Input1	Input2	Output1	Output2	Output3	Output4
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

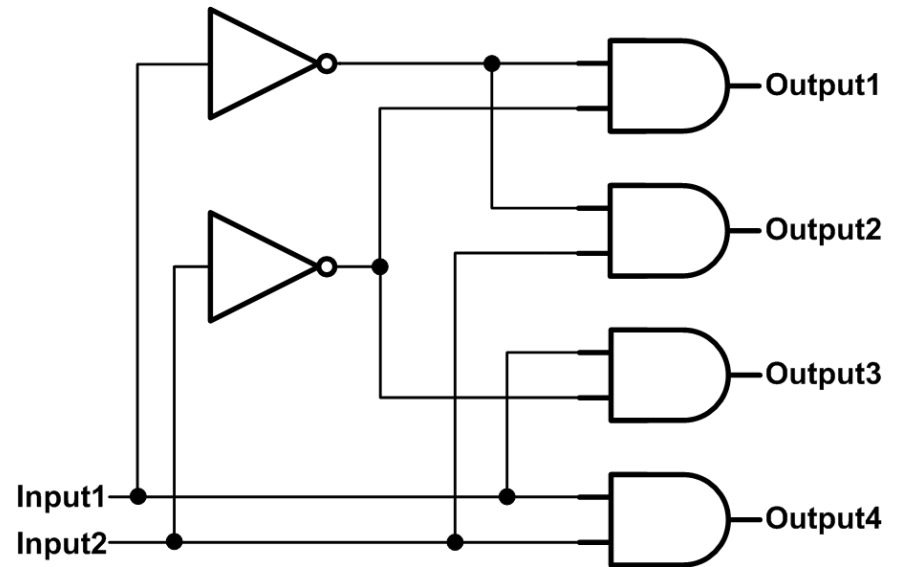

The circuitry


Combinational Circuits from Gates: Multiplexer

Multiplexer

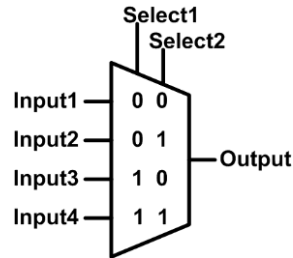

The truth table


Select1	Select2	Output
0	0	Input1
0	1	Input2
1	0	Input3
1	1	Input4

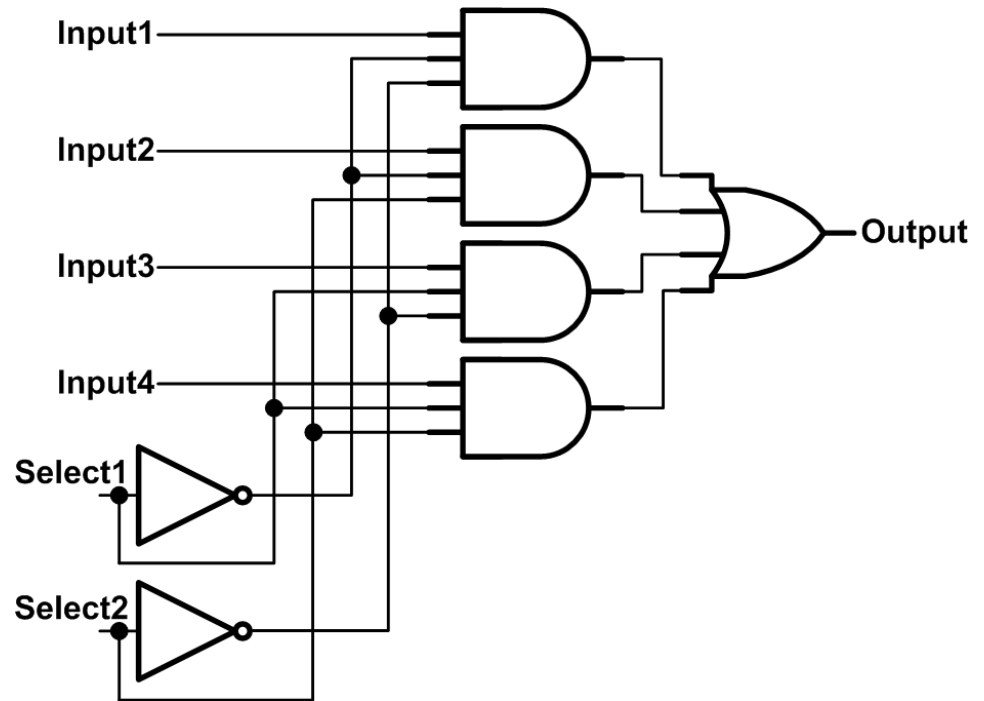

The circuitry


Combinational Circuits from Gates: Half Adder

Half Adder

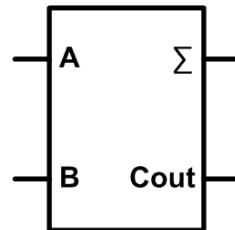

The truth table

A	B	Σ	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

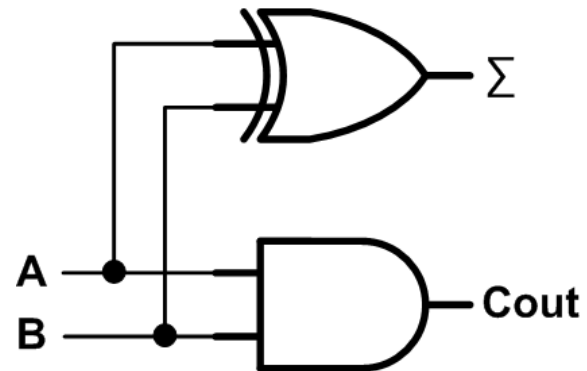


The circuitry

Combinational Circuits from Gates:


Full Adder

Full Adder

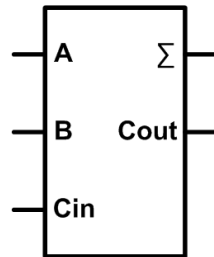

The truth table

A	B	Cin	Σ	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

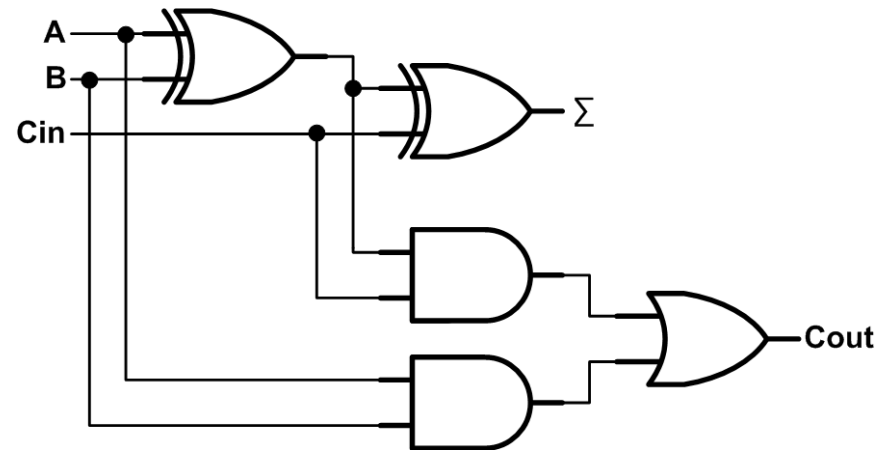


The circuitry

Sequential Circuits from Gates: S-R Latch

S-R Latch

The truth table


S	R	Q	\overline{Q}
0	0	Not Allowed	
0	1	0	1
1	0	1	0
1	1	Q	\overline{Q}

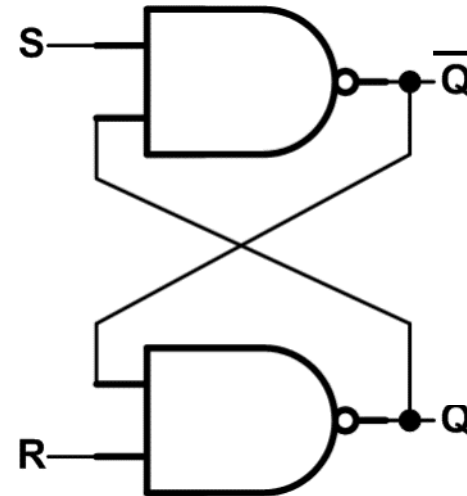



The circuitry

Sequential Circuits from Gates: D Latch


D Latch

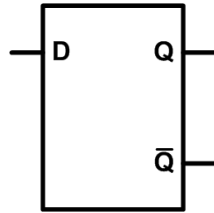

Gated D Latch

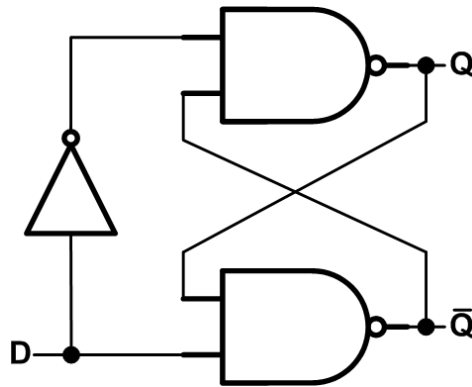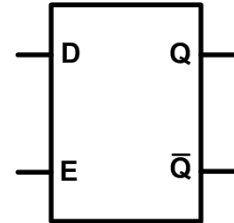

The circuitry


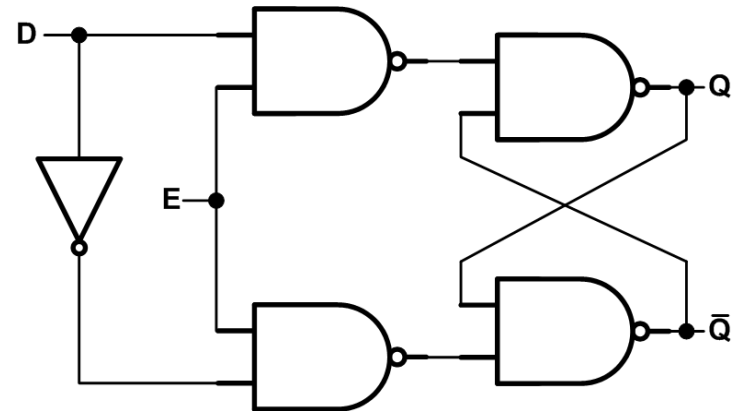


The circuitry

Sequential Circuits from Gates:



Master-slave flip flop

Master-slave flip flop

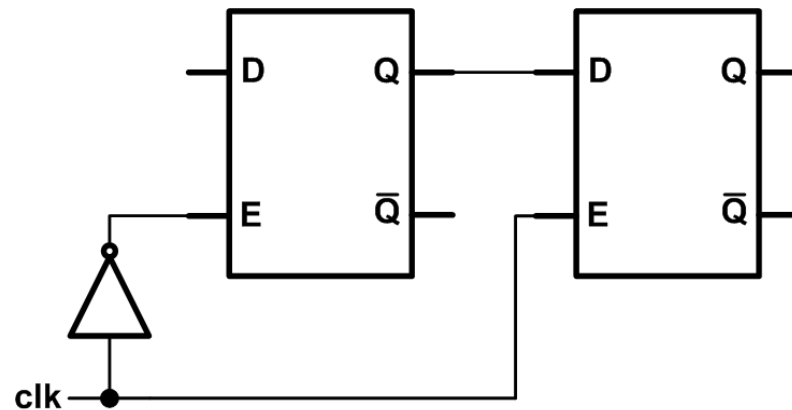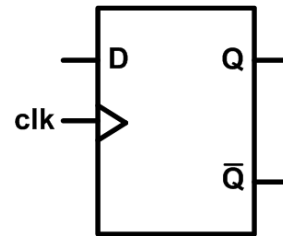


Sequential Circuits from Gates: Counter

Counter

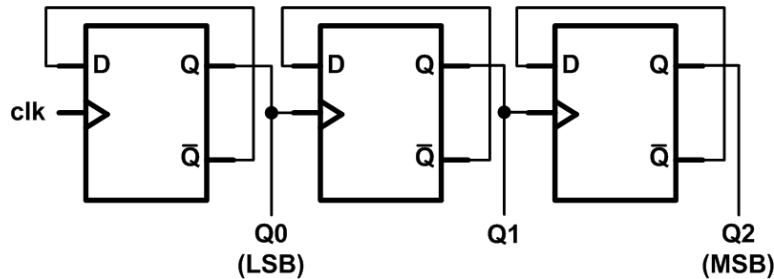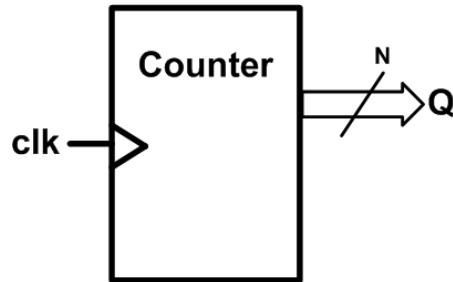

Three bit ripple counter


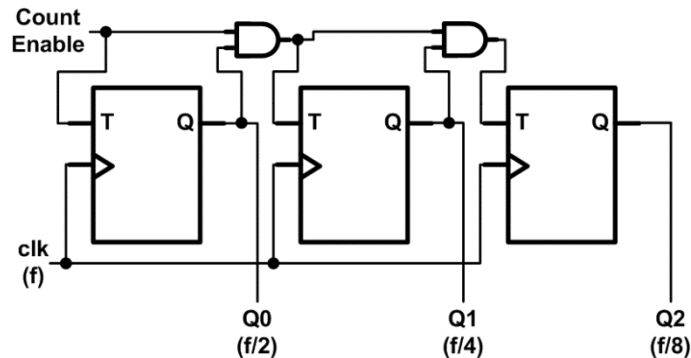


Three bit synchronous counter


Sequential Circuits from Gates:

4 bit register

4 bit register

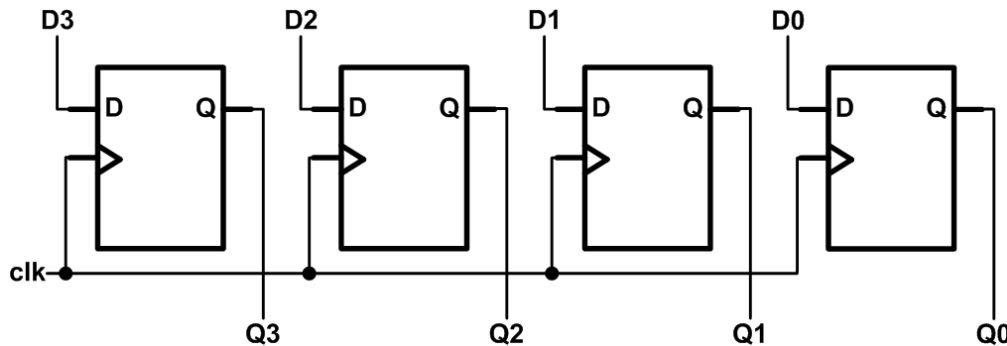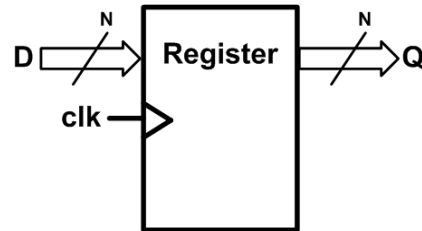

Four bit register

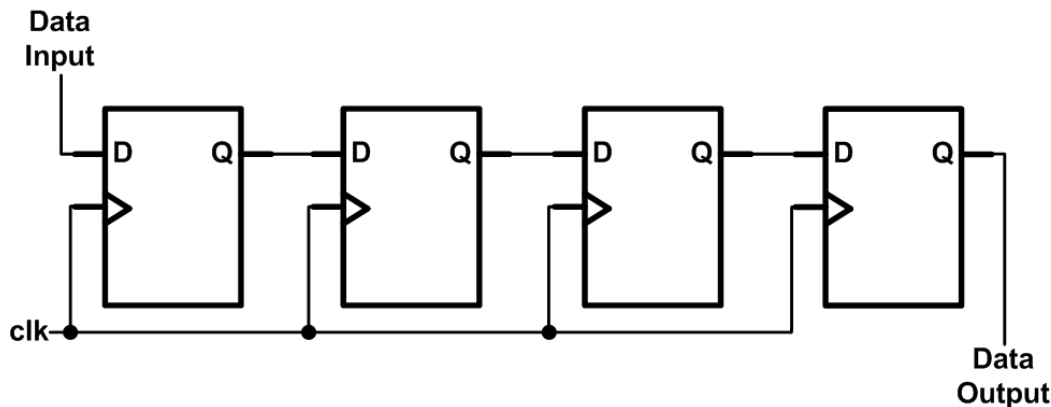

Serial in serial out
shift register

Sequential Circuits from Gates:

Memory from registers

Memory from registers

