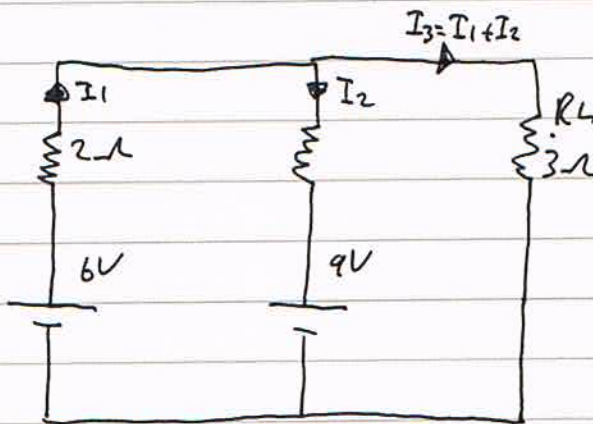


Q1



$$\begin{aligned} I_1 &= \frac{V_1}{R_1} \\ &= \frac{6}{2} \\ &= 3A \end{aligned}$$


$$\begin{aligned} I_2 &= \frac{V_2}{R_2} \\ &= \frac{9}{4} \\ &= 2.25A \end{aligned}$$

$$I_3 = I_1 + I_2$$

$$= 3 + 2.25$$

$$= 5.25A$$

Q2

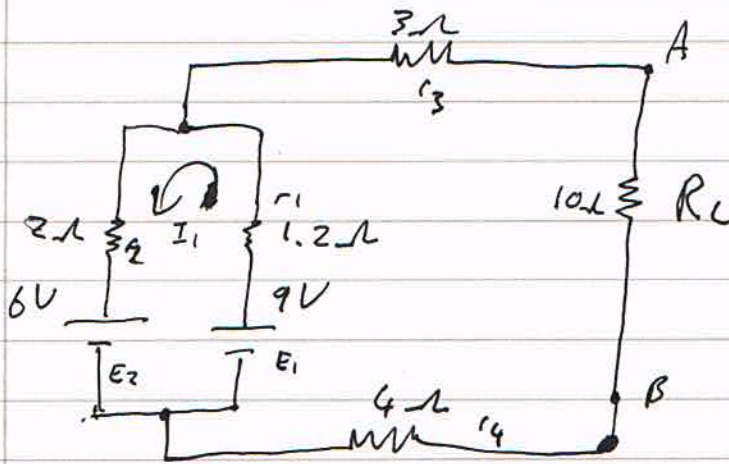

$$i) I_1 = \frac{9-6}{2+1.2}$$

$$= 0.9375 A$$

P.D across AB

$$E = E_1 - I_1 r_1$$

$$= 9 - (0.9375)(1.2)$$

$$= 7.875 V$$

ii) Remove emf sources:

$$r = \frac{r_1 \times r_2}{r_1 + r_2} + r_3 + r_4$$


$$= \frac{(1.2 \times 2)}{1.2 + 2} + 3 + 4$$

$$= \cancel{0.75} + 7.75 \Omega$$



$$iii) I = \frac{E}{r + R} = \frac{7.875}{7.75 + 10}$$

$$= 0.443 A$$

Equivalent circuit:

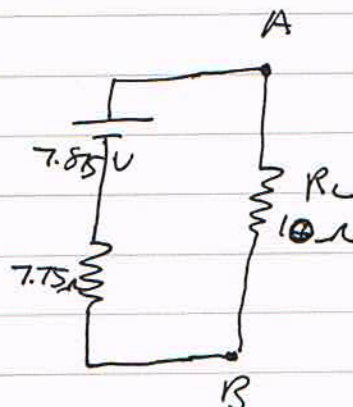

Q3

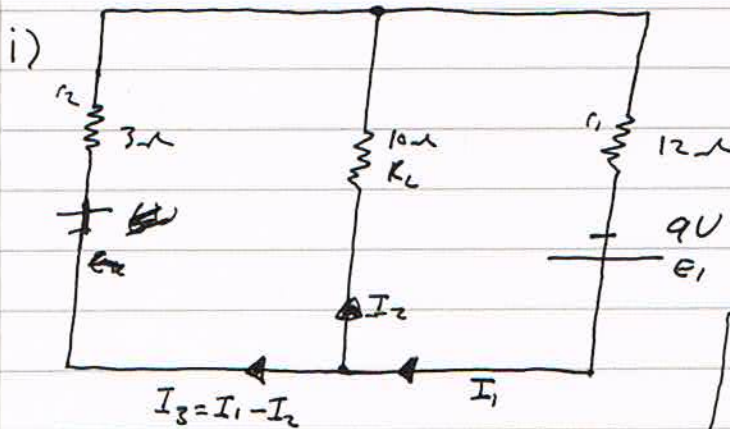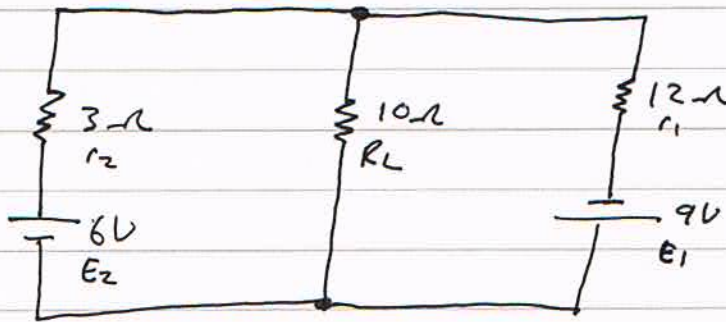

Remove E_2

$$R_{//} = \frac{3 \times 10}{3 + 10} = 2.308 \Omega$$

$$I_1 = \frac{9}{12 + 2.308} = 0.629 \text{ A}$$


$$I_2 = \left(\frac{10}{10 + 3} \right) I_1 = \frac{10}{13} (0.629) = 0.4838 \text{ A}$$

$$I_3 = 0.629 - 0.483 = 0.146 \text{ A}$$

$$R_{//} = \frac{10 \times 12}{10 + 12} = 5.455 \Omega$$

$$I_4 = \frac{6}{3 + 5.455} = 0.709 \text{ A}$$

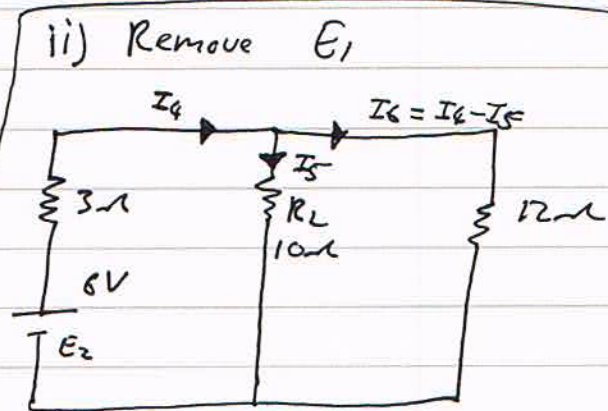
$$I_5 = \left(\frac{10}{10 + 12} \right) I_4 = 0.322 \text{ A}$$



$$I_6 = 0.709 - 0.322 = 0.387 \text{ A}$$

$$\therefore I_{RL} = 0.387 - 0.146 = 0.241 \text{ A}$$

Q4

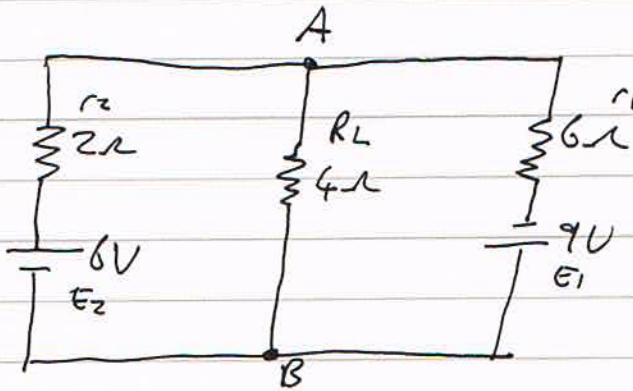

$$i) I = \frac{6+9}{2+6}$$


$$= 1.875 A$$

P.D. across AB:

$$E = 9 - (1.875)2$$

$$= 2.25 V$$


ii) Remove emf sources

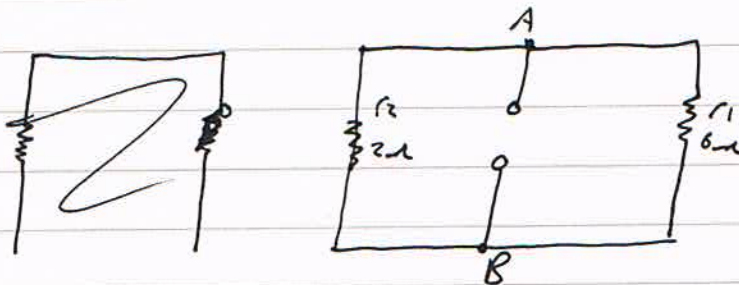

$$r = \frac{2 \times 6}{2+6}$$

$$= 1.5 \Omega$$

iii) Th. equivalent

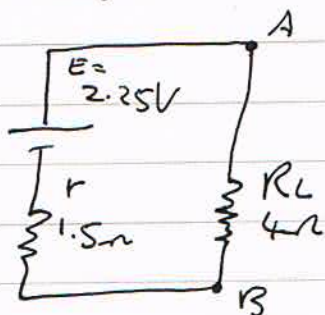


$$I_{RL} = \frac{E}{r+R}$$

$$= \frac{2.25}{1.5+4}$$

$$= 0.409 A$$

Q5

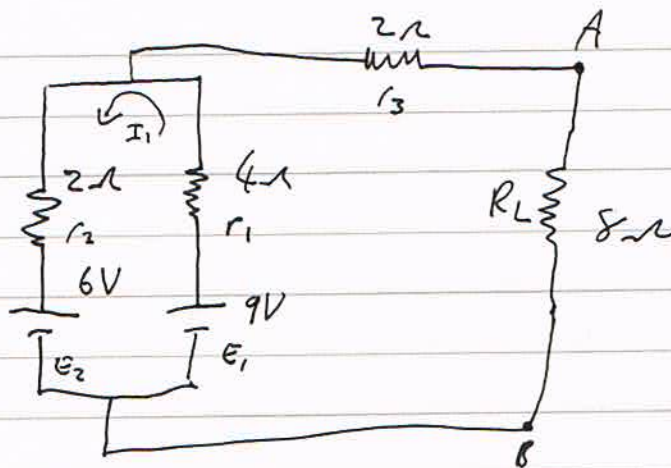


$$\begin{aligned} \text{i) } I_1 &= \frac{E_1 - E_2}{r_1 + r_2} \\ &= \frac{9 - 6}{4 + 2} \\ &= 0.5 \text{ A} \end{aligned}$$

P.D. across AB:


$$\begin{aligned} E &= E_1 - I_1 r_1 \\ &= 9 - (0.5 \times 4) \\ &= 7 \text{ V} \end{aligned}$$

ii) Remove emf sources:

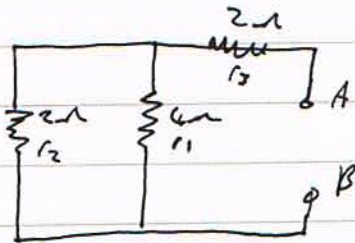


$$\begin{aligned} R_T &= \frac{(2 \times 4)}{2 + 4} + 2 \\ &= 3.333 \Omega \end{aligned}$$

iii) Th. equiv circuit

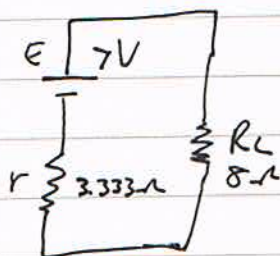

$$\begin{aligned} I &= \frac{E}{r + R_L} \\ &= \frac{7}{3.333 + 8} \\ &= 0.617 \text{ A} \end{aligned}$$

Q6

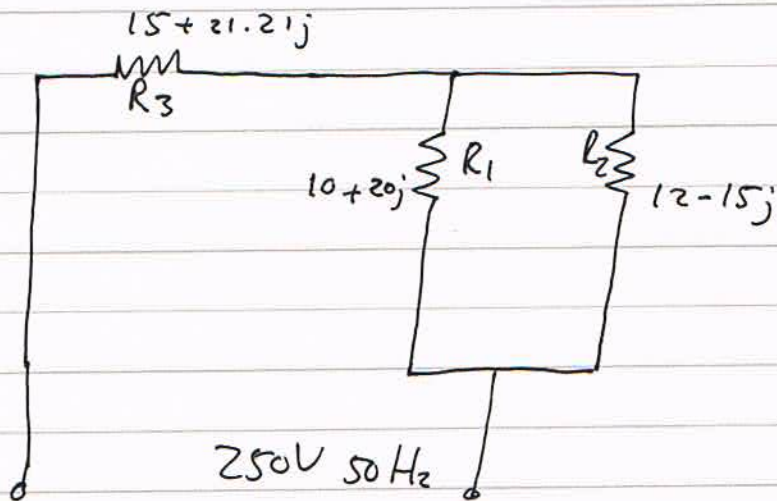

$$R_{11} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$i) R_1 \times R_2$$

$$= (10 + 20j)(12 - 15j)$$

$$= 120 + 240j - 150j - 300j^2$$

$$= 120 + 90j + 300$$

$$= 420 + 90j$$

$$ii) R_1 + R_2$$

$$= (10 + 20j) + (12 - 15j)$$

$$= 22 + 5j$$

$$iii) \frac{420 + 90j}{22 + 5j}$$

$$= \frac{420 + 90j}{22 + 5j} \times \frac{22 - 5j}{22 - 5j}$$

$$= \frac{9240 + 1980j - 2100j - 450j^2}{22^2 - 5^2}$$

$$= \frac{9690 - 120j}{22}$$

$$= \frac{4845}{11} - \frac{60}{11}j$$

$$iv) R_{11} + R_3 = R_T$$

$$\therefore \left(\frac{4845}{11} - \frac{60}{11}j \right) + (15 + 21.21j)$$

$$Z = \frac{5010}{11} + 15.755j$$

$$I = \frac{V}{Z}$$

$$= \frac{250}{\frac{5010}{11} + 15.755j}$$

$$= 0.548 - 0.019j$$

$$1) f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$= \frac{1}{2\pi} \sqrt{\frac{1}{(125 \times 10^{-3}) \times 0.20264 \times 10^{-6}} - \frac{5^2}{125^2 \times 10^{-3}}}$$

$$= 1000.003 \text{ Hz}$$

$$2) X_L = 2\pi fL$$

$$= 2\pi (1000) (125 \times 10^{-3})$$

$$= 785.398 \Omega$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{5^2 + 785.398^2}$$

$$= 785.416 \Omega$$

$$I_{Lr} = \frac{V}{Z_L} = \frac{20}{785.416}$$

$$= 0.0255 \text{ A}$$

$$= 25.464 \text{ mA}$$

$$3) X_C = \frac{1}{2\pi fC}$$

$$= \frac{1}{2\pi (1000) (0.20264 \times 10^{-6})}$$

$$= 785.407 \Omega$$

$$I_C = \frac{V}{X_C} = \frac{20}{785.407}$$

$$= 0.0255 \text{ A}$$

$$= 25.464 \text{ mA}$$

(90°)

$$4) Z = \frac{L}{CR}$$

(Dgn imp)

$$= \frac{125 \times 10^{-3}}{0.20264 \times 10^{-6} \times 5}$$

$$= 123371.696 \Omega$$

$$= 123.371 k\Omega$$

$$5) \cancel{I_{LR}} \quad \theta = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{785.398}{5}$$

$$\theta = 89.635^\circ \quad \text{lagging}$$

$$\cancel{I_{LR} \cos 89.635}$$

$$= \cancel{25.466 \times 10^{-3} \cos 89.635}$$

$$= \cancel{162.216 \mu A}$$

$$I_T = \frac{V_T}{Z + R}$$

$$= \frac{20}{785.398 + 5}$$

$$= 0.0253 A$$

$$= 25.303 mA$$

$$6) \theta = \tan^{-1} \frac{X_L}{R}$$

$$= \tan^{-1} \frac{785.398}{5}$$

$$\theta = 89.635^\circ \text{ lagging}$$

$$I_{LR} \cos 89.635$$

(Horizontal comp)

$$= 25.464 \cos 89.635$$

$$= 162.216 \mu A$$

$$-I_{LR} \sin 89.635$$

(Vert. comp)

$$= -25.464 \sin 89.635$$

$$= -25.463 A$$


Vert comp of I_C

$$I_C \sin 90 = 25.464 \sin 90$$

$$= 25.464 A$$

$$\theta = \tan^{-1} \left(\frac{25.464}{25.463} \right)$$

$$= 45^\circ$$

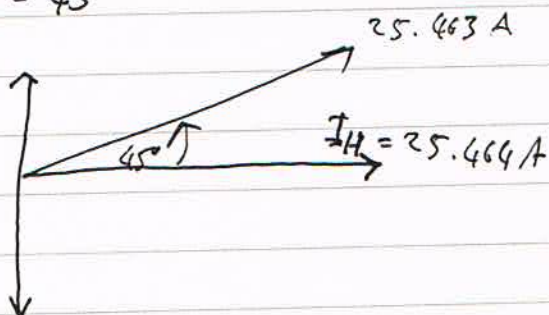

Q8

$$a) R_T = \frac{100 \times 120}{100 + 120} + 0$$
$$= 54.545 \Omega$$

$$P = \frac{V^2}{R}$$
$$= \frac{6^2}{54.545}$$

$$= 0.66 \text{ W}$$

$$b) R_T = \overset{100}{54.545} + 50$$
$$= 104.545$$

$$\therefore P = \frac{6^2}{104.545}$$

$$= 0.3443 \text{ W}$$

c) 0.3 ; conducts

d) positive

e) junction diode

f) 8.9 - 9.1 V


g) minimum ; R

h) V_R ; maximum

Q9

- d) Impedance is the combination of resistances in a RL, RC, or RLC circuit. It can also be said to be the ratio applied voltage to current.
- b) The Q-factor is the amount by which V_L and V_C are magnified. It gives an indication of how many times V_L or V_C is greater than V_T
- c) maximum; minimum
- d) ~~a series~~ both series & parallel
- e) acceptor
- f) rejector
- g) 1

Q10

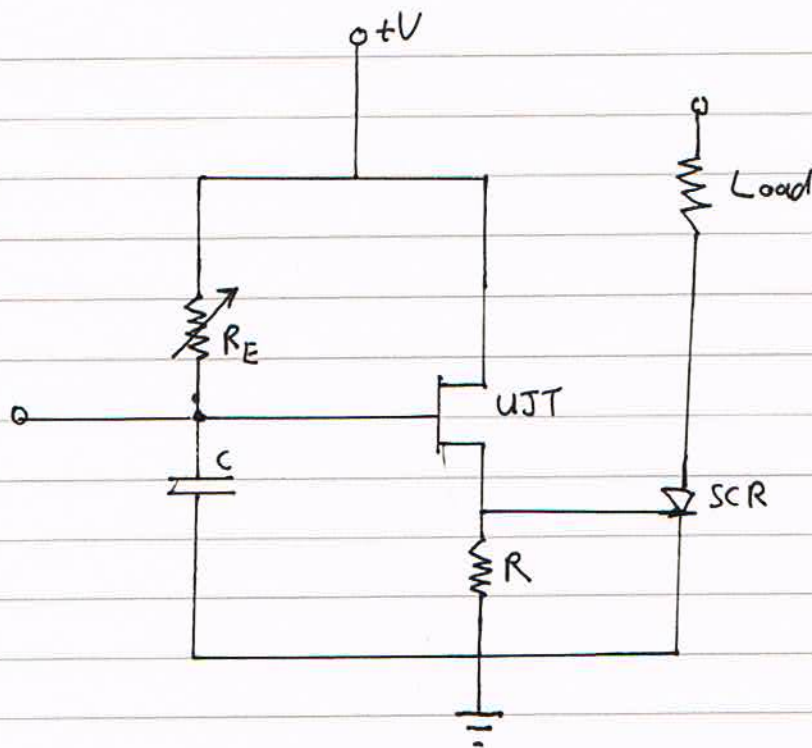

The resistor R_E is chosen so that the load line is determined by R_E passes through the device characteristic in the negative resistance region.

The capacitor determines the time interval between triggering pulses and the time duration of each pulse.

By varying R_E , the time constant $R_E C$ alters the point at which the UJT fires thus allowing the control of the conduction angle of the SCR, controlling the control of the load.