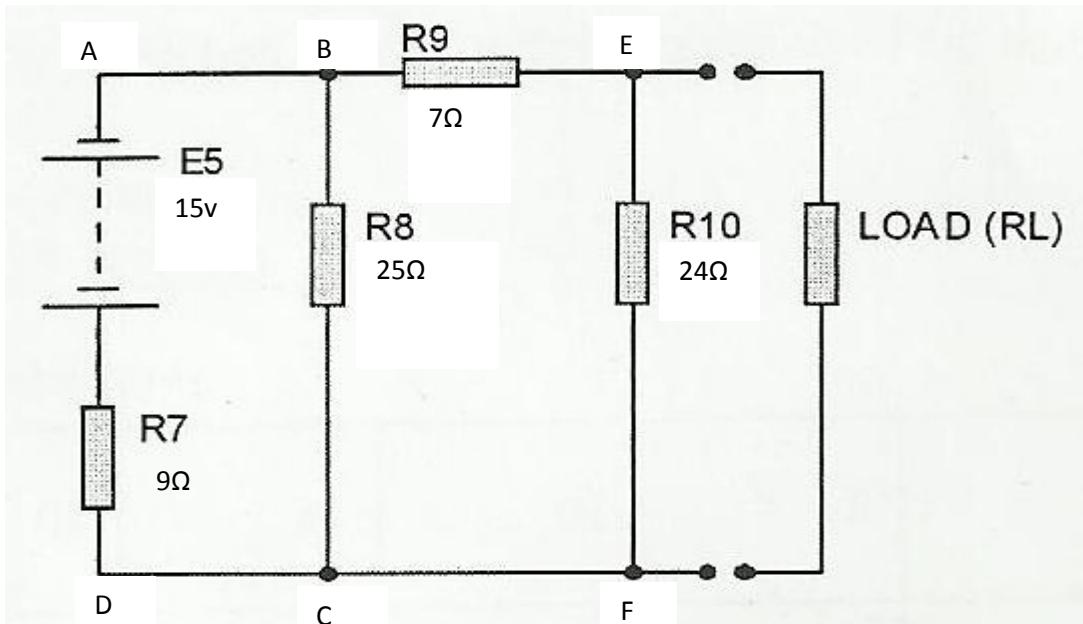


Task Two
Kirchoffs Law



Loop A B C D

$$15v = 9\Omega I_1 + 25\Omega (I_1 - I_2)$$

$$15v = 10\Omega I_1 + 25\Omega I_1 - 25\Omega I_2$$

$$15v = 34\Omega I_1 - 25\Omega I_2 \quad \text{--- (1)}$$

Loop B E F C

$$0v = 7\Omega I_2 + 25\Omega (I_2 - I_1) + 24\Omega I_2$$

$$0v = -25\Omega I_1 + 56\Omega I_2 \quad \text{--- (2)}$$

$$15v = 34\Omega I_1 - 25\Omega I_2 \quad \text{--- (1)} \times 25$$


$$0v = -25\Omega I_1 + 56\Omega I_2 \quad \text{--- (2)} \times 34$$

$$375v = 850\Omega I_1 - 625\Omega I_2$$

$$0v = -850\Omega I_1 + 1904\Omega I_2$$

$$375v = 1279\Omega I_2$$
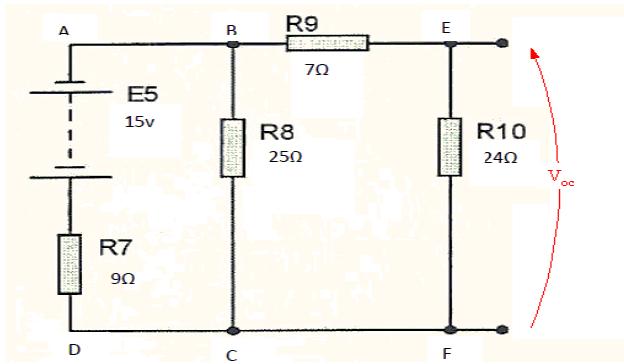
$$I_2 = \frac{375v}{1279\Omega} = 0.293a$$




$$V_o = 0.293a * 24\Omega I^2 = 7.032v$$

$$ISC = 25\Omega I_1 * 15v = 375v$$

$$25\Omega I_1 * 9\Omega I = 225\Omega$$

$$34\Omega I_1 * 7\Omega I_2 = 238\Omega$$

$$\frac{375v}{463\Omega} = 0.81a$$

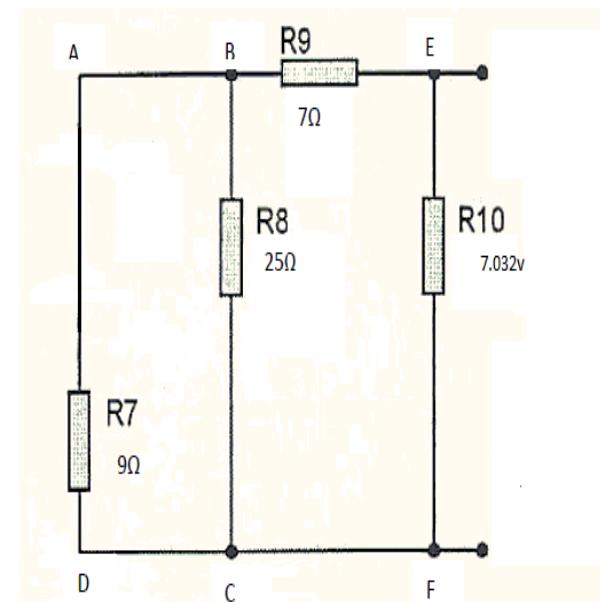

$$RL = \frac{V_o}{ISC} = \frac{7.032v}{0.81a} = 8.68\Omega$$