

ENGINEERING TEAM PROJECT

University Technology of PETRONAS


AUTOMATIC RETRACTABLE WIPER SYSTEM [ARWIS]

ELECTRICAL & ELECTRONIC PART

Prepared by: Luqman Radzuan


www.electroniccircuitbook.com

INTRODUCTION

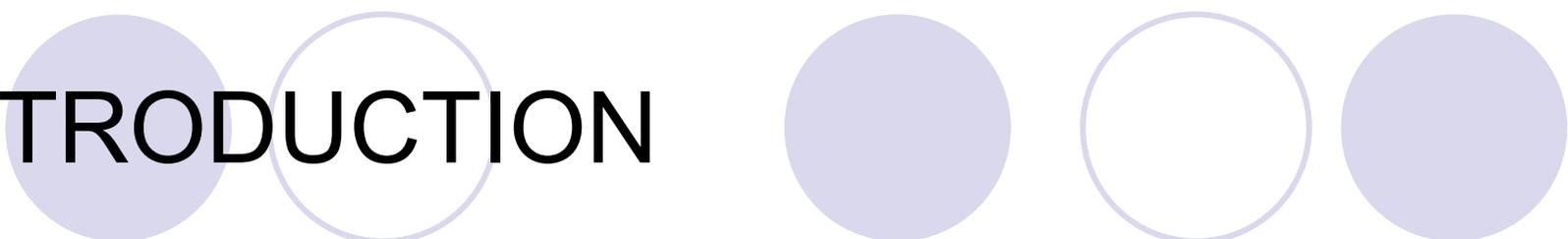


In this project we divide the electrical & electronic discussion into 2 parts.

1. Software
2. Hardware

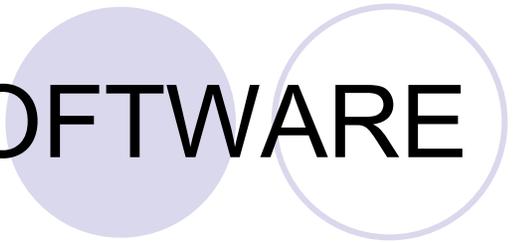


SOFTWARE

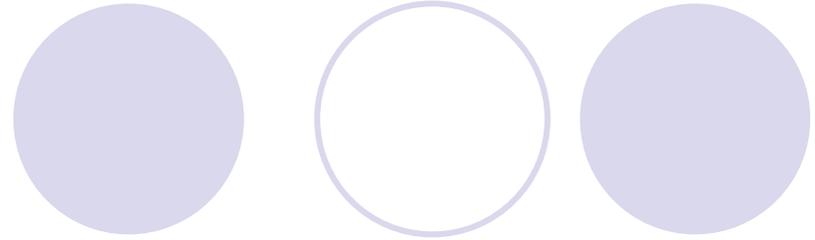- C language
- PCWH compiler
- UP00A programmer
- Flow Chart & Source Code
- Program description
- Calculation




C LANGUAGE

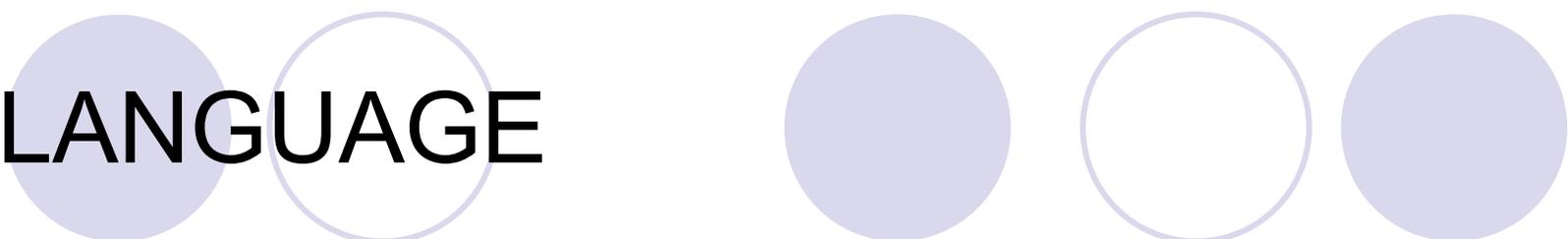

- It's a common programming language
- Easier to understand
- Require less time to program.

PCWH COMPILER

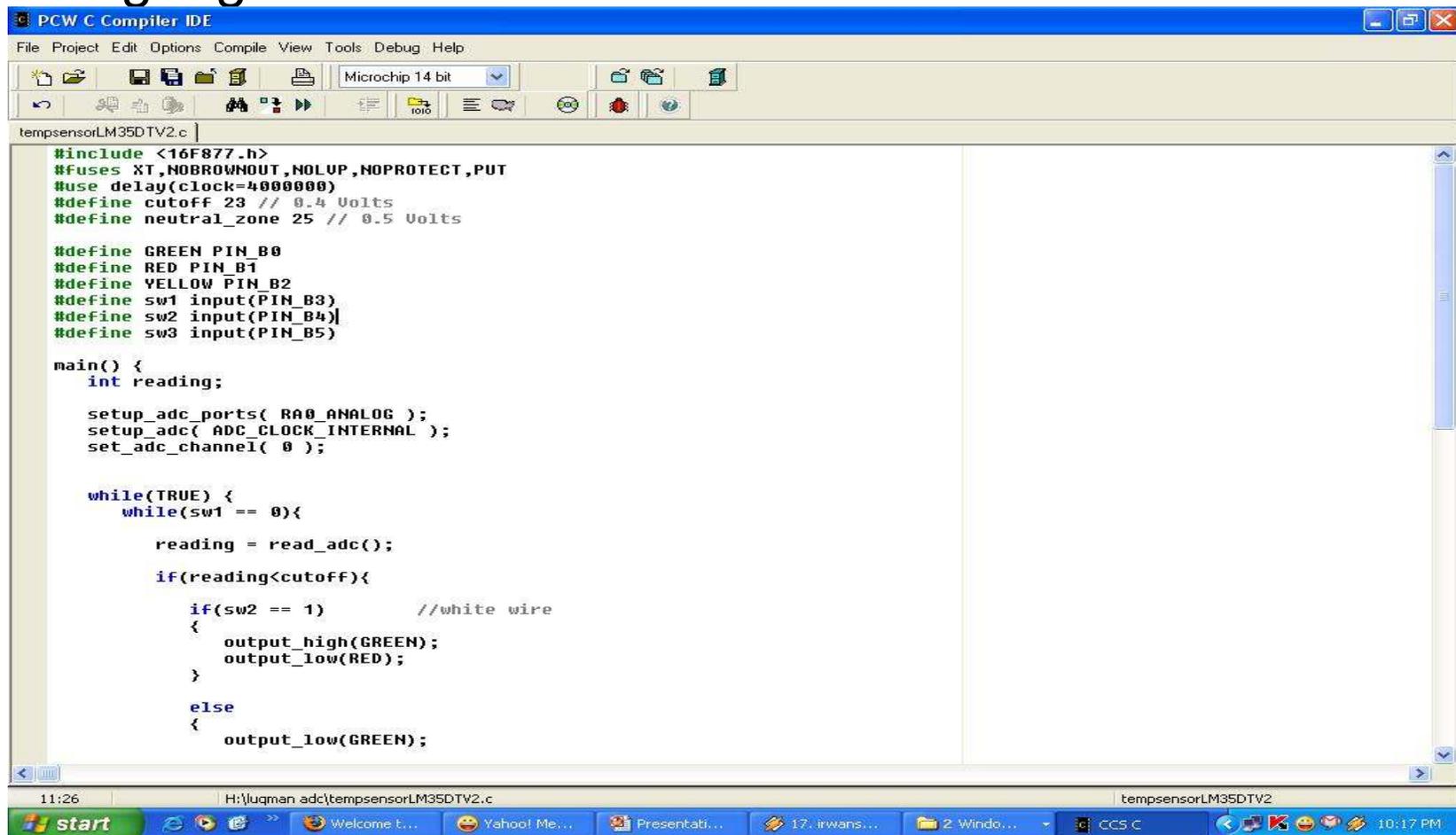- A program that compile C language to machine language.



The screenshot displays the PCWH C Compiler IDE interface. The window title is "PCWH C Compiler IDE". The menu bar includes "File", "Project", "Edit", "Options", "Compile", "View", "Tools", "Debug", and "Help". The toolbar contains various icons for file operations and compilation. The main editor area shows the source code for "tempensorLM35DTV2.c". The code includes headers, defines for hardware pins and switches, and a main function that reads an ADC value and controls LEDs based on the reading and switch states.

```
#include <16F877.h>
#fuses XT,NOBROWNOUT,NOLUP,NOPROTECT,PUT
#use delay(clock=4000000)
#define cutoff 23 // 0.4 Volts
#define neutral_zone 25 // 0.5 Volts

#define GREEN PIN_B0
#define RED PIN_B1
#define YELLOW PIN_B2
#define sw1 input(PIN_B3)
#define sw2 input(PIN_B4)
#define sw3 input(PIN_B5)

main() {
    int reading;

    setup_adc_ports( RA0_ANALOG );
    setup_adc( ADC_CLOCK_INTERNAL );
    set_adc_channel( 0 );


    while(TRUE) {
        while(sw1 == 0){
            reading = read_adc();
            if(reading<cutoff){
                if(sw2 == 1) //white wire
                {
                    output_high(GREEN);
                    output_low(RED);
                }
                else
                {
                    output_low(GREEN);
                }
            }
        }
    }
}
```

UP00A PROGRAMMER

- The programmer that is used to download the program onto the PIC16F877



FLOW CHART

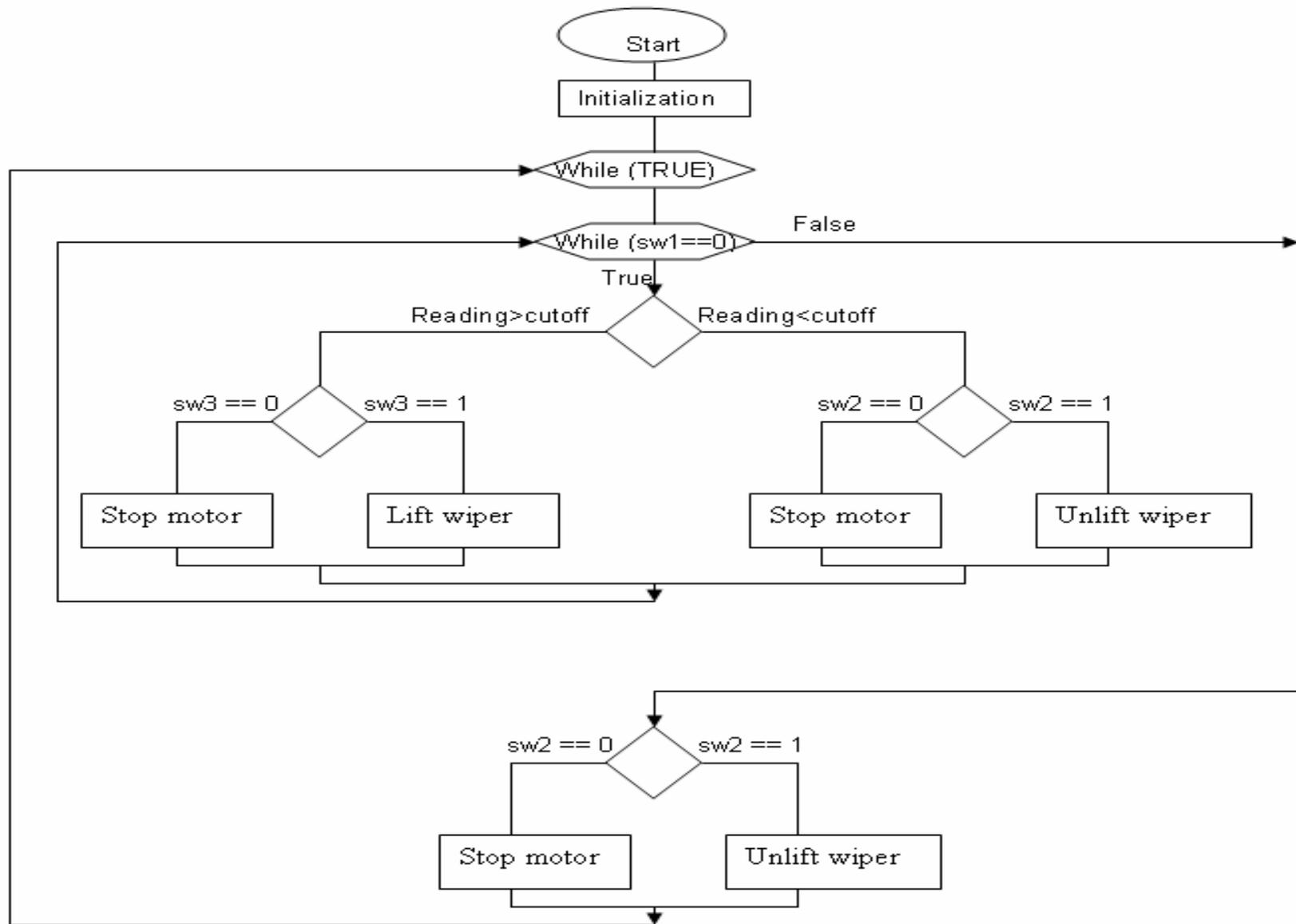

SOURCE CODE

```
#include <16F877.h>
#fuses XT:NOBROWNOUT,NOLVP,NOPROTECT,PUT
#use delay(clock=4000000)
#define cutoff 21 // 0.4 Volts

#define GREEN PIN_B0
#define RED PIN_B1
#define YELLOW PIN_B2
#define sw1 input(PIN_B3)
#define sw2 input(PIN_B4)
#define sw3 input(PIN_B5)

main() {
    int reading;
    setup_adc_ports( RA0_ANALOG );
    setup_adc( ADC_CLOCK_INTERNAL );
    set_adc_channel( 0 );

    while(TRUE) {
        while(sw1 == 0){

            reading = read_adc();

            if(reading<cutoff){

                if(sw2 == 1)    //white wire
                {
                    output_high(GREEN);
                    output_low(RED);
                }

                else
                {
                    output_low(GREEN);
                    output_low(RED);
                }
            }
        }
    }
}
```

```
else if(reading>cutoff){

    if(sw3 == 1)    //purple wire
    {
        output_high(RED);
        output_low(GREEN);
    }

    else
    {
        output_low(RED);
        output_low(GREEN);
    }

}

else {}

}

if(sw2 == 1)    //white wire
{
    output_high(GREEN);
    output_low(RED);
}

else
{
    output_low(GREEN);
    output_low(RED);
}

}

}
```

CALCULATION

- By default, the analog to digital converter is 8 bits. Thus, a range of 0 to 5 volts analog is represented by the numbers 0-255. The A/D reading can be converted to volts by the formula:

$$\text{Volts} = \text{Reading} * (5.0/255)$$

$$\text{Reading} = \text{Volts} * (255/5)$$

Voltage produce by temperature sensor at 40°C,

$$V_{ts} = 10\text{m} * 40$$

$$= 400\text{mV}$$

$$= 0.4\text{V}$$


$$\text{Reading} = 0.4 * (255/5)$$

$$= 20.4$$

$$= 21$$

- So in the programming we set 21 as the limit where the temperature sensor exceeds 40°C.


HARDWARE

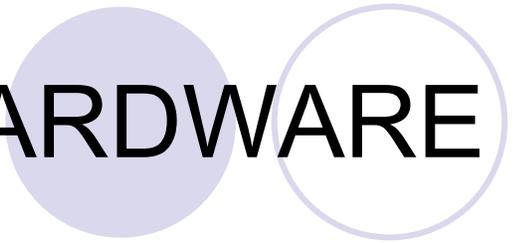

- Circuit Implementation


- Analog Circuit

- Digital Circuit

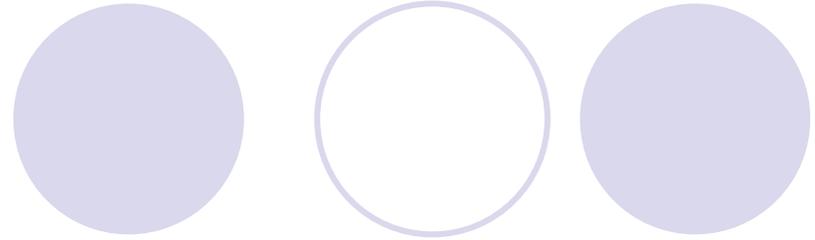



ANALOG CIRCUIT

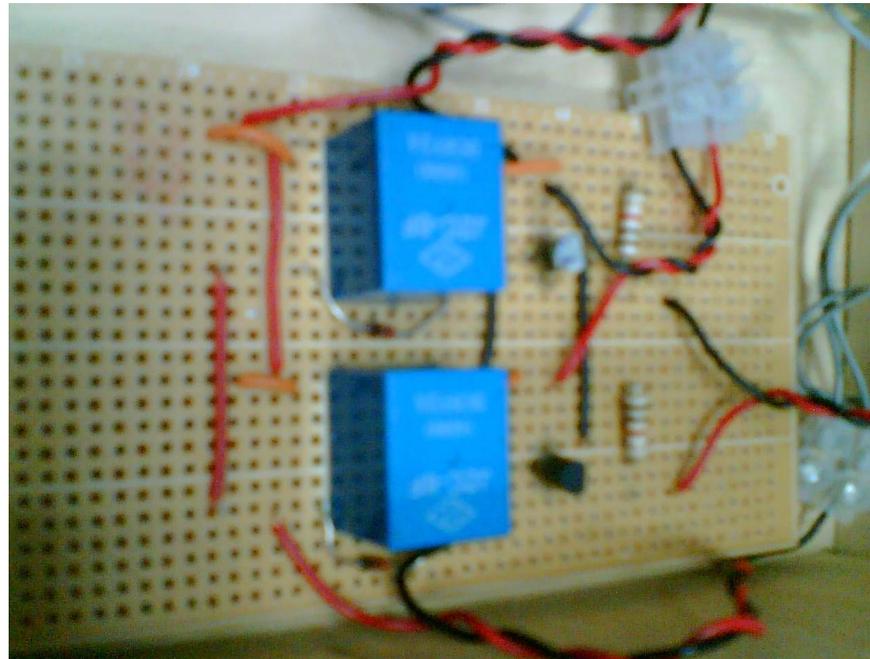- The function of this circuit is to interchange the terminal of the DC motor so that it can turn clockwise and counter-clockwise.
- We achieve the goal by using two relays.





ANALOG CIRCUIT SCHEMATIC

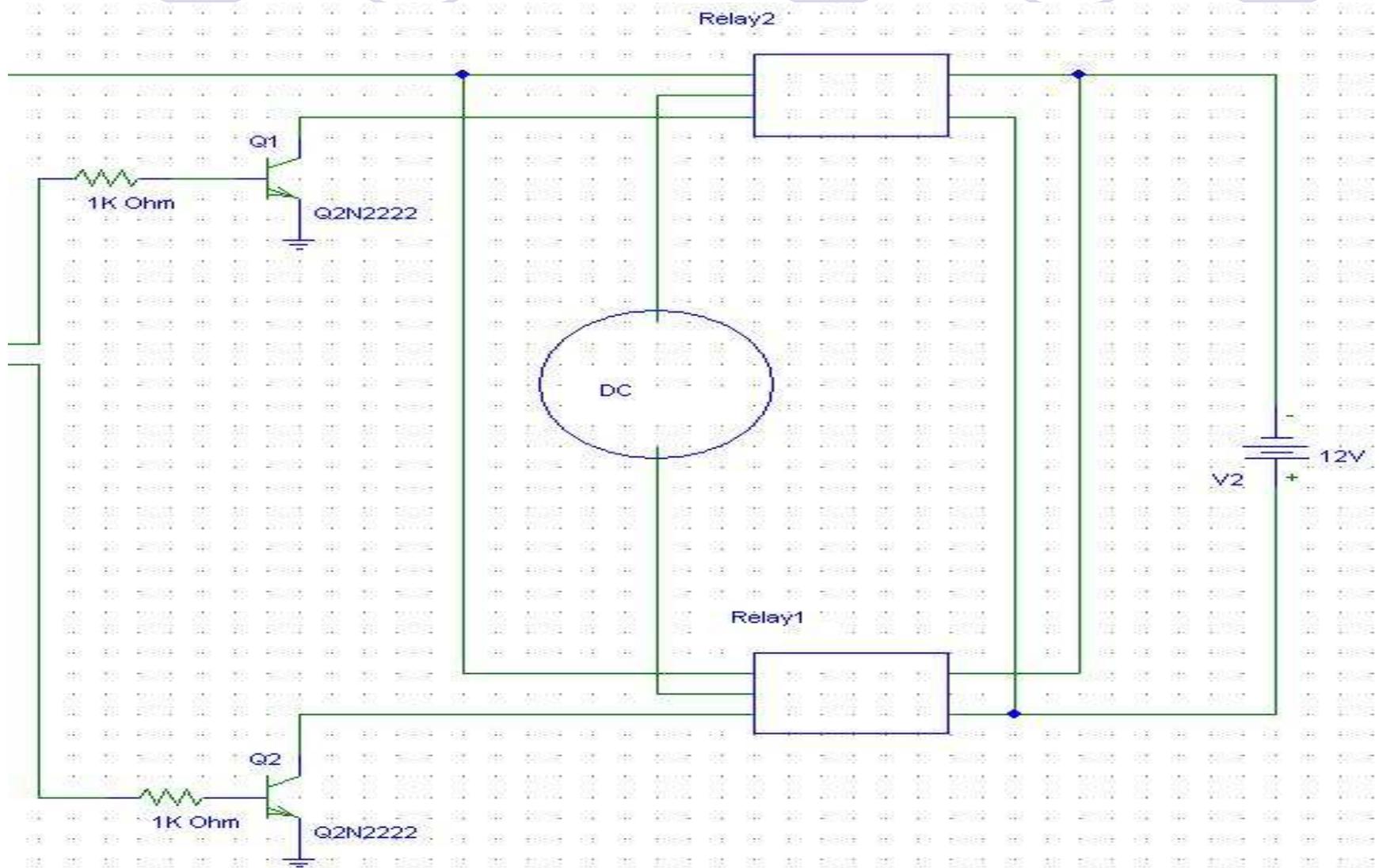

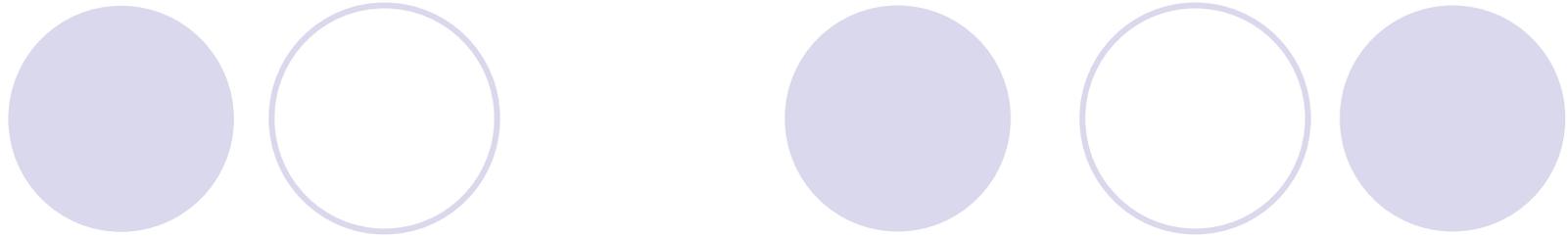


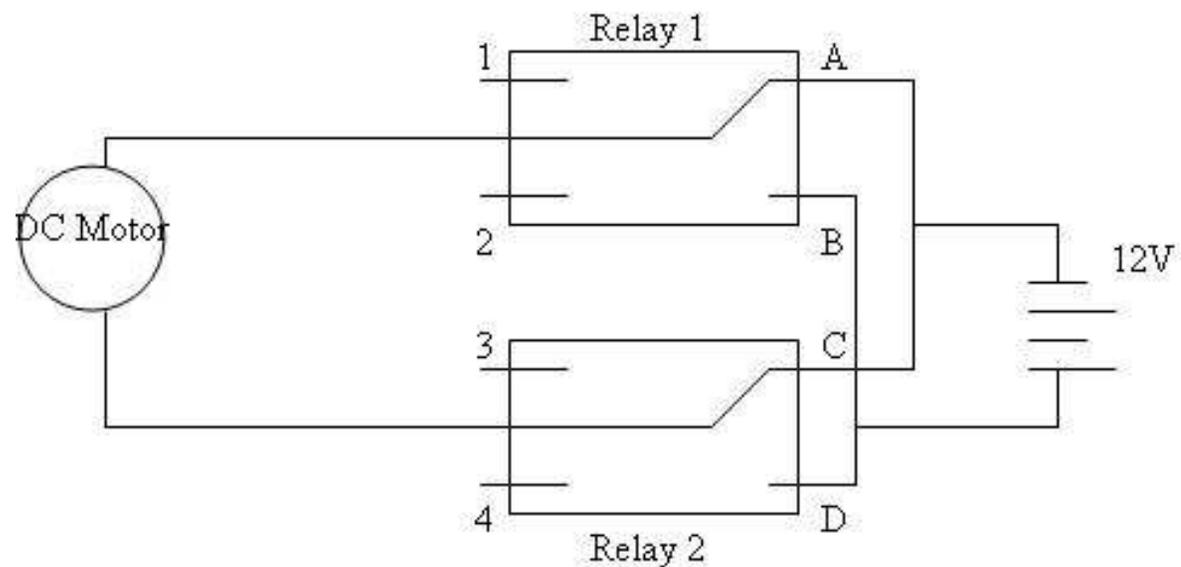
- Initially, both of the DC motor terminal are connected to the negative terminal of the 12V battery. Thus the motor will not turn.



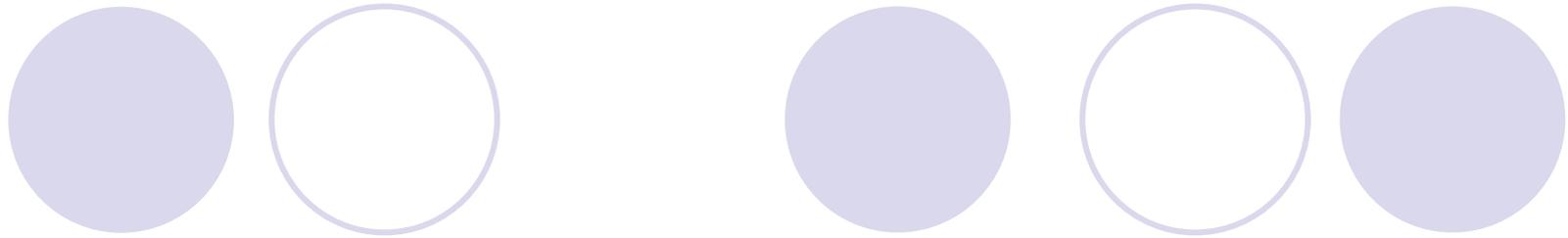


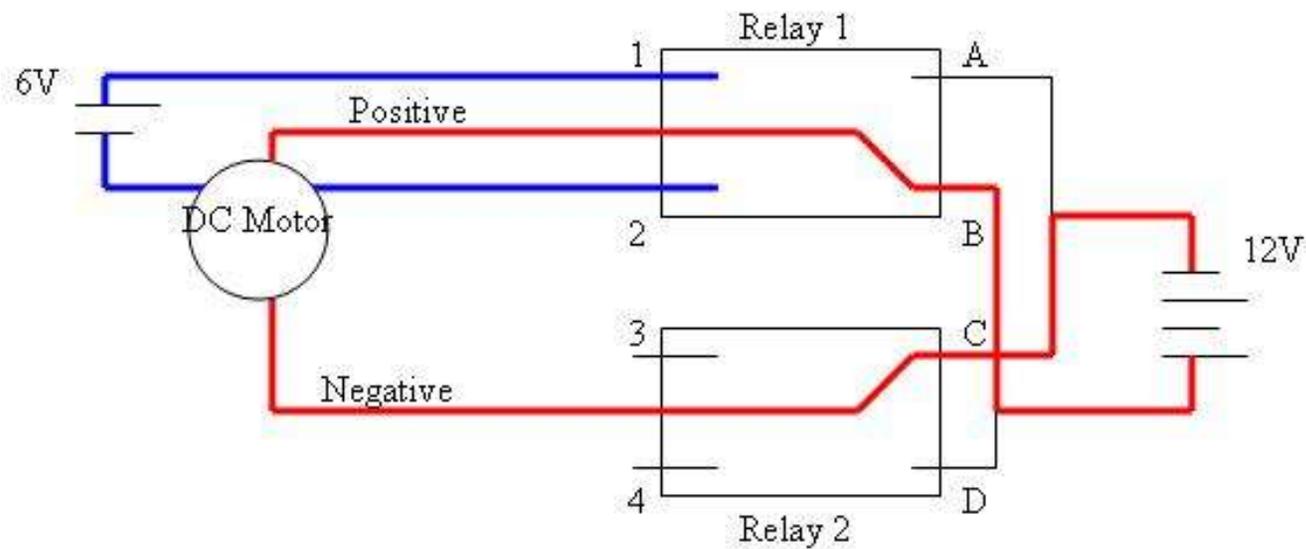- When relay1 is activated, the inner connection of relay1 change from A to B. This will complete the circuit.




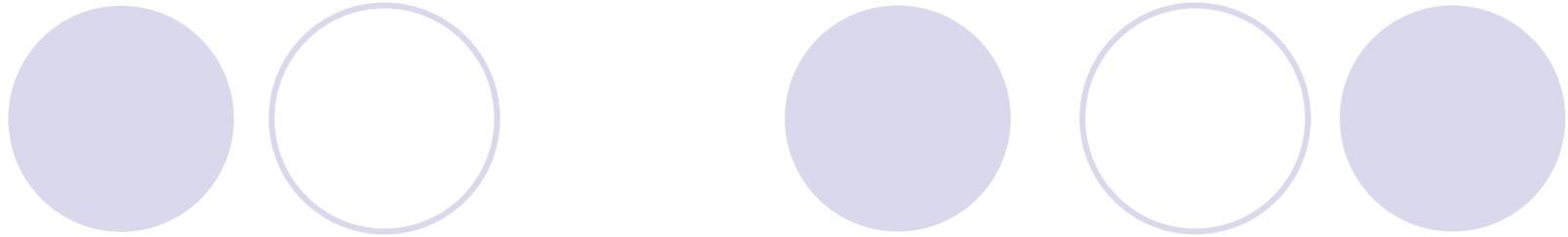

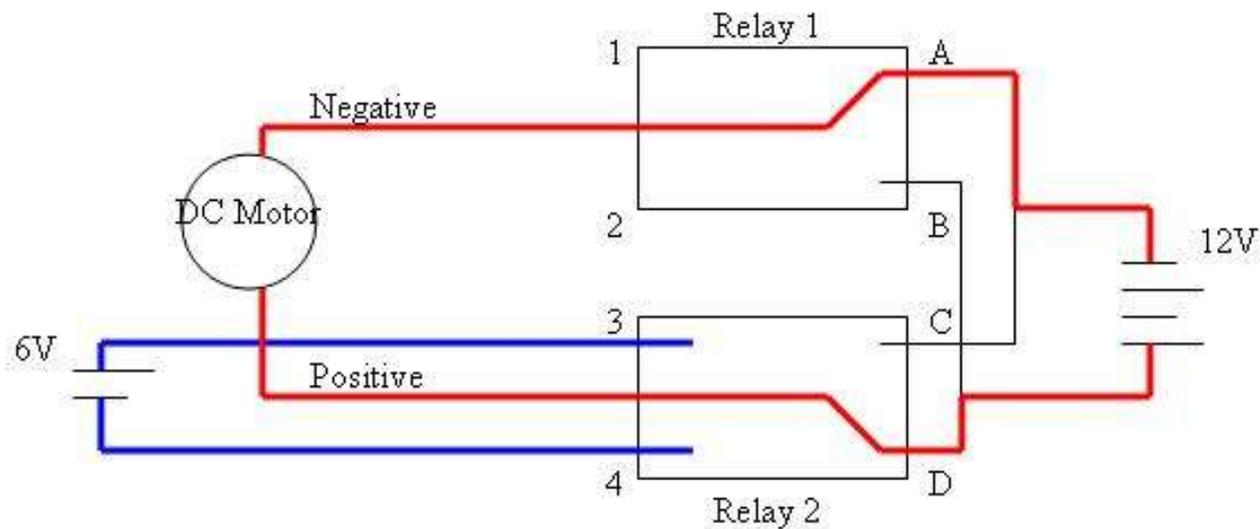- When relay2 is activated, the inner connection of relay2 change from C to D. This will complete the circuit.



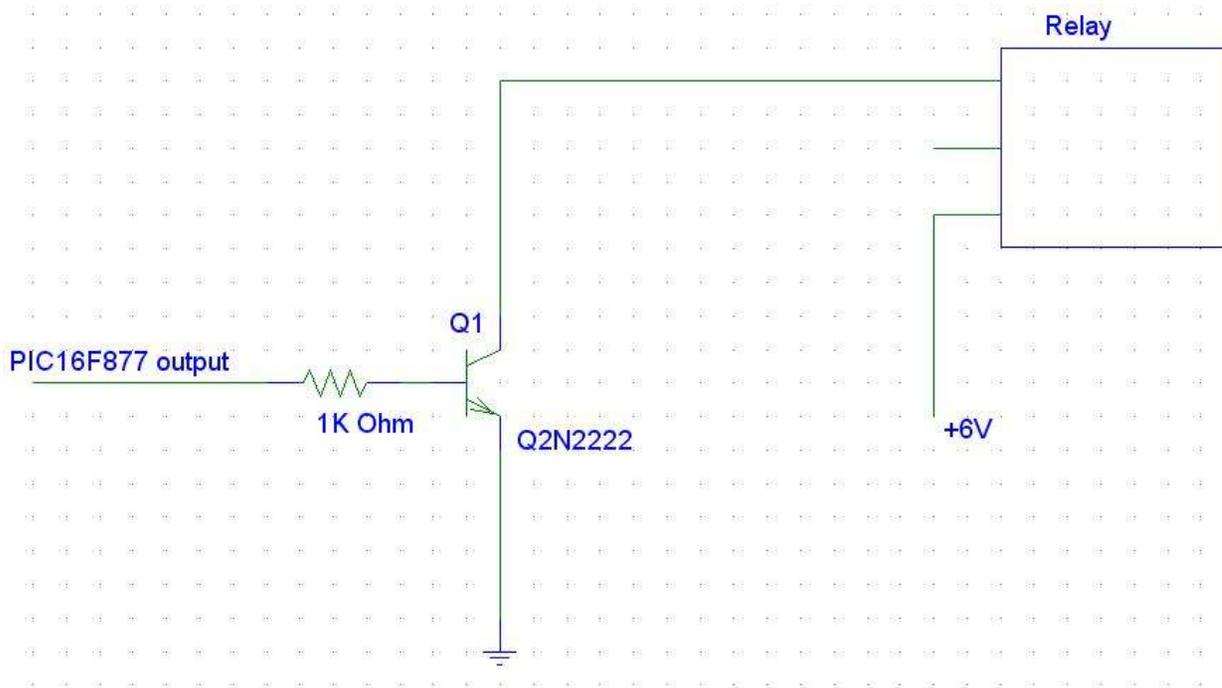
To activate the relay, we need to have at least 6V of supply. The output of the PIC16F877 only generates 4.6V. This is insufficient to trigger the relay. We solve the problem by using the 2N2222 BJT. As we all know, BJT can act as a switch.



From the diagram above, the current from collector(C) will be allowed to pass to emitter(E) only if there is current flowing in from base(B) which is from the PIC16F877. When the PIC16F877 output is HIGH, the current will flow from collector to emitter and complete the circuit. Thus the relay will be activated.

DIGITAL CIRCUIT

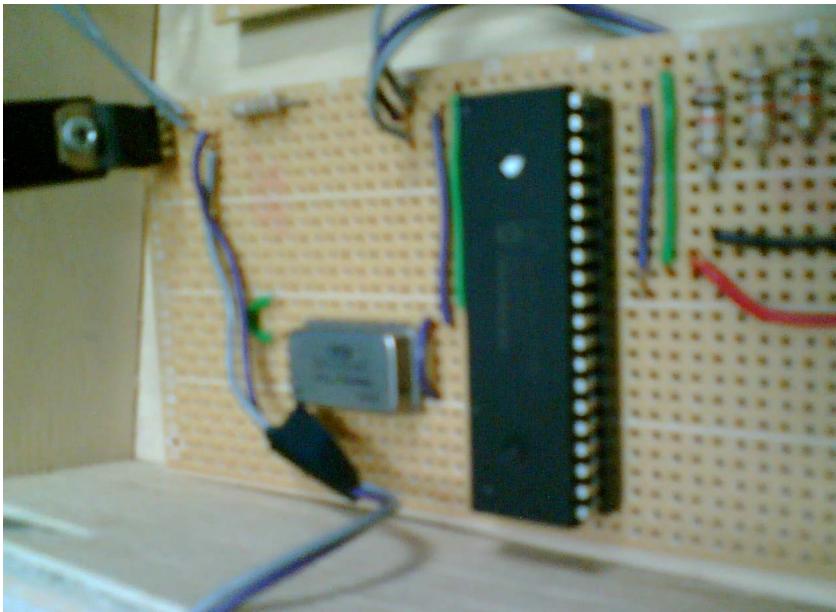- The function of this circuit is to control the DC motor based on the temperature changes.
- It consist of the PIC16F877,LM35DT(temperature sensor),4MHz oscillator,L7806CV(voltage regulator) and three 10K Ohm resistor.



MAIN CIRCUIT

