

- **Circuit Description**

- Assume:-

- 1. Motor is stationary,
- 2. Throttle is at minimum, ie. $V_r = -0.6$ Volt,
- 3. C1 is charged to +14 Volt.

Now advance the throttle until $V_r = 2.7$ Volt (for example).

- Y will switch from +14 V to -14 V since $V_r > X$.
- C1 will charge towards -14 V.
- When $V_1 = -8.9$ V the Op Amp output V_0 switches from -14 V to +14 V.

Diode D5 turns on and the power circuit applies +14 V to Motor.

- V_t thus goes from 0V to +14 V.
- So X goes from 0V to +9.5 V thus $X > V_r$, therefore Y goes high (+14 V).

C1 charges (via R5 & R6) towards +14 V.

- When $V_1 = +8.9$ V, V_0 goes low and this terminates the power pulse.
- V_t falls from +14 V to a potential determined by the motor EMF (which is proportional to its speed)


Since one pulse will not be sufficient to accelerate the motor to the required speed, X will be less than V_r .

- Therefore, Y goes low and C1 discharges via D4 & R5.
This cycle repeats until the motor has reached the desired speed.

- When the power pulse terminates, X will not fall below V_r so Y will remain high until the motor EMF decays to the point where $X < V_r$.
- C1 is charged towards -14 V.

- When V_1 reaches -8.9 V, V_0 goes high and starts another power pulse.
- The motor speed will thus oscillate around the required value.

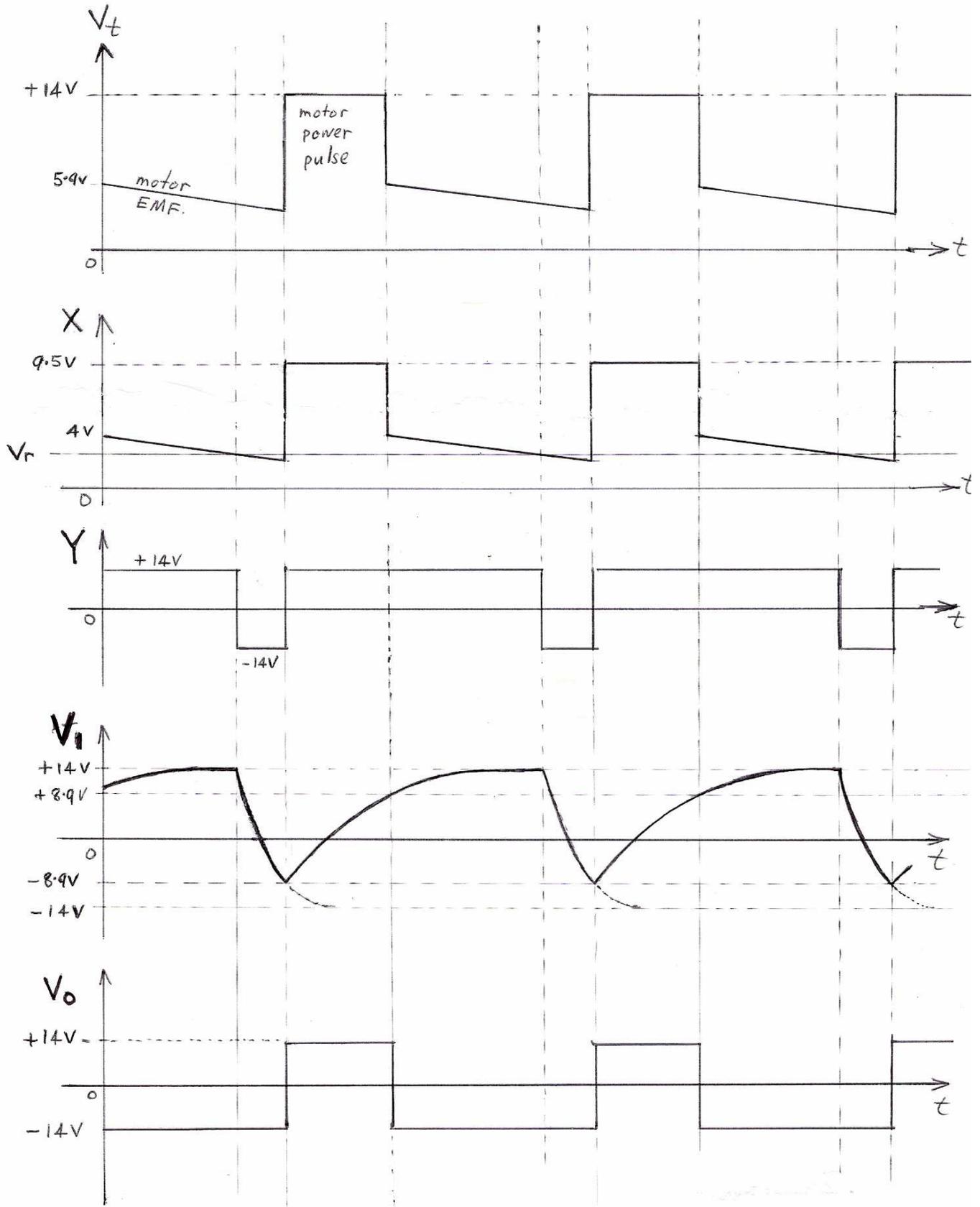If the throttle is advanced until $V_r > 10.5$ V, then X can never reach V_r . Thus continuous power is applied to the motor.



Steady State Waveforms.