

The figure below shows a source, amplifier, and load. The source resistance is 0.

- Find the parameters of a single transconductance amplifier that is equivalent to the amplifier shown. Draw the equivalent transconductance amplifier. Clearly label all parameters and show their values.
- Find the current gain i_o/i_{in} .

