

Design a structure of the circuit controlling the work of the  $G_1$  and  $G_2$  heaters via the  $W_1$ ,  $W_2$ , and  $W_3$  switches in dependence on temperature  $T$ :

- when  $T \geq T_a$  –  $G_1$  and  $G_2$  turned off
- when  $T_b \leq T < T_a$  –  $G_1$  and  $G_2$  connected in series and turned on
- when  $T_c \leq T < T_b$  – only  $G_2$  turned on
- when  $T_d \leq T < T_c$  – only  $G_1$  turned on
- when  $T < T_d$  –  $G_1$  and  $G_2$  connected in parallel and turned on

