

# Pulse width to logic


Note Title

$$\underline{T_{low}} < T_o < T_{high}$$


Pulses

One shot output

D-flip flop output

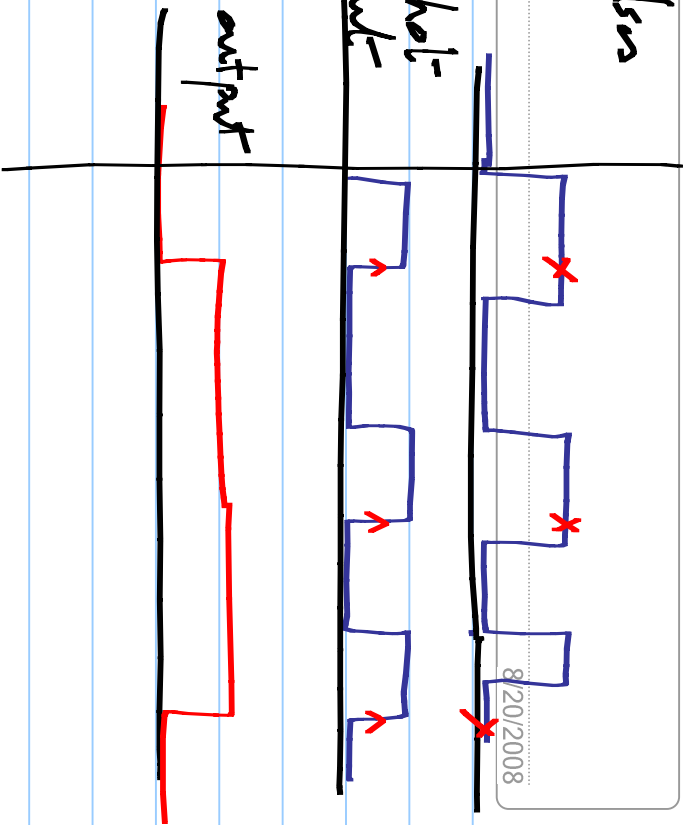


8/20/2008

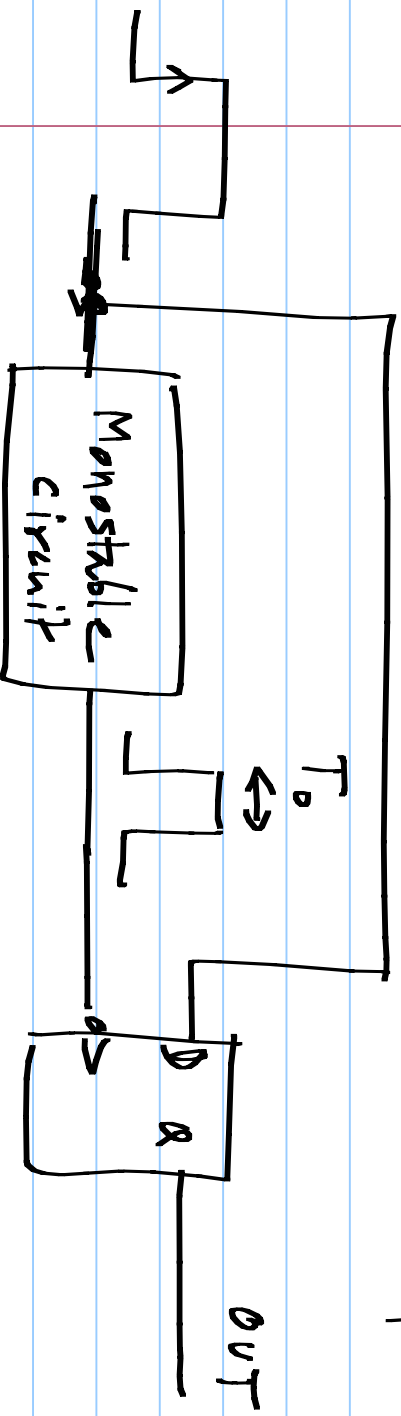

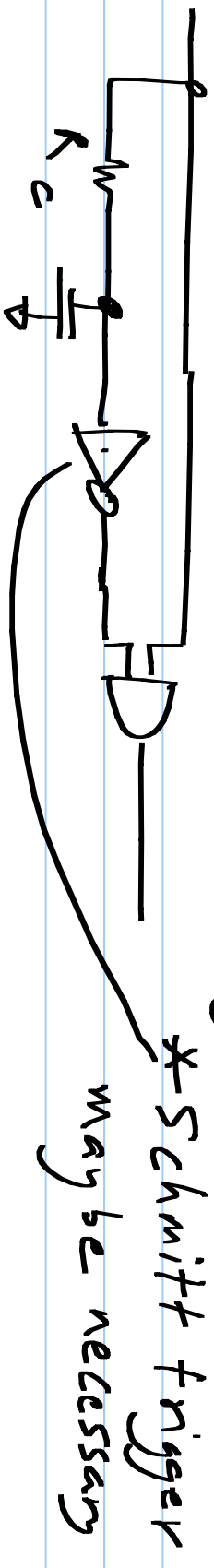
## Principle:

- \* On the rising edge of the input pulse, trigger a one-shot of width  $T_0$ .
  - \* On the falling edge of the one shot output, latch the input. This will be zero if the i/p lasts less than  $T_0$  & one otherwise
-

One shot implementation: \* Adjust  $R_C$  to get the right  $T_o$ .



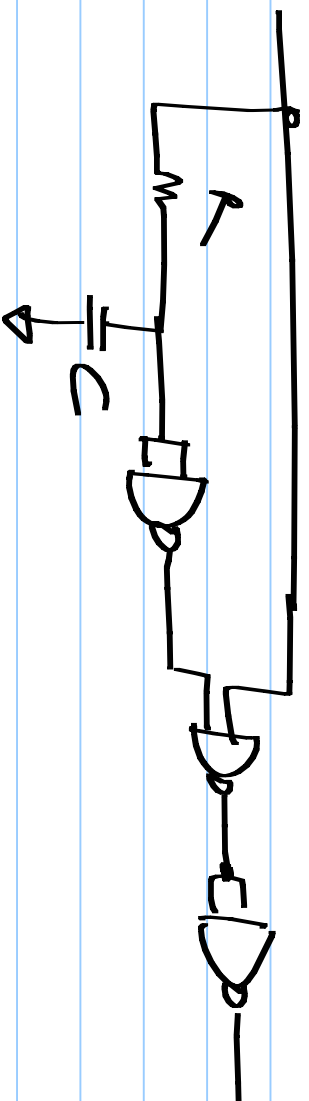Without schmitt trigger: Single NAND IC will do.



Two ICs in total: 1 NAND & 1 Flip flop.
<u>CMS ICs for low power</u>