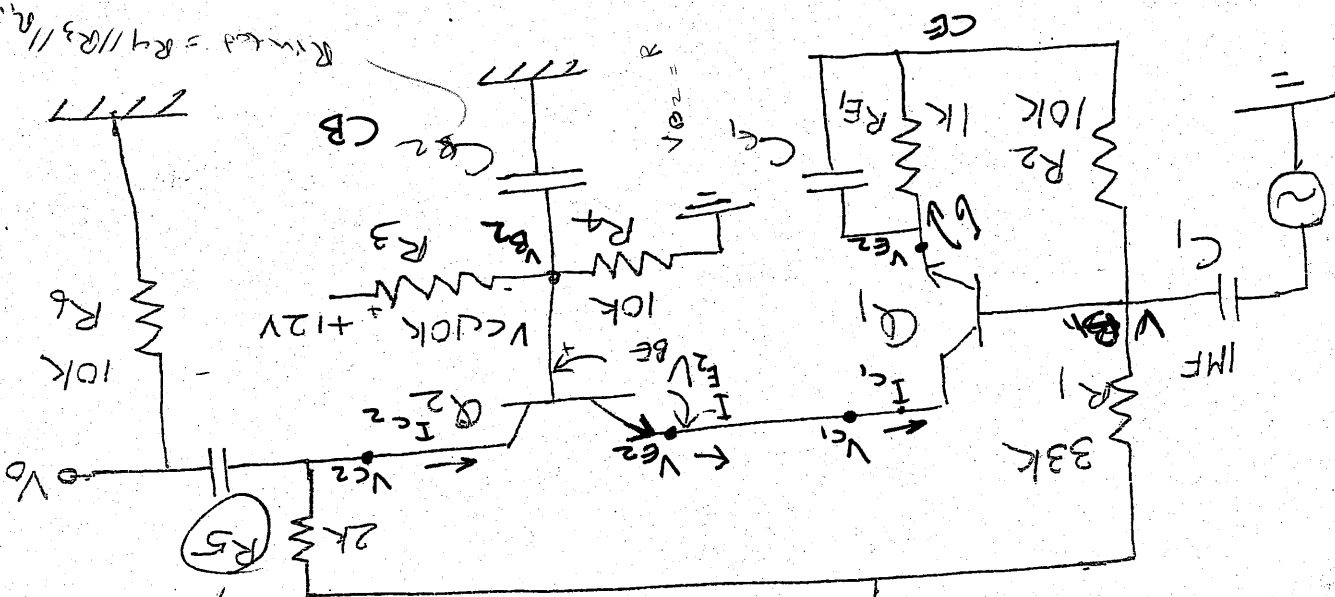


Problem

22



For the above cascode amplifier (CE stage) followed by a CB stage), Determine

(v) $\overline{c_1}, \overline{c_2}, \overline{c_3}, \overline{c_4}$

(v) Overall voltage gain

Frequency off (vvr)

Take $B = 100$

50.47795

(v)

Step 1 find I_{C1} and I_{C2}

$$V_{B1} = \frac{12 \times R_2}{R_1 + R_2} = \frac{12 \times 10k}{10k + 33k}$$

$$V_{E1} = V_{B1} - V_{BE1} = 2.8 - 0.7 = 2.1V$$

$$I_c \approx I_E = V_{E1} \frac{R_{E1}}{2.1 \text{ k}} = \frac{2.1 \text{ V}}{2.1 \text{ mA}}$$

Since emitter of Q_1 is in series with collector of Q_2 , $I_{E1} = I_{C2} = 2.1 \text{ mA}$

$$I_{C2} \approx I_{C1} = 2.0 \text{ mA}$$

step 2 Find V_{C1} & V_{C2}


$$V_{B2} = \frac{12 \times R_4}{R_4 + R_3} = \frac{12 \times 10k}{10k + 10k} = 6V$$

$$V_{C1} = V_{E2} = V_{B2} - 0.7 = 6 - 0.7 = 5.3V$$

$$V_{C2} = V_{CC} - I_{C2} R_5 = 12 - 2.1 \times 10^{-3} \times 2 \times 10^3 = 7.8V$$

(A) To find overall voltage gain, find individual voltage gain and then multiply.

step 1 Draw the AC equivalent circuit

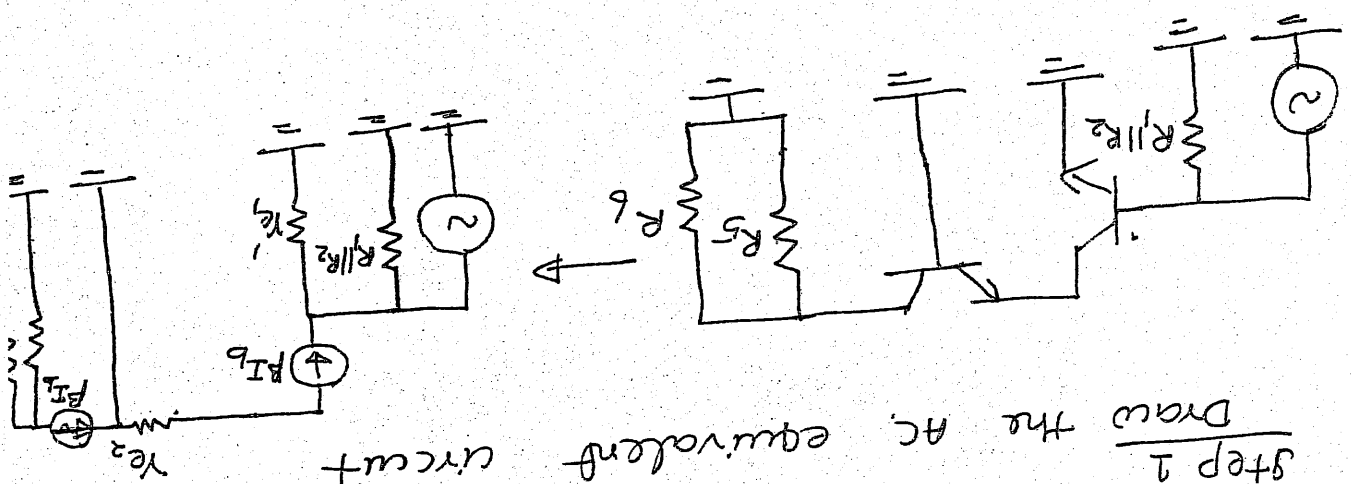

$$A_{V1} = \frac{-R_{L1}'}{r_{e1}} \quad \text{--- (1)}$$

$R_{L1}' = \text{Total collector load resistance of } Q_1 = r_{e2}'$

Since $I_{E1} = I_{E2}$, $r_{e1}' = r_{e2}' = \frac{25mV}{2.1mA} = 12\Omega$

Substituting r_{e1}' and r_{e2}' in (1)

$$A_{V1} = \frac{-R_{L1}'}{r_{e1}'} = \frac{-12\Omega}{12\Omega} = -1$$

2/5

X

$$\therefore f_{CL} = \frac{1}{2\pi \times 10^{-4} \times 10^3 \times 10^{-6}} = 649.5$$

$$= 1.04k$$

$$= 100k \parallel 7.67k \parallel 1200$$

$$= (33k \parallel 10k) \parallel (100 \times 12)$$


$$R_{in(stage)} = (R_1 \parallel R_2) \parallel \beta r_{e1}$$

(44) Lower cut off frequency $f_{CL} = \frac{1}{2\pi R_{in} C_1}$

overall gain $= A_{V1} \times A_{V2} = -1 \times 138 = -138$

$$A_{V2} = \frac{R_{L2}}{R_{L2} + r_{e2}} = \frac{R_5 \parallel R_6}{R_5 \parallel R_6 + r_{e2}} = \frac{2k \parallel 10k}{2k \parallel 10k + 1.66 \times 10^{-3}} = \frac{12}{12.166} = 138$$

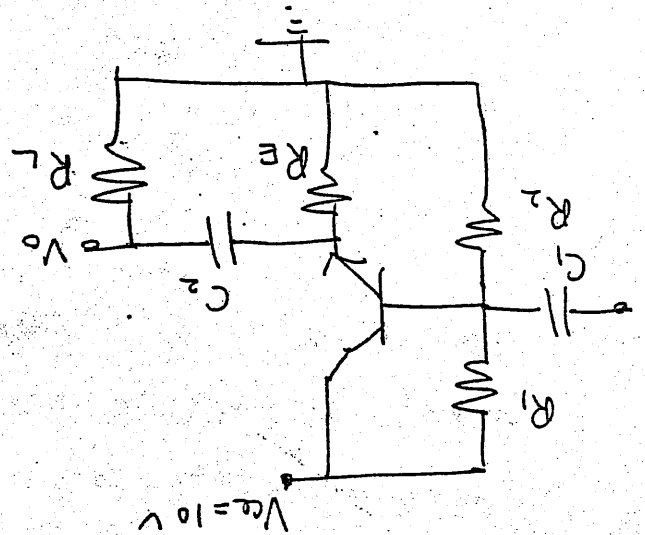31.
Design a c.c amplifier with $V_{CC} = 10V$.
Determine its current gain and input-impedance. Given $\beta = 175$, $R_C = 25k$.



$$\begin{aligned}
 V_{CC} &= 10V \\
 \text{Take } I_C &= 2mA \\
 V_{CE} &= 50\% \text{ of } V_{CC} = 5V \\
 V_{RE} &= V_{CC} - V_{CE} = 5V \\
 \therefore R_E &= \frac{V_{RE}}{I_E} = \frac{5}{2} = 2.5k \\
 I_B &= \frac{I_C}{\beta} = \frac{2mA}{175} = 0.0114mA \\
 \therefore R_B &= \frac{V_{CC}}{I_B} = \frac{10}{0.0114mA} = 868.42k
 \end{aligned}$$

$$\begin{aligned}
 \text{Take } I_{R1} \approx I_{R2} &= 10I_B = 0.114mA \\
 V_B = V_{R2} &= V_{RE} + V_{BE} = 5 + 0.7 = 5.7V \\
 \therefore R_2 &= \frac{V_{R2}}{I_{R2}} = \frac{5.7}{0.114mA} = 50k \\
 R_1 &= \frac{V_{R1}}{I_{R1}} = \frac{V_{CC} - V_{R2}}{I_{R1}} = \frac{10 - 5.7}{0.114} = 38k \\
 \therefore R_1 &= 38k
 \end{aligned}$$

$$\begin{aligned}
 R'_L &= R_C \parallel R_L = 2.5k \parallel 25k = 1.25k \\
 R_{in}(\text{base}) &= \beta (r_e' + R'_L) = 175(12.5 + 1.25k) = 219k \\
 R_{in} &= R_1 \parallel R_2 \parallel R_{in}(\text{base}) = 38k \parallel 50k \parallel 219k = 19.6k \\
 \therefore R_{in} &= 19.6k
 \end{aligned}$$


$$\begin{aligned}
 I_E &= \frac{V_E}{R'_E} = \frac{A_v \cdot V_{in}}{R'_E} = \frac{0.99 \cdot V_{in}}{1.25k} = 0.05 \times 10^{-3} V_{in} \\
 \therefore I_E &= 0.05 \times 10^{-3} V_{in}
 \end{aligned}$$

$$\begin{aligned}
 I_{in} &= \frac{V_{in}}{R_{in}} = \frac{V_{in}}{19.6k} = 0.05 \times 10^{-3} V_{in} \\
 A_v &= \frac{I_E}{I_{in}} = \frac{0.05 \times 10^{-3} V_{in}}{0.05 \times 10^{-3} V_{in}} = 1
 \end{aligned}$$

Figure shows an amplifier consisting of a C-E stage driving an emitter follower stage. The transistors have the following parameters.

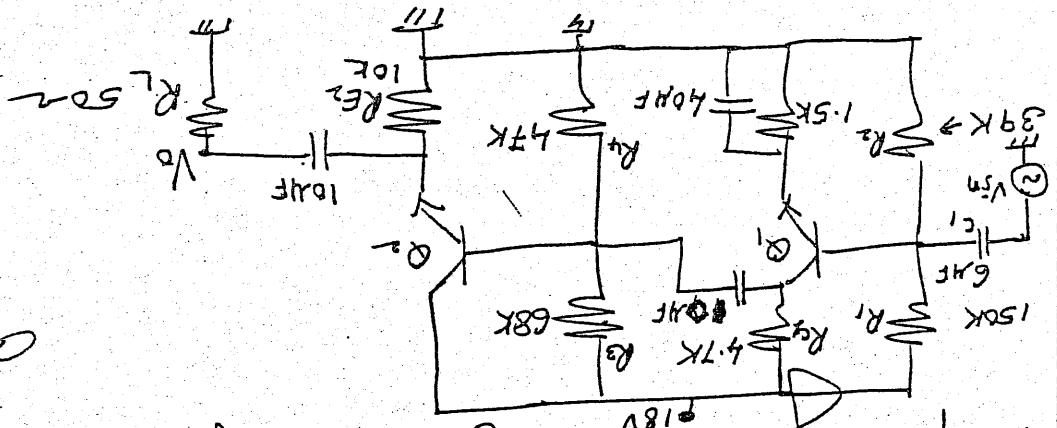Q1 $\rightarrow r_{e1} = 15\Omega$ $\beta_1 = 180$
 Q2 $\rightarrow r_{e2} = 40\Omega$ $\beta_2 = 100$

Find the voltage gain and the approximate value of the lower cut-off frequency. Coupled by the capacitor C1.



a.c eqn at

$R_{in1} = R_1 \parallel R_2 \parallel \beta_1 r_{e1} = 150k \parallel 39k \parallel (180 \times 15) = 2.48k\Omega$
 Load of stage 1 $= R_{L1}' = R_{C1} \parallel R_{in2} = 4.7k \parallel R_{in2}$
 $R_{in2} = R_2 \parallel R_3 \parallel \beta_2 (r_{e2} + R_{L2})$
 $R_{L2}' = R_{E2} \parallel R_L$
 $= 10k \parallel 50 = 50\Omega$
 $= 68k \parallel 4.7k \parallel 100(40 + 50)$
 $= 6.8k$
 $\therefore R_{L1}' = 4.7k \parallel 6.8k = 2.8k$

Capacitor open in DC

out	C	CE	CB
-----	---	----	----

For Resistors use DC Anal.
 Capacitors AC.