



AGC is a circuit that provides a relatively constant V_{out} over a range of input voltages. It accomplishes this by supplying both positive and negative feedback simultaneously. The positive feedback, however, depends greatly on the equivalent resistance between the drain to source of Q2. This r_{ds} varies as the output voltage varies. This essentially creates a voltage divider on the positive op amp input, as shown below.