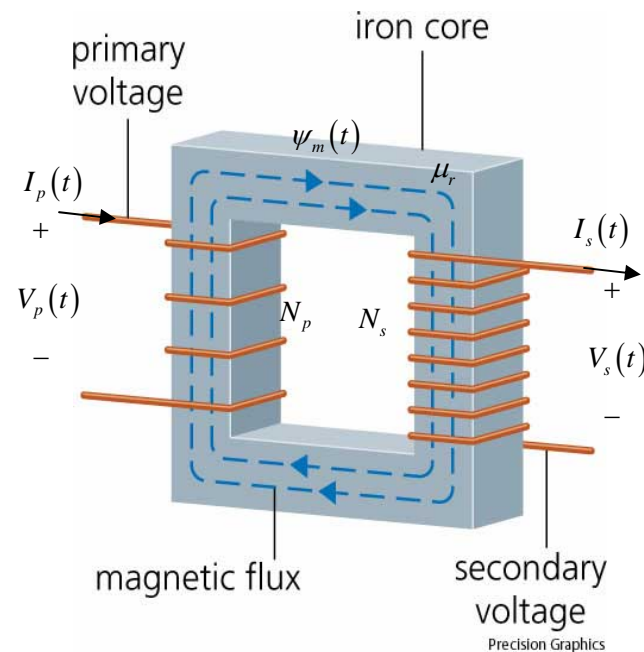


Transformers & Tuned Transformers

Transformers

- A transformer is an N -port device that transforms voltages, currents and impedances
 - Magnetically coupled
 - DC block (high-pass)
 - Parallel inductance (tuned-transformer)
- 2-port transformer:



$I_p(t)$ = Primary winding current
 $V_p(t)$ = Primary winding voltage (emf)
 N_p = # of turns on the primary winding
 μ_r = relative permeability of the core

$I_s(t)$ = Secondary winding current
 $V_s(t)$ = Secondary winding voltage
 N_s = # turns on the secondary winding
 $\psi_m(t)$ = magnetic flux in the core

Transformers & Tuned Transformers

Magnetic Flux

- Total flux flowing through core:

$$\begin{aligned}\psi_m(t) &= \iint_S \vec{B}(t) \cdot d\vec{s} = \iint_S [\vec{B}_p(t) + \vec{B}_s(t)] \cdot d\vec{s} \\ &= \psi_{m,p}(t) + \psi_{m,s}(t)\end{aligned}$$

- Flux is produced by the currents flowing through the windings
- Predicted by Ampere's law:


$$\psi_{m,j}(t) = N_j A_\ell I_j(t)$$

N_j = # of turns on the j -th winding,

$I_j(t)$ = current on the j -th winding,

A_ℓ = core constant (H/turn²)

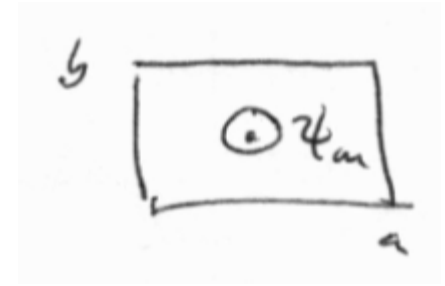- The core constant is a function of the core permeability, the cross-sectional area, and the axial length.
 - Typically provided by the manufacturer
 - See Table D.2 of the text
- The core constant can be frequency dependent
 - Look for the rated frequency in the specs



Transformers & Tuned Transformers


Faraday's Law:

- Faraday's law:

$$\oint_C \vec{E} \cdot d\vec{\ell} = -\frac{\partial}{\partial t} \iint_S \vec{B} \cdot d\vec{s}$$

$$emf = -N \frac{\partial}{\partial t} \psi_m$$

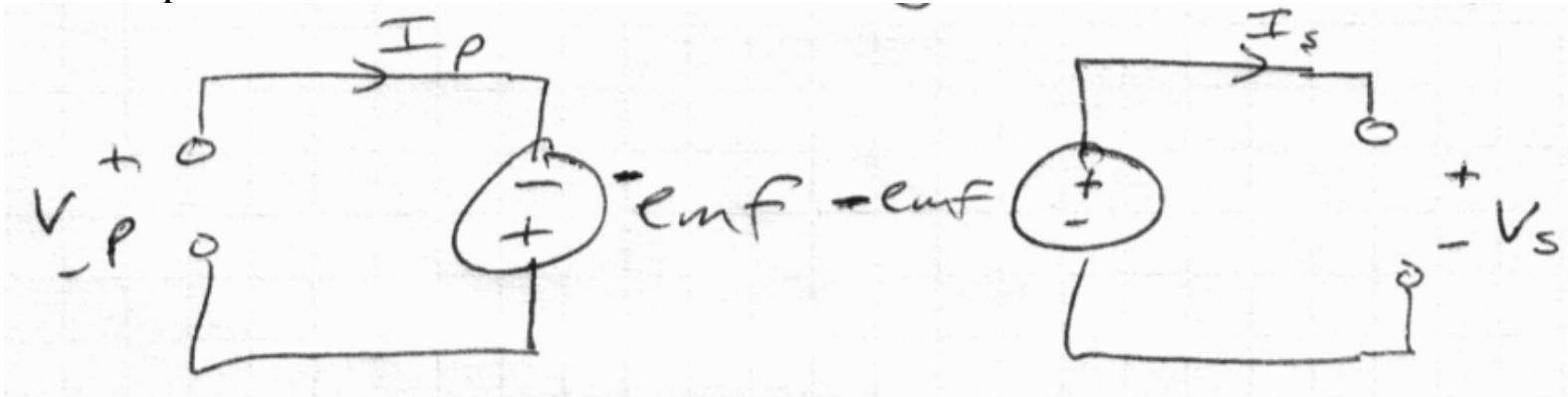- The emf (“electro-motive force”) is the “net push” felt by a charge on the contour C
 - An electrical potential energy
- The factor of N is because the flux is linking through N turns of the coil. Each turn experiences an emf of $\partial \psi_m / \partial t$.
- The emf is a measurable voltage
 - Equivalent circuit:



Transformers & Tuned Transformers

Sinusoidal Steady State Voltage

- Port voltages:

$$V_p = -\text{emf}_p = j\omega N_p \psi_m$$

$$V_s = -\text{emf}_s = j\omega N_s \psi_m$$

- Evaluating the quotient of these two equations:

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

- Turns Ratio:

$$V_p = \frac{N_p}{N_s} V_s; \quad \frac{N_p}{N_s} = \text{turns ratio}$$

- Observations:

If $N_s > N_p$, then $V_s > V_p \Rightarrow$ "Step up transformer"

If $N_s < N_p$, then $V_s < V_p \Rightarrow$ "Step down transformer"

Transformers & Tuned Transformers

Transformer Currents

- Assume that the primary is driven by a voltage source (with internal resistance), and the secondary is terminated with a load.
- Recall:

$$\psi_m = \psi_{m,p} + \psi_{m,s}$$

- $\psi_{m,s}$ will be negative since the current is flowing *out* of the secondary winding
 - Lenz's law: The current induced on the secondary is such that the secondary flux produced opposes the primary flux.
- The total flux in the core is:

$$\psi_m = N_p A_\ell I_p - N_s A_\ell I_s$$


- Port current relationship:

$$I_p = \frac{\psi_m}{N_p A_\ell} + \frac{N_s}{N_p} I_s. \quad \because V_p = j\omega N_p \psi_m$$

$$I_p = \frac{V_p}{j\omega N_p^2 A_\ell} + \frac{N_s}{N_p} I_s$$

- However, $N_p^2 A_\ell$ is the inductance of the primary winding. Thus:
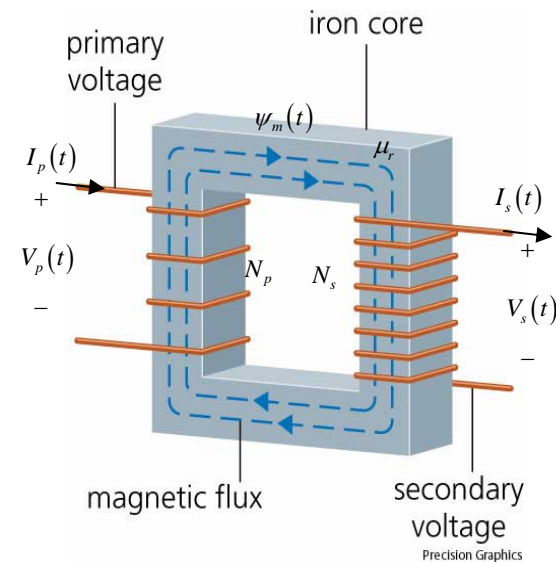
$$I_p = \frac{V_p}{j\omega L_p} + \frac{N_s}{N_p} I_s$$



Transformers & Tuned Transformers


$$I_p = \frac{V_p}{j\omega L_p} + \frac{N_s}{N_p} I_s$$

- $\frac{V_p}{j\omega L_p}$ is the magnetization current
 - Current is independent of the secondary winding.
 - This is the current of an N_p turn inductor wound on the core
- $\frac{N_s}{N_p} I_s$ is the transformer current due to a current on the secondary winding.
 - Current is transformed similar to the voltage – but with a reciprocal relationship
 - If $N_s > N_p$, $I_s < I_p$ ($V_s > V_p$) (step-up transformer)
 - If $N_p > N_s$, $I_p < I_s$ ($V_p > V_s$) (step-down transformer)


Transformers & Tuned Transformers

The Ideal Transformer

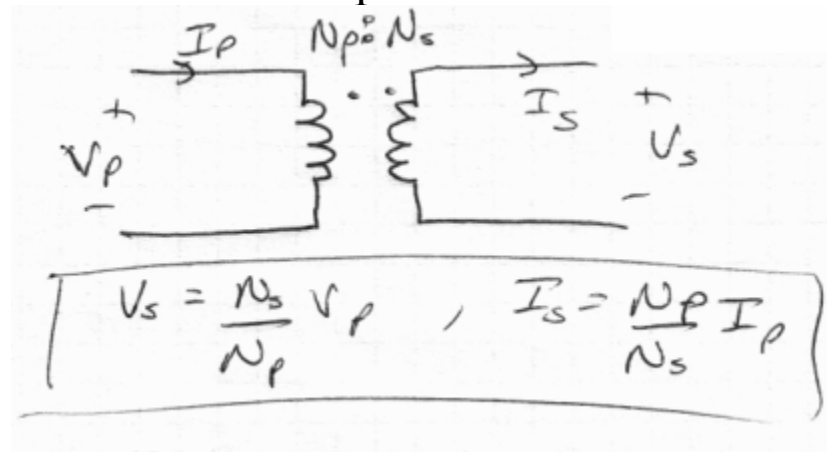- Assume that $\frac{V_p}{j\omega L_p} \ll \frac{N_s}{N_p} I_s$
 - true if ω or L_p is sufficiently large
- Then: $I_p \approx \frac{N_s}{N_p} I_s$
- Ideal Transformer makes this assumption:




- Impedance Transformation:

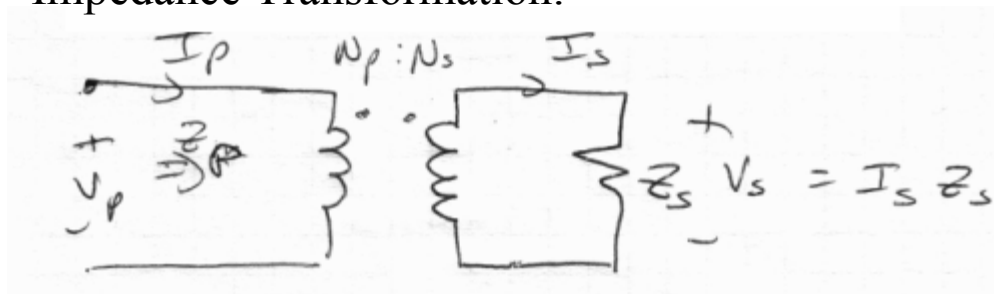

$$Z_p = \frac{V_p}{I_p} = \frac{(N_p / N_s) V_s}{(N_s / N_p) I_s} = \frac{N_p^2}{N_s^2} Z_s$$

Transformers & Tuned Transformers

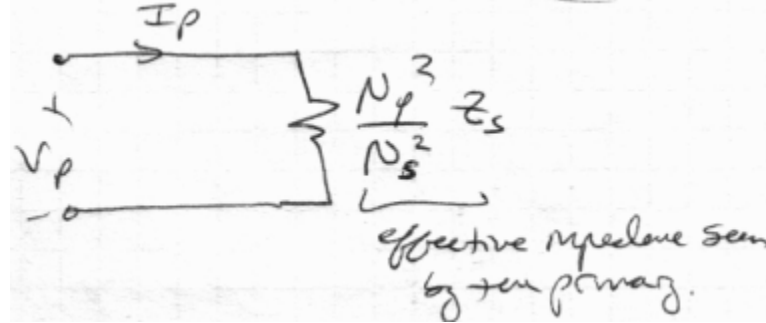- An equivalent circuit can be drawn relative to the primary winding:



- The transformer effectively “transforms” the load impedance by the turns-ratio squared.
- Power of the ideal transformer:

$$P_p(t) = V_p(t) I_p(t) = \text{instantaneous power}$$

$$P_s(t) = V_s(t) I_s(t)$$

$$= \frac{N_s}{N_p} V_p(t) \frac{N_p}{N_s} I_p(t)$$


$$= V_p(t) I_p(t)$$

$$\therefore P_s(t) = P_p(t)$$

Transformers & Tuned Transformers

Transformers of the NORCAL40A

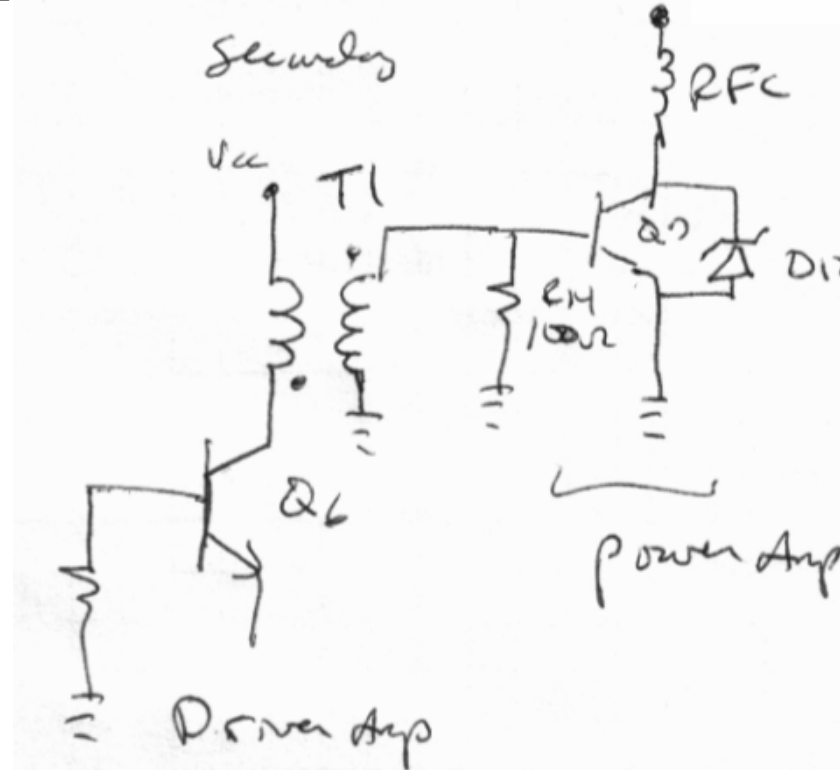- Transformer “T1” (see ckt diagram on the inside of the front cover of text):
 - Couples the output of the driver amplifier to the input of the power amp
 - Decouples the DC bias networks
 - Doubles the efficiency of the driver amp, since the DC bias current is not dissipated by the effective RF collector load (R14).
 - Steps up the current in the power amp (turns ratio 14:4)



Transformers & Tuned Transformers


- Transformers T2 and T3 are “tuned transformers” (studied next)
- T2
 - provides the inductance of a parallel resonator of the RF filter.
 - It also transforms the impedance to match the 50 ohm filter to the 1500 ohm input of the RF Mixer.
- T3
 - Parallel LC (C6 combined with the parallel capacitance of the output of the RF mixer) is resonant at the IF frequency, such that the reactance cancels.
 - Used to transform the impedance to match the output of the RF mixer (3 kΩ) to the input of the IF filter (200 Ω)

$$Z_s = \left(\frac{N_s}{N_p} \right)^2 Z_p = \left(\frac{6}{23} \right)^2 3000 = 204.2 \Omega$$

Transformers & Tuned Transformers

Tuned Transformer

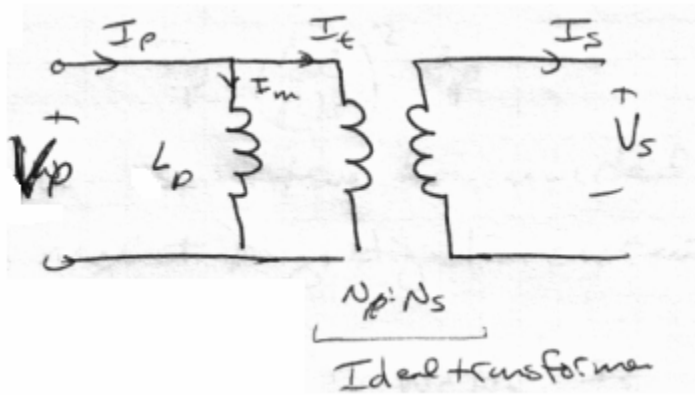
- Equivalent circuit of the transformer (including magnetization and transformer currents):



$$I_p = I_m + I_t = \frac{V_p}{j\omega L_p} + \frac{N_s}{N_p} I_s = \frac{V_p}{j\omega A_\ell N_p^2} + \frac{N_s}{N_p} I_s$$


or,
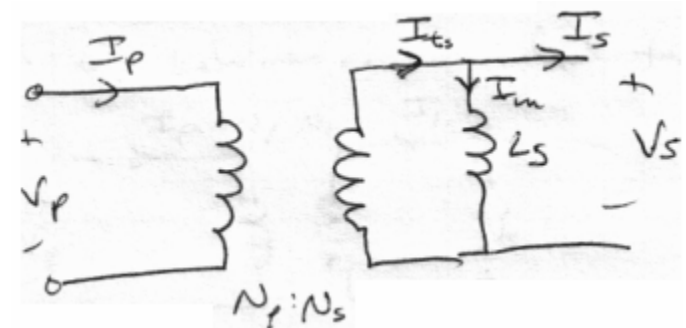
$$\begin{aligned} I_s &= \frac{N_p}{N_s} I_p - \frac{N_p}{N_s} \frac{V_p}{j\omega A_\ell N_p^2} = \frac{N_p}{N_s} I_p - \frac{1}{N_s} \frac{V_p}{j\omega A_\ell N_p} = \frac{N_p}{N_s} I_p - \frac{1}{N_s} \frac{V_s (N_p / N_s)}{j\omega A_\ell N_p} \\ &= \frac{N_p}{N_s} I_p - \frac{V_s}{j\omega A_\ell N_s^2} = \frac{N_p}{N_s} I_p - \frac{V_s}{j\omega L_s} = I_{t_s} - I_{m_s} \end{aligned}$$



Transformers & Tuned Transformers

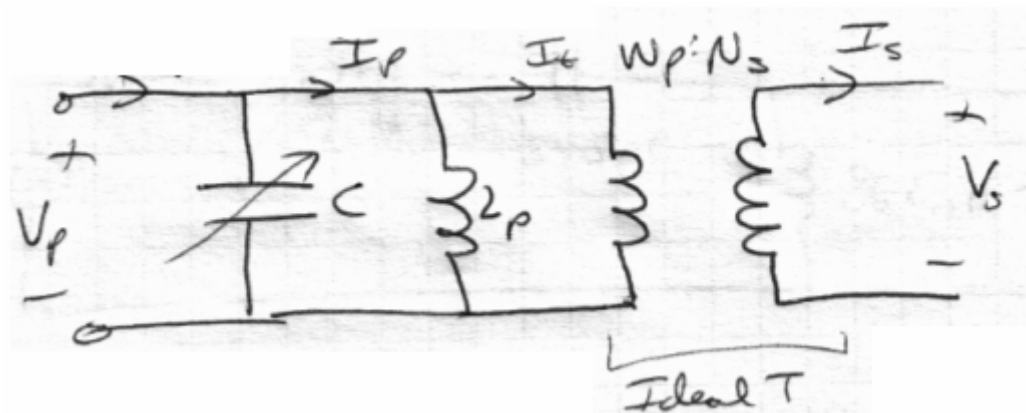- Observations
 - The primary inductance maps into the secondary inductance through the transformer
 - The secondary current drops due to the magnetization current.
 - If the reactance of the shunt inductance is sufficiently small, it significantly loads the transformer
- The reactance can be “tuned” out with a shunt capacitance at a resonant frequency.
 - Example:




Adjust C such that:

$$j\omega_o C = \frac{-1}{j\omega_o L_p} \Rightarrow \omega_o = \frac{1}{\sqrt{L_p C}}, \text{ or, } C = \frac{1}{L_p \omega_o^2} = \frac{1}{(2\pi f_o)^2 L_p}$$


The network then behaves as an ideal transformer at f_o . (T3)

Transformers & Tuned Transformers

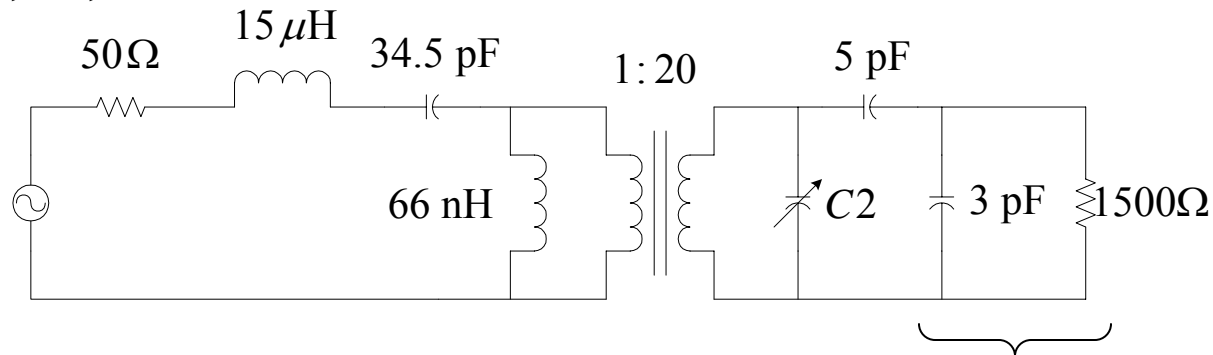- The tuned transformer can also be used as a parallel resonator branch of a band-pass filter
- The parallel susceptances will cancel at the center frequency of the filter.
- L_p and C are chosen according to the BPF design (from prototype).
- Example, T2, Problem 16





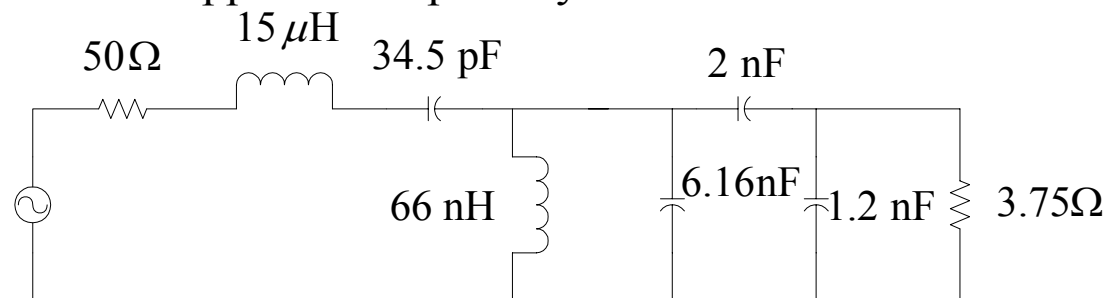- In problem 16, the 3 pF load is the 13.3 pF scope capacitance
 ○ Here, we assume the actual load, and let $C_2 = 15.4$ pF.
- The circuit can be mapped to the primary:




Transformers & Tuned Transformers

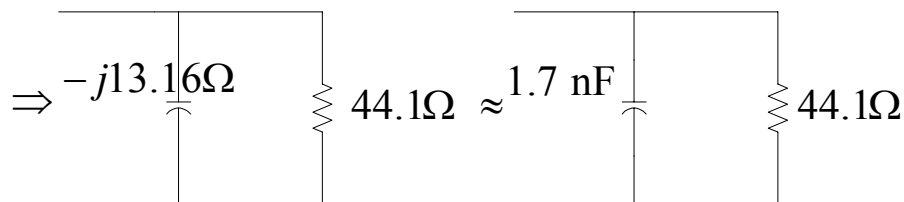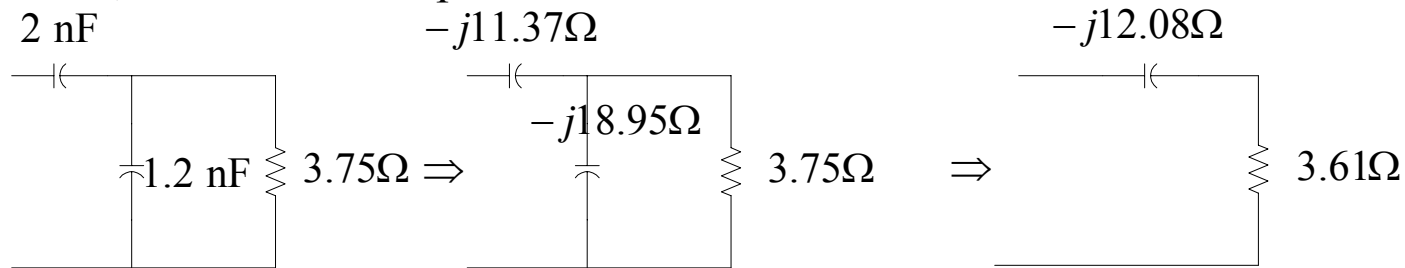- The load with the blocking capacitor is transformed via a parallel-to-series conversion, then a series to parallel conversion as:



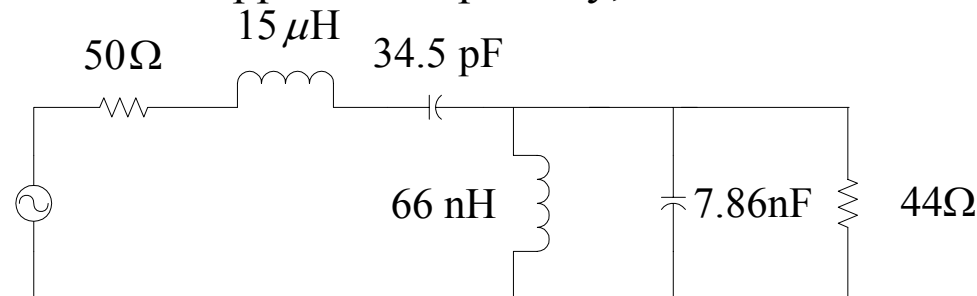- Combining this with C2 mapped to the primary, leads to the final circuit:




- This is close to the Butterworth design (“BandPassFilters.pdf”, pg. 5)
 - Parallel resonator slightly out of tune. $Z_{in} = 43.8 - j1.6\Omega$ @ 7 MHz


Transformers & Tuned Transformers

Loading by Scope Probe

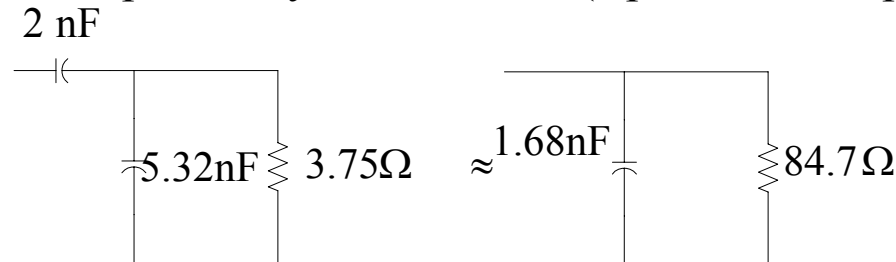- In P16, scope probe capacitively loads the ckt ($C_{\text{probe}} = 13.3 \text{ pF}$)




- Final circuit:

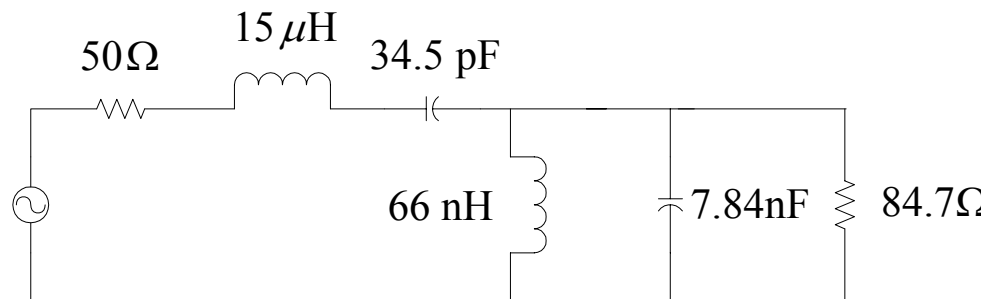


- Load has significantly increased.
 - $Z_{in} = 84.6 - j1.66 \Omega @ 7 \text{ MHz}$
- The probe loads the circuit, degrading the performance from what it actually is. Though, it still approximates it, as seen from the following PUFF simulations

Transformers & Tuned Transformers

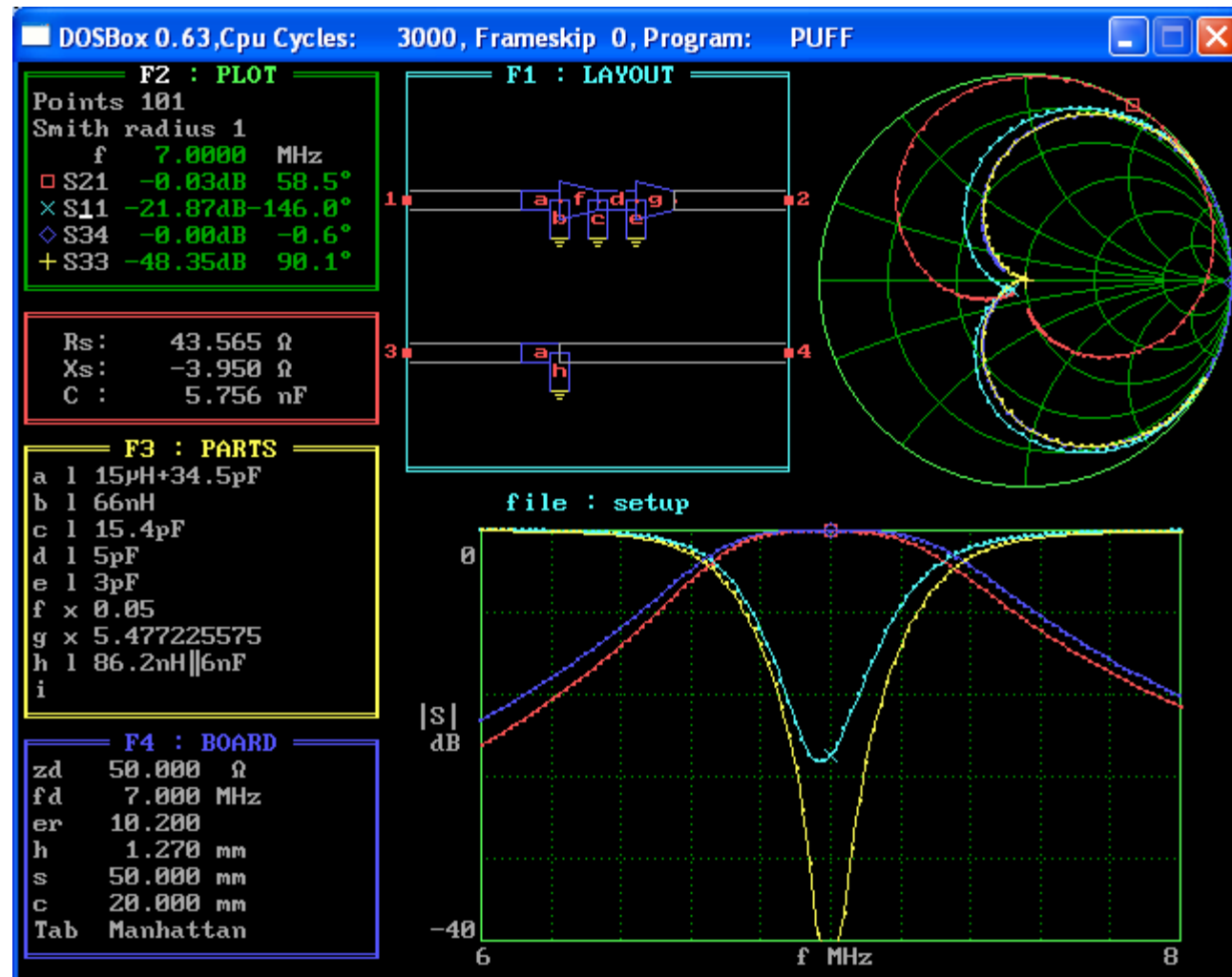

Transformers & Tuned Transformers


Loaded with the Scope Capacitance

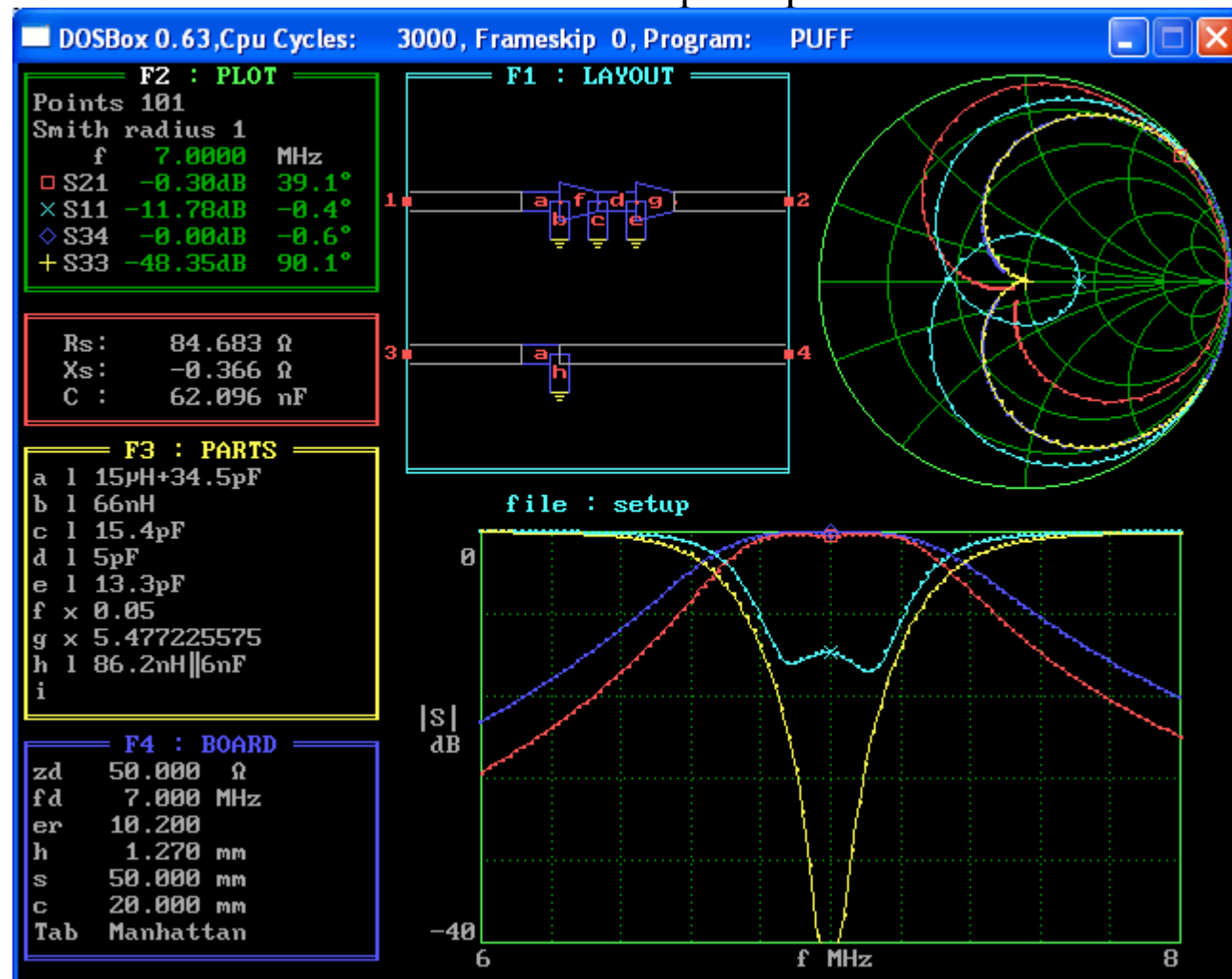

Transformers & Tuned Transformers

Loss Factor

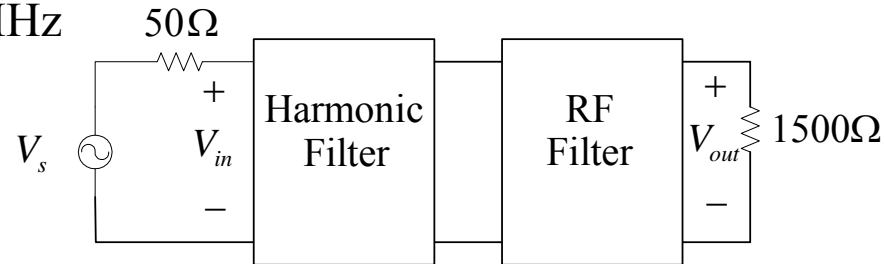
- The principal purpose of the combined RF and Harmonic Filter is to reject the image frequency of the RF mixer, as well as other “spurs” of the Gilbert cell mixer.
 - Image frequency = 4.9 MHz – 2.1 MHz = 2.8 MHz
 - Dominant *spur* = 5.6 MHz



- At resonance (7 MHz), there is insertion loss due to miss-matches and losses of the filters. We measure this via the loss factor at 7 MHz
- We will also measure the “Rejection” Loss at the IF and spurious frequencies.

- We measure the loss factor as: $L = 10 \log \left(\frac{P^+}{P_{out}} \right)$

- P_{out} = power delivered to the load = $\frac{1}{8} \frac{V_{out}^2}{1500}$

- P^+ = the *available power* from the source = $\frac{1}{8} \frac{V_{in}^2}{50}$ 

- Note that the available power P^+ is the maximum power available from the source, and is the power that would be dissipated by a matched load.
 - Also, note that $L \neq 20 \log(V_{out}/V_{in})$!! Why not?