



I use a tie point for neatness. Two distinct wires for the track and two for the DCC booster. The top color diagram shows the foils side of the board with components underneath. Ask your electronics store for the NPN equivalent of a BD442 power transistor. Then common ground for Twin-T will be negative. This is just like your last circuit without any diodes. The power transistors take care of the high currents so diodes are not needed.