



**SOUTH WEST GAUTENG COLLEGE**  
EDUCATION OF DISTINCTION

# **INDUSTRIAL ELECTRONICS N4**


## **ASSIGNMENT 1**

INDUSTRIAL ELECTRONICS N4

SUBJECT CODE: IEL 400

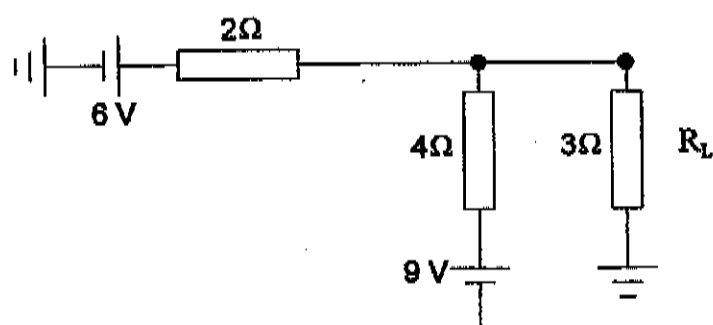QUESTION 1


Determine the value of the current through  $R_L$  in the following diagram using Kirchhoff's law (only).



[10]

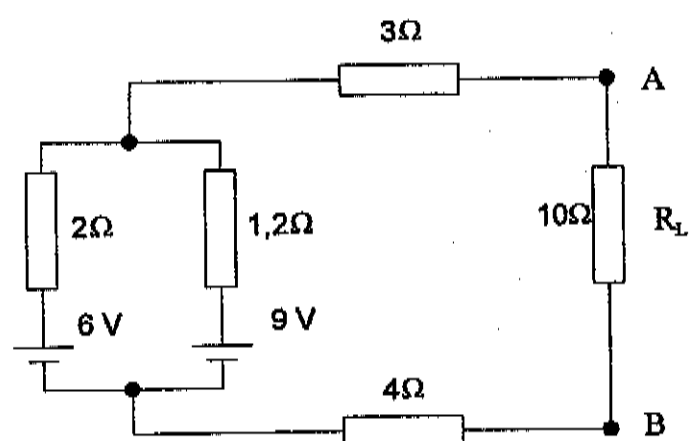QUESTION 2


Use Thevenin's method to calculate the potential difference across  $R_L$  in the following figure.



[10]
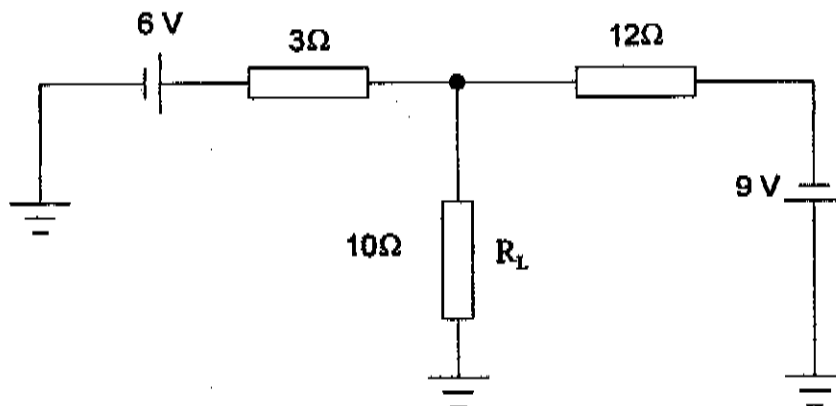
## QUESTION 3


Use the superposition method to calculate the current flow through  $R_L$  in the following figure.



[10]
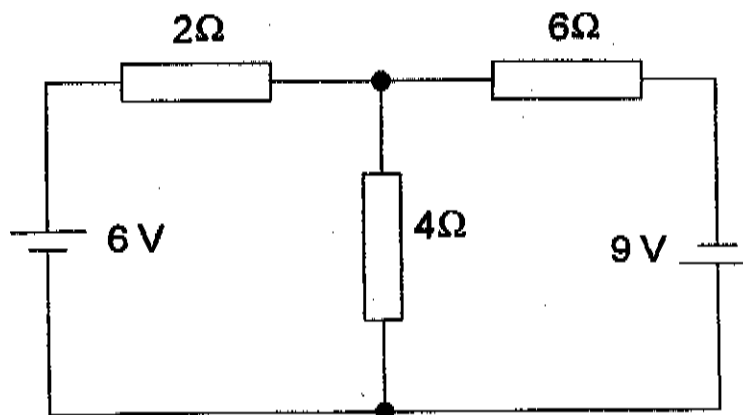
## QUESTION 4


Use Thevenin's theorem to calculate through the  $4\Omega$  resistor in the following diagram.



[10]

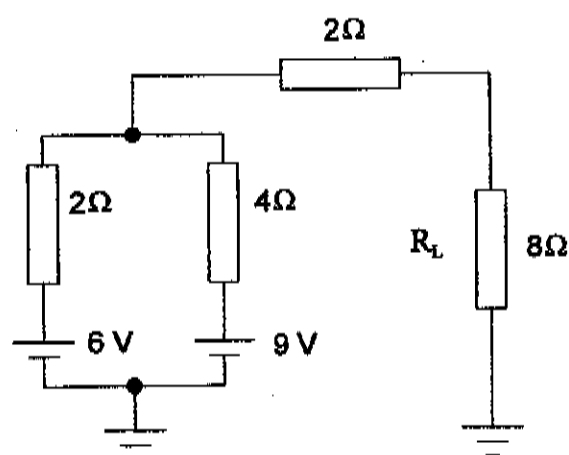QUESTION 5


Use Thevenin's method to calculate the current flow through  $R_L$  in the following figure.



[10]

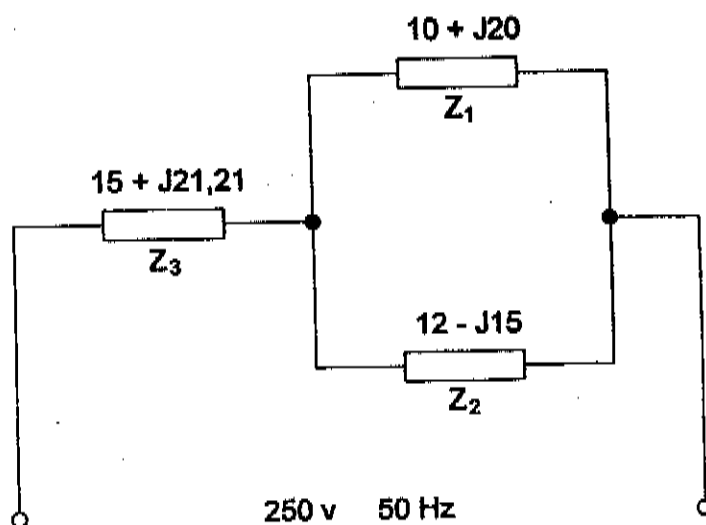QUESTION 6

Calculate the total circuit impedance and circuit current using j-notation only.




[10]

## QUESTION 7

If the following circuit is resonant, calculate the following:

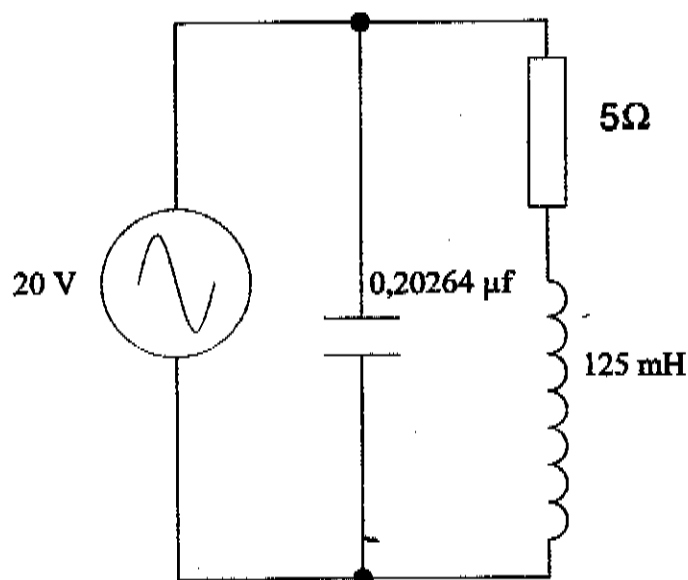
- (1) The resonant frequency.
- (2) The current through the coil.
- (3) The current through the capacitor.
- (4) The dynamic impedance.
- (5) The total current from the supply.
- (6) Draw the phasor diagram.



[10]

## QUESTION 8

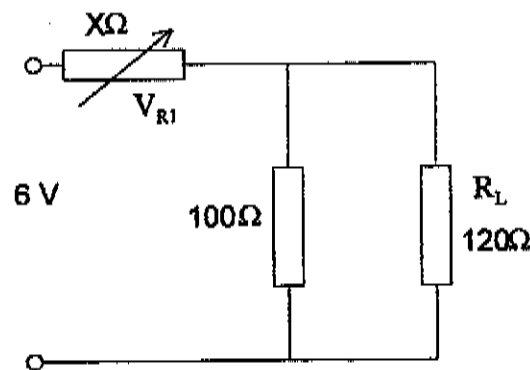- (a) From the following circuit diagram what is dissipated in  $R_L$  when  $VR_1$  is set to 0  $\Omega$ ?  
(1)
- (b) From the circuit diagram what power is dissipated in  $R_L$  when  $VR_1$  is set to 50  $\Omega$ ?  
(1)



(For the following type of question only write the correct answer in your assignment)

- (c) A germanium diode must have at least (0,3/0,7) volts or greater forward bias before the diode (switches off/conducts). (1)
  - (d) When a junction diode is forward biased the (positive/negative) side of the supply is coupled to the diode. (1)
  - (e) If a zener diode is inserted the wrong way round (incorrectly) it behaves like a (junction diode/varactor diode/tunnel diode). (1)
  - (f) What is expected output voltage of a zener diode, specified as  $9\text{ V} \pm 10\%$ ? (1)
  - (g) In a series RLC circuit at resonance the impedance is at (minimum/maximum) and is equal to  $(R/X_L/X_C)$ . (2)
  - (h) In a series RLC circuit at resonance the supply voltage is equal to  $(V_R/V_L/V_C)$  and the circuit current is at a (minimum/maximum). (2)
- [10]

#### QUESTION 9

- (a) Define impedance. (2)
  - (b) Define or describe Q factor. (2)
  - (c) In a parallel resonant circuit at resonance the impedance is (minimum/maximum) and the circuit current is at (minimum/maximum). (2)
  - (d) At resonance  $X_L = X_C$  in (a series/parallel/both series and parallel) circuit/s. (1)
  - (e) A series resonant circuit is also known as an (acceptor/rejector). (1)
  - (f) A parallel resonant circuit is also known as an (acceptor/rejector). (1)
  - (g) At resonance the power factor of a circuit is  $(1/0^\circ)$  (1)
- [10]

**QUESTION 10**

Explain with the aid of a neat, labeled circuit diagram, how a unijunction transistor can be used to trigger a silicon controlled rectifier(SCR). [10]



**SOUTH WEST GAUTENG COLLEGE**  
EDUCATION OF DISTINCTION

# **INDUSTRIAL ELECTRONICS N4**

## **ASSIGNMENT 2**



## INDUSTRIAL ELECTRONICS N4


SUBJECT CODE: IEL 400

## QUESTION 1

- (a) A 9 volt regulator uses a 0,5 W zener diode to supply a constant voltage of 9 volts from a 12 volt supply. Calculate a suitable value for the series resistor if the load current is 15 mA. (4)
- (b) A power supply delivers a no-load voltage of 22 volts. At full load the voltage drops to 18 volts. Calculate the percentage voltage regulation. (2)
- [6]
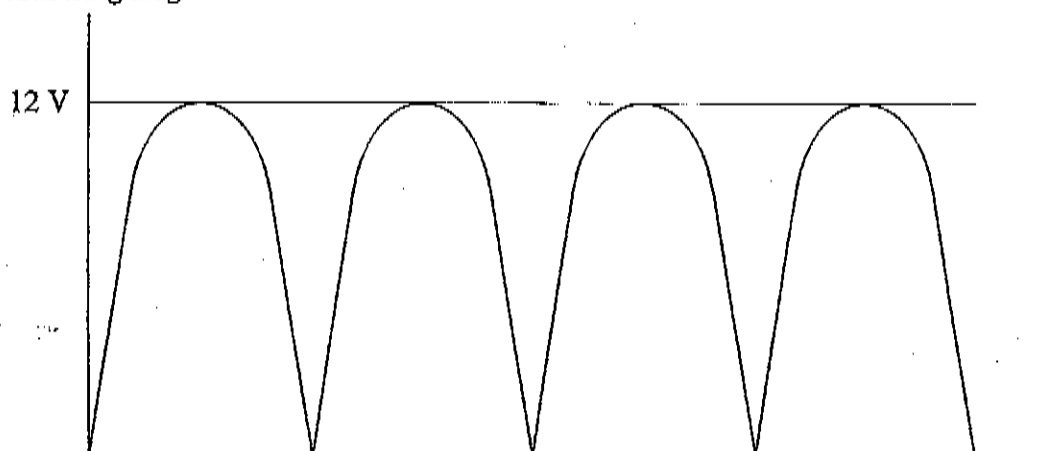
## QUESTION 2

The following diagram is of the waveform obtained from a full wave bridge rectifier.




Calculate:

- (1) The average DC voltage. (2)
- (2) The pulsating DC voltage when no filter circuit is used. (1)
- (3) The transformer's secondary RMS voltage. (1)
- (4) The output ripples voltage. (2)
- (5) The ripple factor when no filter is used. (1)
- (6) The transformer's secondary peak voltage. (1)
- (7) The transformer's average DC voltage. (1)
- (8) The peak inverse voltage (PIV). (1)
- [10]

## QUESTION 3

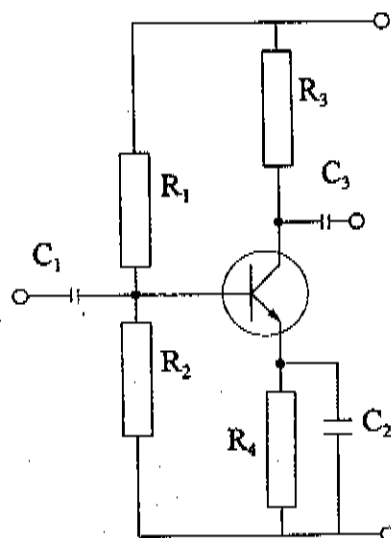- (a) In a CE transistor circuit if the emitter current is 40 mA and the base current is  $75 \mu\text{A}$ , what is the collector current? (2)
- (b) What is the function of each numbered component in the following diagram? (3)



What is the affect on the amplifier if C2 is removed? Gain will (increase/decrease). (1)

- (c) Draw a neat, fully labeled characteristic curve of a unijunction transistor. (3)
- (d) A FET is a (current/voltage) controlled device. (1)
- (e) Draw a neat, fully labeled characteristic curve of a tunnel diode. (4)
- [14]

## QUESTION 4

- (a) Draw a neat, fully labeled circuit diagram to show how a triac can be used to control the speed of a small AC motor. The following voltage waveforms must be shown: (i) Input voltage. (ii) Voltage across the motor. (iii) Voltage across the triac. (6)
- (b) Draw the circuit diagram and calculate the output voltage of a voltage summing op-amp. The values of the input voltages and resistances are given in the table and the feedback resistance is  $680 \text{ k}\Omega$ .

$V_1 = 1,75$ volt	$R_1 = 100$ k $\Omega$
$V_2 = 2,854$ volt	$R_2 = 120$ k $\Omega$
$V_2 = 2,325$ volt	$R_3 = 500$ k $\Omega$

(4)

[10]

**QUESTION 5**

- (a) Define a transducer. (2)
- (b) What is the basic function of a potentiometer as a transducer? (2)
- (c) Give four requirements of a transducer. (4)
- (d) Give two physical quantities that are converted to electrical output values by transducers. (2)

[10]

**QUESTION 6**

- (a) What is a function generator? (2)
- (b) Can a function generator supply different output waveforms simultaneously? Motivate your answer. (2)
- (c) Draw a block diagram of a basic function generator; your drawing must be fully labeled. (4)
- (d) Draw a neat square wave with a mark to space ratio of one. Clearly label the mark, space, a leading edge and a trailing edge. (2)

[10]

**QUESTION 7**

- (a) A sine wave is displayed on a CRO screen (oscilloscope). The peak-to-peak distance is 5 cm and the distance between cycles is 4 cm. The volts/cm dial is set to 10v/cm and the time/div is set at 100  $\mu$ sec/cm. From the following list of possible answers, choose the correct answer for each of the questions.

25 volt	5 volt	0,4 ms	35,4 volt	4 ms
50 volt	250 Hz	2,5 volt	2,5 kHz	17,7 volt

- (i) Determine the peak-to-peak voltage.
- (ii) Determine the periodic time of the waveform.

- (iii) Determine the maximum value of the voltage.
- (iv) Determine the frequency of the waveform.
- (v) Determine the RMS value of the waveform. (5)
- (b) For a PNP silicon transistor the voltage drop across the base-emitter junction in normal operations is  $\pm$ 

200 mV	600 mV	0 V	4,4 V
--------	--------	-----	-------

 and the current flow across the base-emitter junction consists of mainly 

electrons	holes	Leakage current
-----------	-------	-----------------

 (2)
- (c) What are the three basic bipolar transistor configurations? (3)
- (d) Show, using a neat circuit diagram how a common emitter amplifier that incorporates a photodiode can be used to draw attention when someone enters a room. (4)
- (e) Name five advantages of the SCR (silicon controlled rectifier). (5)
- (f) Name three ways in which op-amps may be used. (3)
- (g) Sketch labeled symbols for each of the following: unijunction transistor, NPN transistor, field effect transistor, N-channel Mosfet, and PNP transistor. (5)
- (h) How is a transistor biased for use as a switch? (2)
- (i) Name two ways in which full wave rectification may be achieved. (2)
- (j) A transformer has 12 times as many primary turns as secondary turns, what is the secondary voltage? (2)
- (k) (i) What is meant by the term "negative temperature coefficient"? (1)
- (ii) When is a system considered "closed loop" (1)
- (iii) What is commutation when referring to SCR's? (1)
- (iv) The unijunction transistor is a bipolar device. (TRUE/FALSE) (1)
- (v) The FET is suitable for input stages to FM receivers. (TRUE/FALSE) (1)

(vi) What is the basic difference between the J-FET and MOS-FET? (1)

(vii) What is the PIV rating for the diodes used in a center tapped full wave rectifier circuit? (1)  
[40]

**TOTAL FOR THIS ASSIGNMENT: 100**

