



R1, R2, R3, R4 = 10K 0.25 w
 Q1, Q5 = N channel Power Mosfet
 Q2, Q6 = P channel Power Mosfet
 Q3, Q4 = N channel Jfet
 D1, D2, D3, D4 = Schottky Diode

When input 1 goes high it turns on Q1 and Q3.
 When Q3 turns on it turns on Q6 which means
 the motor rotates.

When input 2 goes high it turns on Q5 and Q4.
 When Q4 turns on it turns on Q2 which means
 the motor rotates in the opposite direction.

Renault Scenic window Motor Controller			
TITLE			
FILE:	window-control1.sch	REVISION:	
PAGE	1 OF 1	DRAWN BY:	Norman Elliott