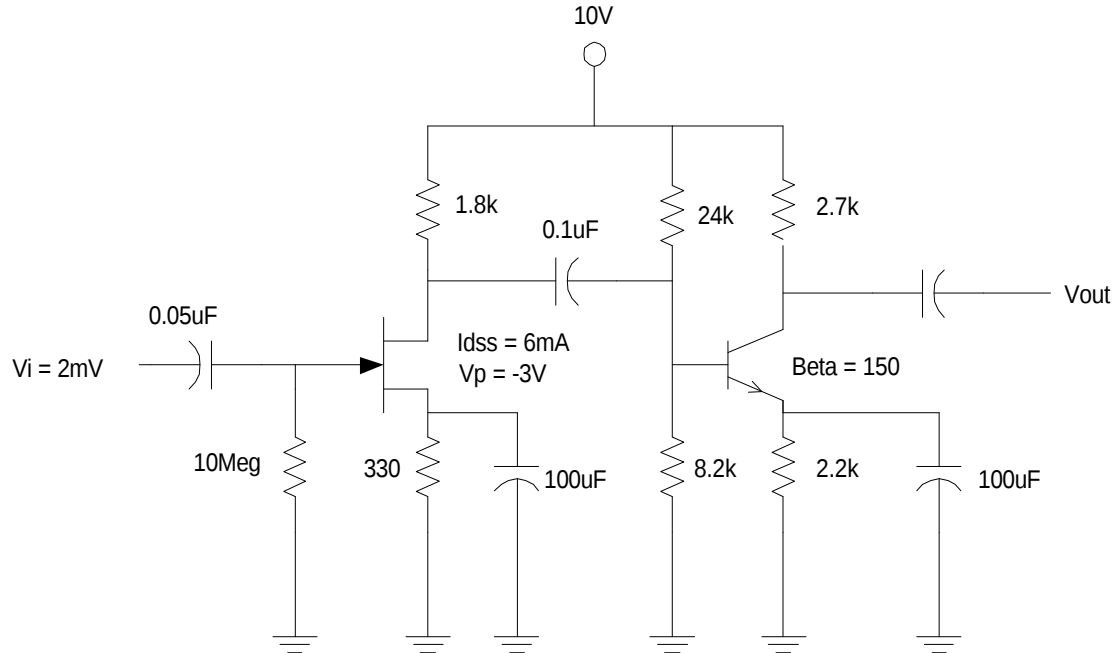


For the following cascade amplifier, calculate the DC bias voltages, the collector currents of each stage, the voltage gain of each stage, the overall amplifier gain, the input impedance, and the output impedance.



Solution

DC Analysis:


$$V_{gsq} = -0.95V \text{ (see graph)}$$

$$I_{dq} = 2.8mA \text{ (see graph)}$$

$$V_d = 10V - (2.8mA)(1.8k) = 4.96V$$

$$V_s = (2.8mA)(330) = 924mV$$

$$V_g = 0V$$

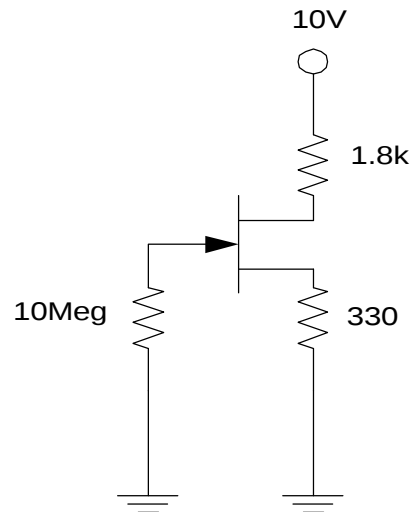


$$V_b = \frac{10V(8.2k)}{24k + 8.2k} = 2.55V$$

$$V_e = 2.55V - 0.7V = 1.85V$$

$$I_e = \frac{1.85V}{2.2k} = 0.84mA = I_c$$

$$V_c = (2.7k)(0.84mA) = 2.27V$$

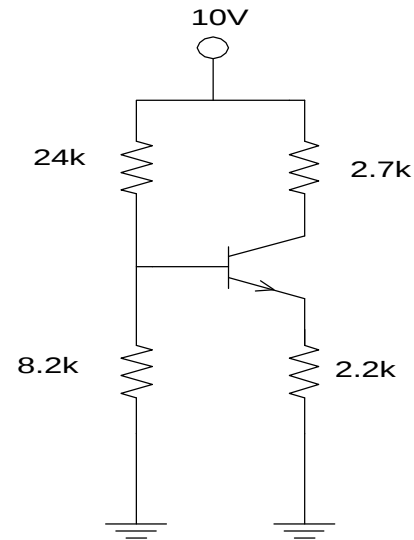
$$I_b = \frac{1}{150}(0.84mA) = 5.6\mu A$$



AC Analysis:

$$r_e = \frac{V_T}{I_{CQ}} = \frac{26mV}{0.84mA} = 30.9\Omega$$
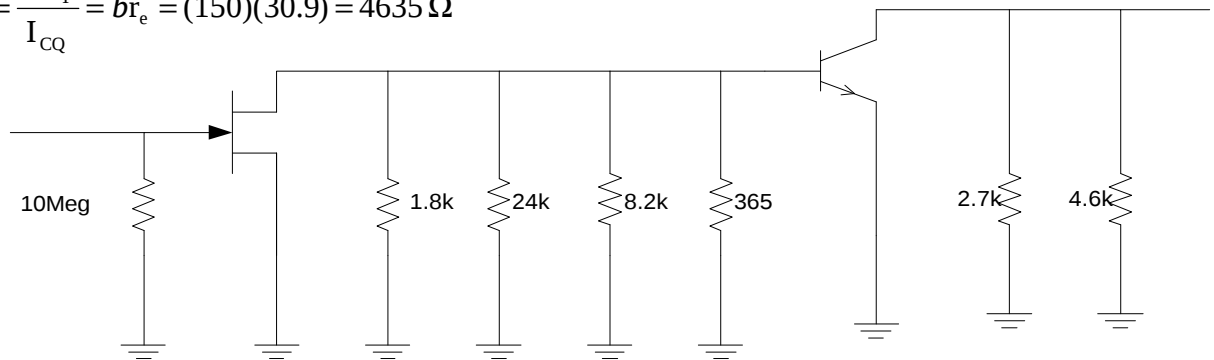
$$r_p = \frac{bV_T}{I_{CQ}} = br_e = (150)(30.9) = 4635\Omega$$



$$g_m = \frac{2(I_{DSS})}{|V_P|} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = \frac{2(6mA)}{3} \left(1 - \frac{-0.95}{-3} \right) = 2.73 \times 10^{-3} \text{ mho}$$

$$r_d = \frac{1}{g_m} = 365\Omega$$

$$A_{V(FET)} = -g_m (r_o \parallel R_D \parallel R_L \parallel r_d)$$

$$A_{V(FET)} = (-2.73mho)(1.8k \parallel 24k \parallel 8.2k \parallel 365\Omega) = (289\Omega)(-2.73 \times 10^{-3} \text{ mho}) = -0.79$$

$$A_{V(BJT)} = \frac{-(b)(R_C \parallel r_p)}{r_p} = \frac{-(150)(2.7k \parallel 4.6k)}{4.6k} = -55$$

$$A_{V(Total)} = (A_{V1})(A_{V2}) = (-0.79)(-55) = 43.75$$

$$R_{in} = 10M\Omega$$

$$R_{Out} = 2.7k$$

Graph of I_d (mA) vs. V_{gs} (V)

$$I_d = 6\text{mA} \left(1 - \frac{V_{gs}}{-3} \right)^2$$

