

EE241 - Spring 2003

Advanced Digital Integrated Circuits

Lecture 20

Multipliers

UC Berkeley EE241

B. Nikolic, J. Rabaey

Binary Multiplication

$$\begin{aligned}
 Z = \vec{X} \times \vec{Y} &= \sum_{k=0}^{M+N-1} Z_k 2^k \\
 &= \left(\sum_{i=0}^{M-1} X_i 2^i \right) \left(\sum_{j=0}^{N-1} Y_j 2^j \right) \\
 &= \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right)
 \end{aligned}$$

with

$$\begin{aligned}
 X &= \sum_{i=0}^{M-1} X_i 2^i \\
 Y &= \sum_{j=0}^{N-1} Y_j 2^j
 \end{aligned}$$

UC Berkeley EE241

B. Nikolic, J. Rabaey

Binary Multiplication

$$\begin{array}{r}
 \begin{array}{r}
 1\ 0\ 1\ 0\ 1\ 0 \\
 \times \quad 1\ 0\ 1\ 1 \\
 \hline
 1\ 0\ 1\ 0\ 1\ 0 \\
 0\ 0\ 0\ 0\ 0\ 0 \\
 1\ 0\ 1\ 0\ 1\ 0 \\
 \hline
 1\ 1\ 1\ 0\ 0\ 1\ 1\ 1\ 0
 \end{array}
 \end{array}$$

N bits
 M bits
 AND operation
 Partial Products
 N+ M bits in the final sum

UC Berkeley EE241

B. Nikolic, J. Rabaey


Shift-and-Add Multiplier

- Standard adder and shift-in the multiplicand
- Shift the result as well and add
- N cycles
- Parallel adders add more hardware (adders) instead.

UC Berkeley EE241

B. Nikolic, J. Rabaey


Array Multiplier

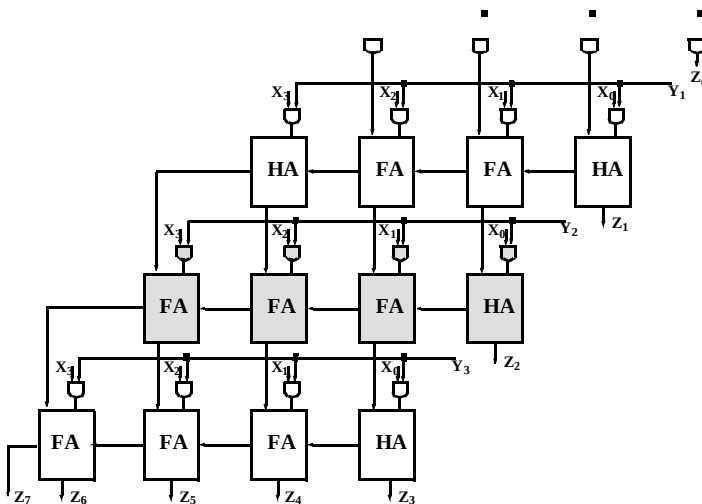

UC Berkeley EE241

B. Nikolic, J. Rabaey

MxN Array Multiplier — Critical Path

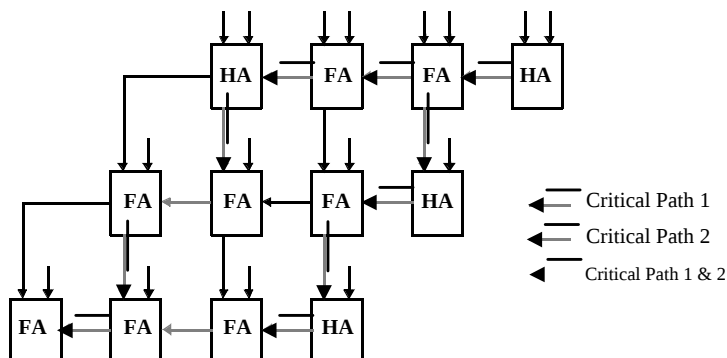


$$t_{mult} \sim [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$

UC Berkeley EE241

B. Nikolic, J. Rabaey

Adder Cells in Array Multiplier

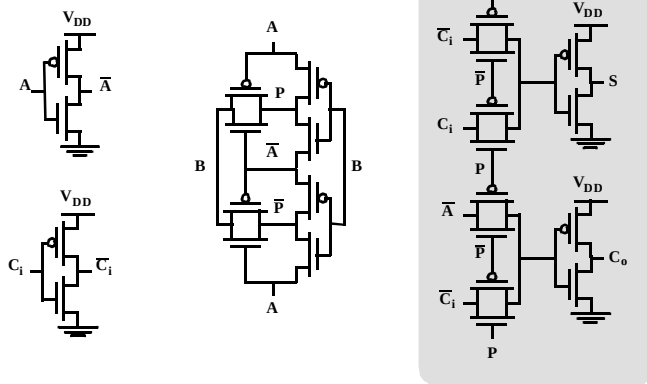


Identical Delays for Carry and Sum

UC Berkeley EE241

B. Nikolic, J. Rabaey

Carry-Save Multiplier

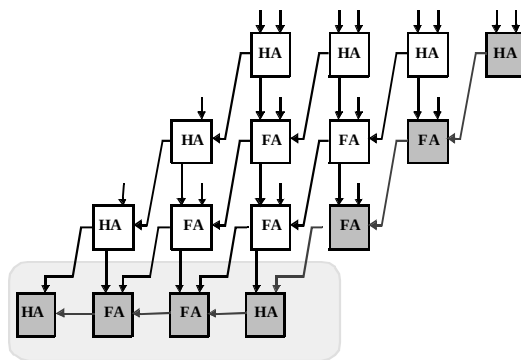


Vector Merging Adder

$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

UC Berkeley EE241

B. Nikolic, J. Rabaey

Multiplier Floorplan

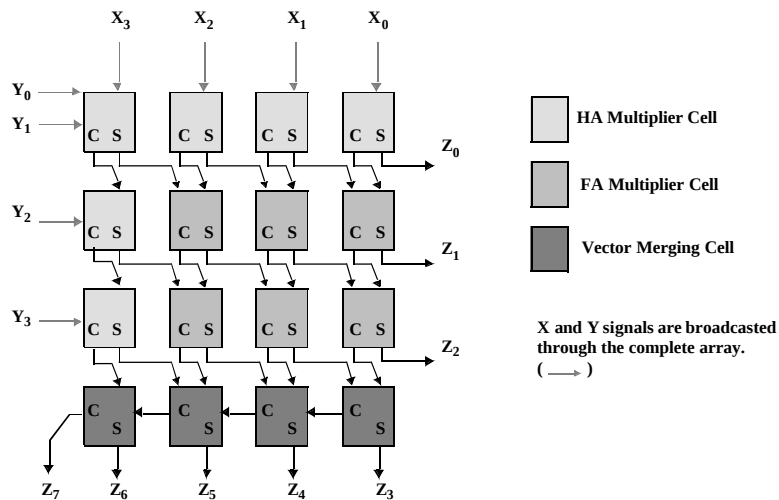

UC Berkeley EE241

B. Nikolic, J. Rabaey

Multipliers


- Partial product generation
- Partial product accumulation
- Final summation

UC Berkeley EE241

B. Nikolic, J. Rabaey

Generating Partial Products

- All partial products: AND

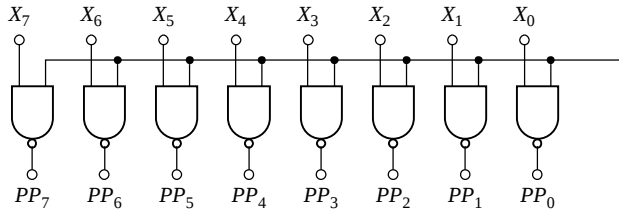

- Booth's recoding – reduction of partial product count

UC Berkeley EE241

B. Nikolic, J. Rabaey

Booth Recoding

- Instead of generating all the partial products
 $0 * x = 0$ $1 * x = x$ $x = \{0,1\}$
- Reduce the number of partial products by grouping

0 0	0	
0 1	1^*	
1 0	2^*	(shift)
1 1	3^*	(or $4^* - 1$)

Booth'51

UC Berkeley EE241

B. Nikolic, J. Rabaey

Booth Recoding

- Instead of using set $\{0, 1*Y, 2*Y, 3*Y\}$
- Use $\{0, 1*Y, 2*Y, 4*Y, -Y\}$
- Shifting and complementing
- $3*Y = 4*Y - Y$
- Can be simplified by looking into three bits – modified Booth recoding

UC Berkeley EE241

B. Nikolic, J. Rabaey

Modified Booth Recoding


Two bits and the MSB of previous two

$x_{i+2}x_{i+1}x_i$	Add to partial product
000	+0Y
001	+1Y
010	+1Y
011	+2Y
100	-2Y
101	-1Y
110	-1Y
111	-0Y


UC Berkeley EE241

B. Nikolic, J. Rabaey

Accumulating Partial Products

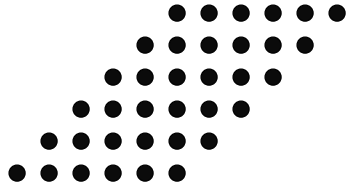

Partial product matrix


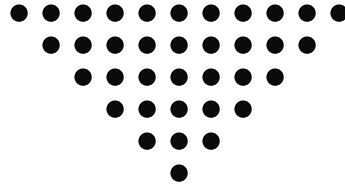


Reorganized matrix

UC Berkeley EE241

B. Nikolic, J. Rabaey


Wallace-Tree Multiplier

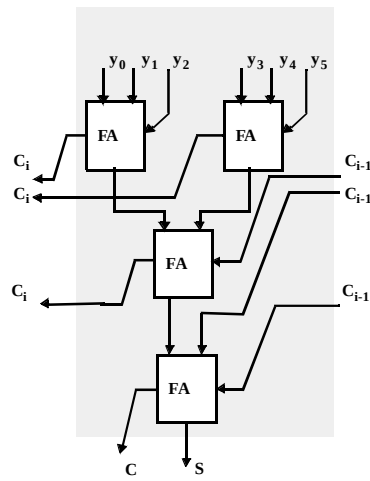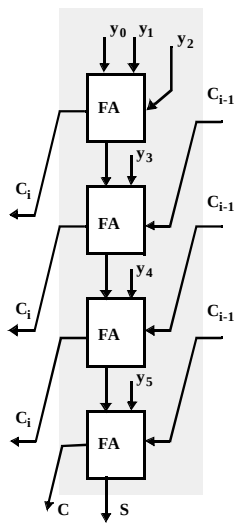

UC Berkeley EE241

B. Nikolic, J. Rabaey


Wallace-Tree Multiplier

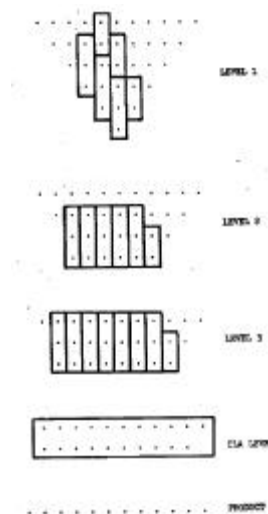

UC Berkeley EE241

B. Nikolic, J. Rabaey

Wallace-Tree Multiplier

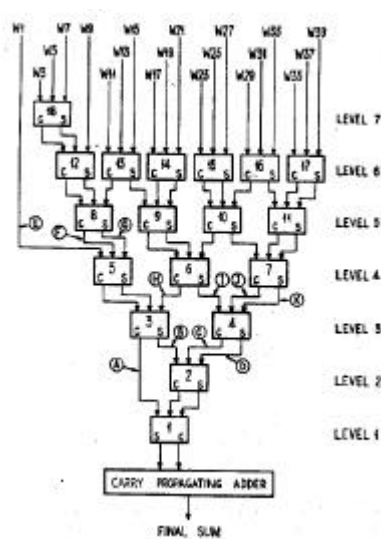

Wallace,
Trans on Comp. 2/64

UC Berkeley EE241

B. Nikolic, J. Rabaey

Tree Multipliers

- Time is proportional to $\log N$
- Wiring is complicated
- Different wire lengths
- Optional pipelining
- Wallace tree: reduce the number of operands at earliest opportunity
- Dadda tree: reduce the number of operands with fewest adders

UC Berkeley EE241

B. Nikolic, J. Rabaey

Minimum Number of Stages


Number of bits in the multiplier	Number of stages
3	1
4	2
$4 < n \leq 6$	3
$6 < n \leq 9$	4
$9 < n \leq 13$	5
$13 < n \leq 19$	6
$19 < n \leq 28$	7
$28 < n \leq 42$	8
$42 < n \leq 63$	9

Dadda, '65

UC Berkeley EE241

B. Nikolic, J. Rabaey

Generalized Counters

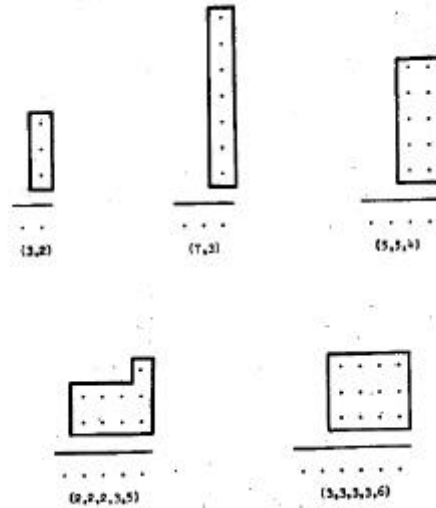


Stenzel,
Trans on Comp 10/77

UC Berkeley EE241

B. Nikolic, J. Rabaey

Generalized Counters

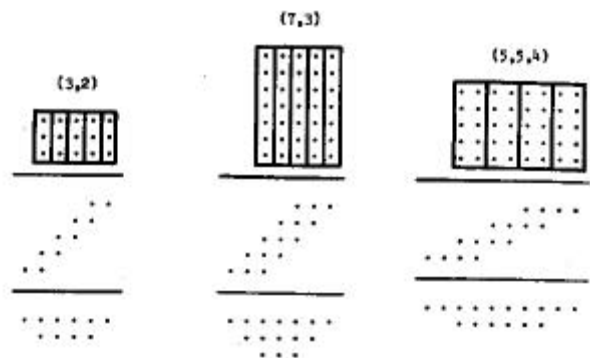


UC Berkeley EE241

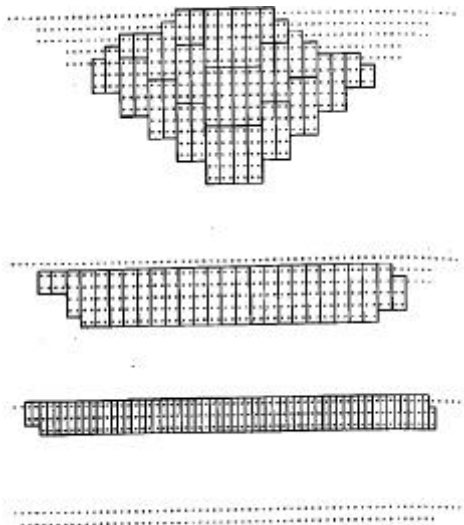B. Nikolic, J. Rabaey

Generalized Counters

32x32b
using (5,5,4)
with (3,2) in
the last stage




UC Berkeley EE241

B. Nikolic, J. Rabaey

4:2 Counters (Compressors)

4-2 carry-save module

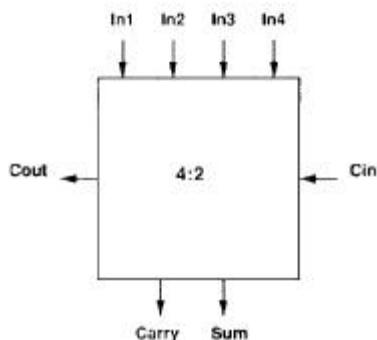

Weinberger, IBM J. ResDev 1/81
Santoro, Horowitz, JSSC 4/89

TRUTH TABLE FOR THE 4:2 ADDER
 n is number of inputs (from $In1$, $In2$, $In3$, $In4$) which = 1, C_{in} is the input carry from the C_{out} of the adjacent bit slice, C_{out} and carry both have weight 2, and sum has weight 1.

n	C_{in}	C_{out}	Carry	Sum
0	0	0	0	0
1	0	0	0	1
2	0	*	*	0
3	0	1	0	1
4	0	1	1	0
0	1	0	0	1
1	1	0	1	0
2	1	*	*	1
3	1	1	1	0
4	1	1	1	1

*Either C_{out} or Carry may be ONE for two or three inputs equal to 1 but NOT both.


C_{out} may NOT be a function of the C_{in} from the adjacent block or a ripple carry may occur.

UC Berkeley EE241

B. Nikolic, J. Rabaey


4:2 Compressors

Built of CSAs

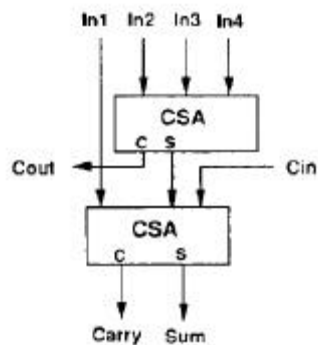


UC Berkeley EE241

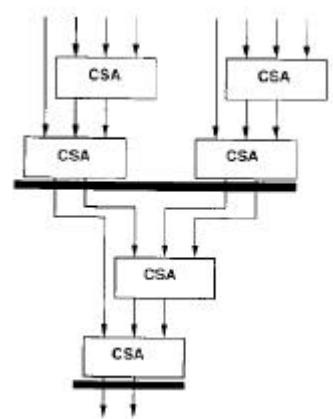Pipelined version compresses
8 partial products per cycle



B. Nikolic, J. Rabaey

4:2 Compressors

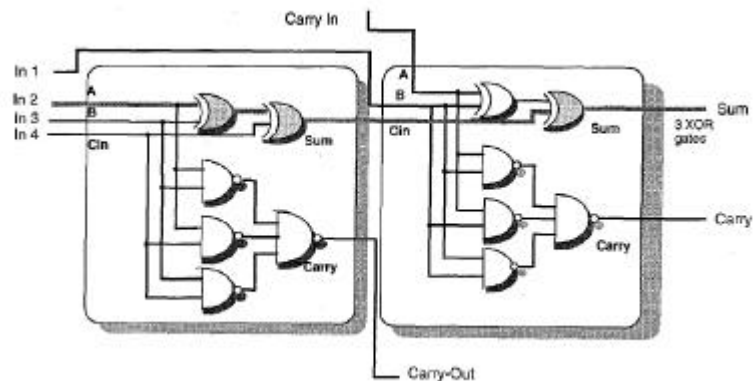


Interconnect can be more regular than in Wallace tree

UC Berkeley EE241

B. Nikolic, J. Rabaey

Three Dimensional Optimization

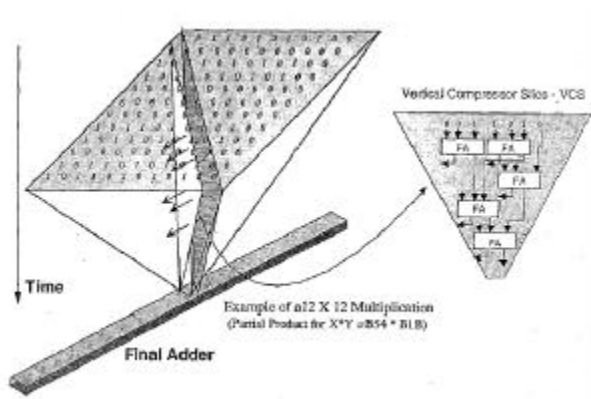


Oklobdzija, Vileger, Liu, Trans on Comp 3/96

UC Berkeley EE241

B. Nikolic, J. Rabaey


Vertical Slices in TDM

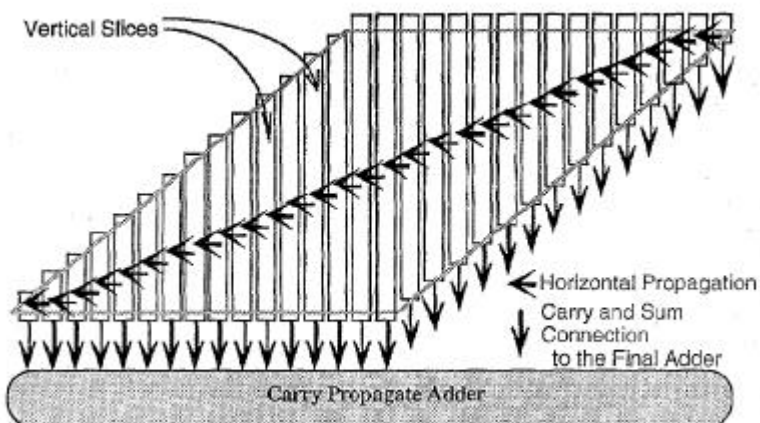

UC Berkeley EE241

B. Nikolic, J. Rabaey


Final Addition

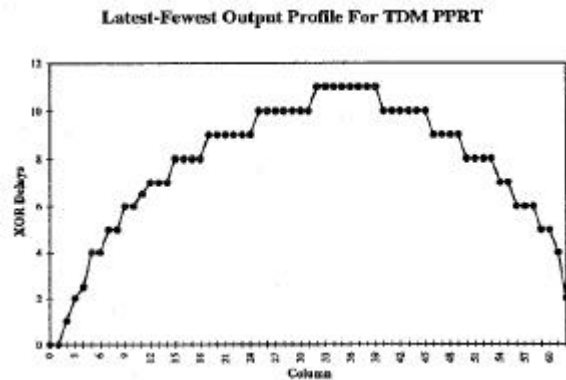

UC Berkeley EE241

B. Nikolic, J. Rabaey


Final Addition

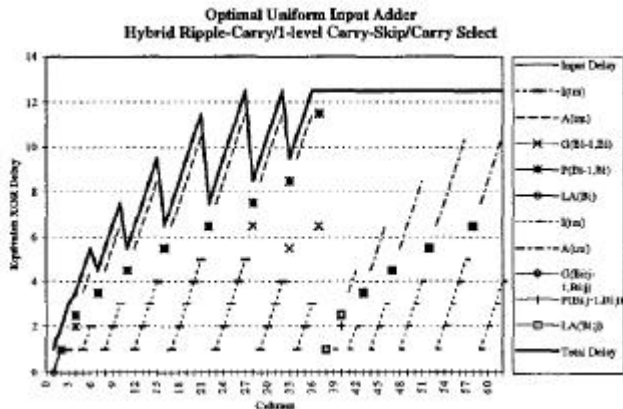


UC Berkeley EE241

B. Nikolic, J. Rabaey


Final Addition

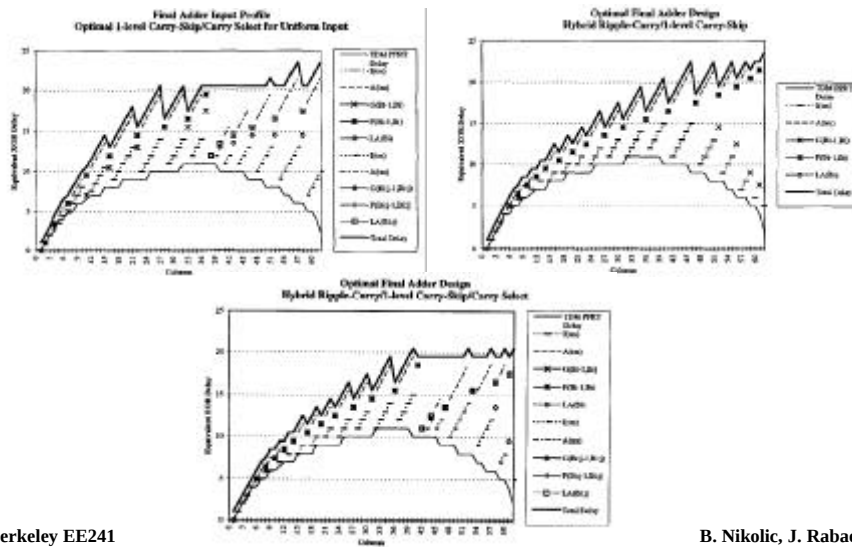

Example: CPL Multiplier

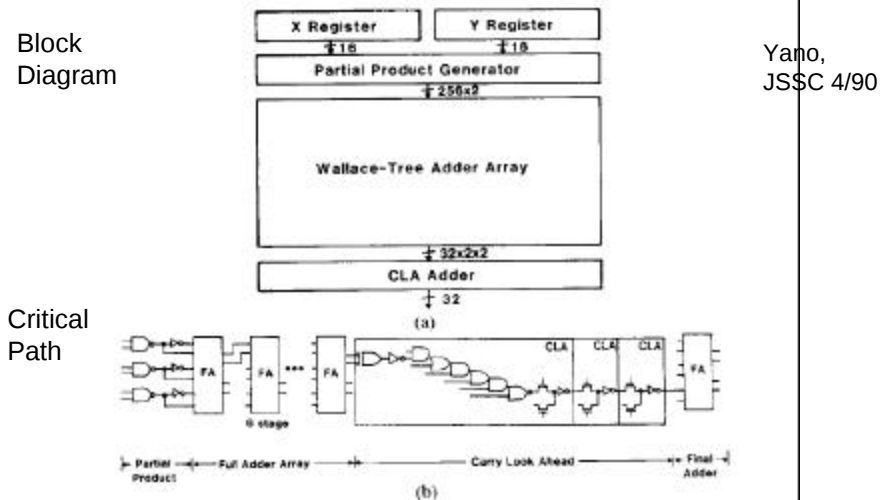


Example: DPL Multiplier

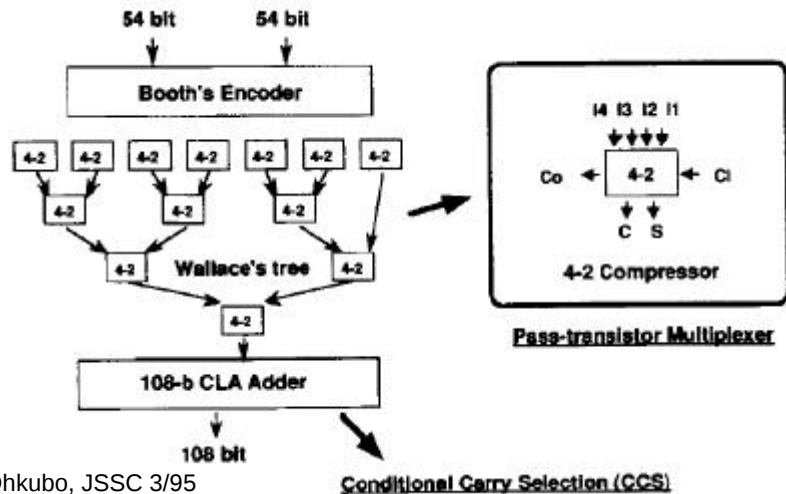

UC Berkeley EE241

B. Nikolic, J. Rabaey

Example: DPL Multiplier

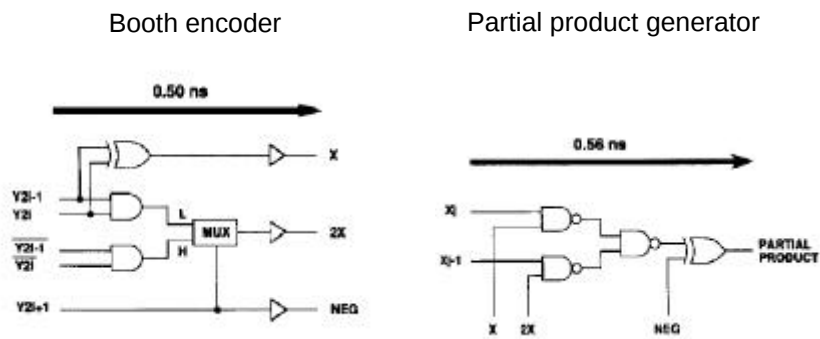


UC Berkeley EE241


B. Nikolic, J. Rabaey

Example: DPL Multiplier

FA-based 4:2

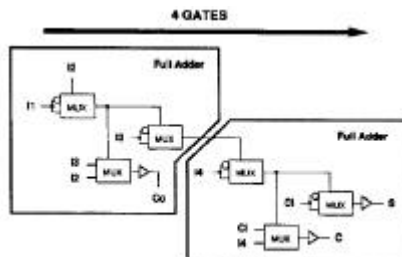

Modified 4:2

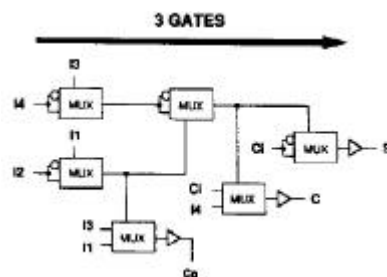


UC Berkeley EE241

B. Nikolic, J. Rabaey

Example: DPL Multiplier

Tree construction

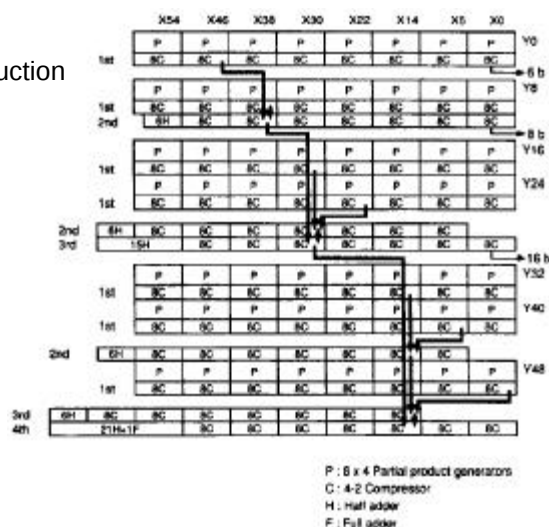


UC Berkeley EE241

B. Nikolic, J. Rabaey

Example: DPL Multiplier


Final adder

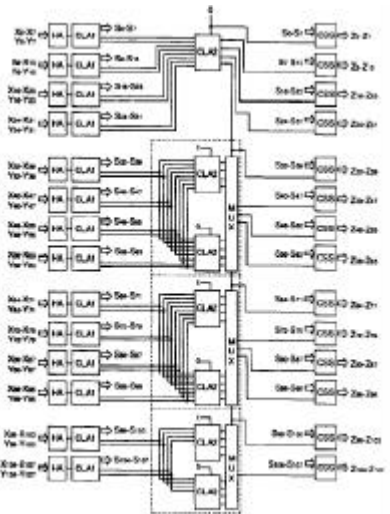

UC Berkeley EE241

B. Nikolic, J. Rabaey

Regularly Structured Tree

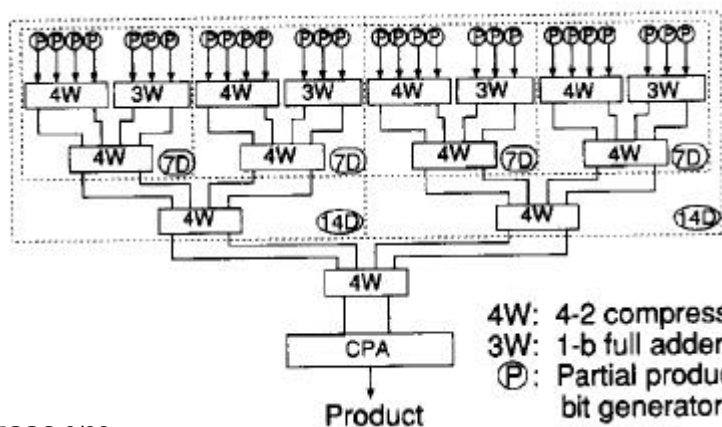


Goto, JSSC 9/92

UC Berkeley EE241

B. Nikolic, J. Rabaey


Regularly Structured Tree

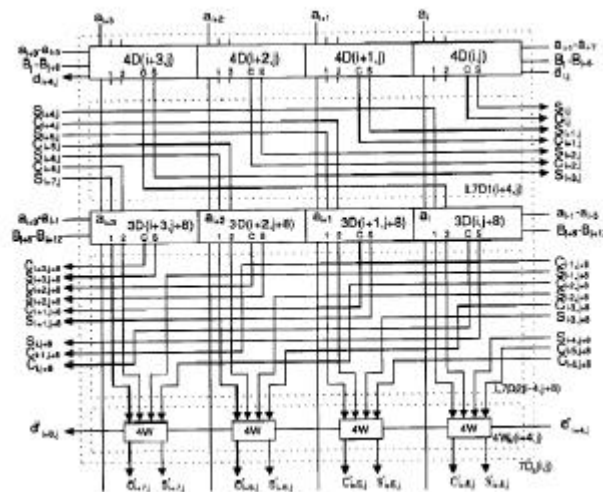

UC Berkeley EE241

B. Nikolic, J. Rabaey


Regularly Structured Tree

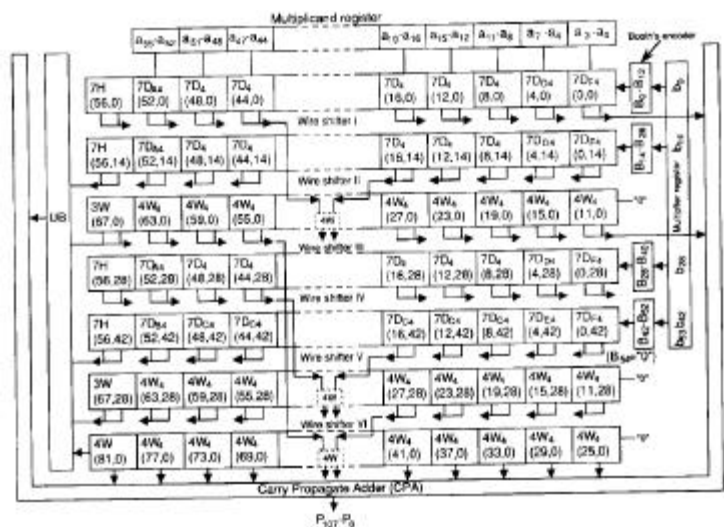

UC Berkeley EE241

B. Nikolic, J. Rabaey

Regularly Structured Tree

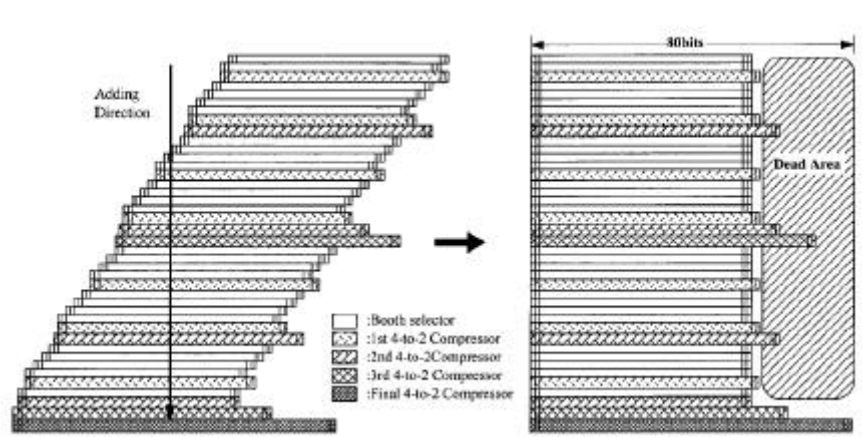


Itoh, JSSC 2/01

UC Berkeley EE241

B. Nikolic, J. Rabaey


Regularly Structured Tree

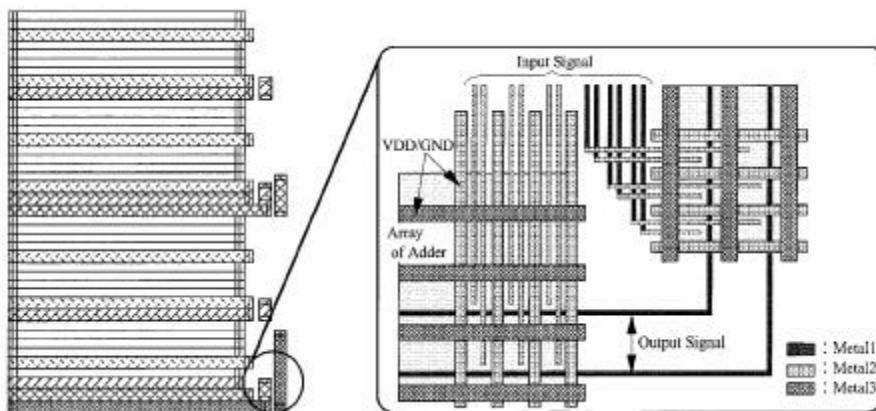

UC Berkeley EE241

B. Nikolic, J. Rabaey

Regularly Structured Tree

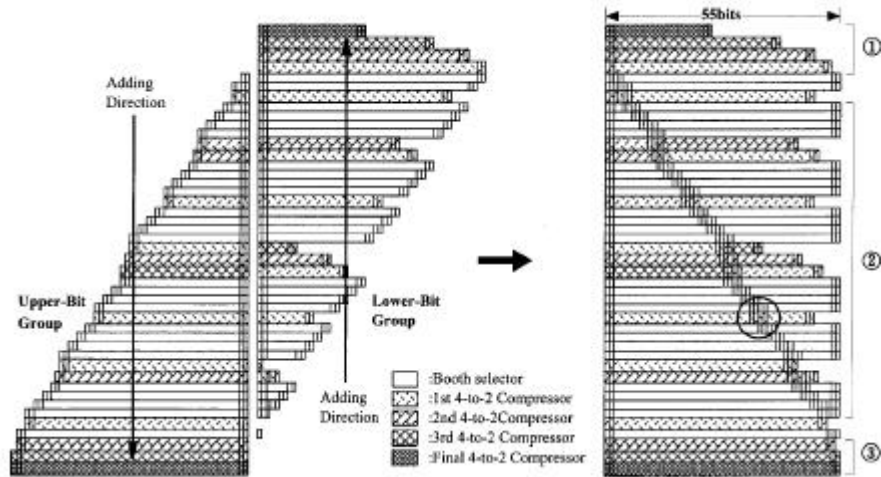

UC Berkeley EE241

B. Nikolic, J. Rabaey