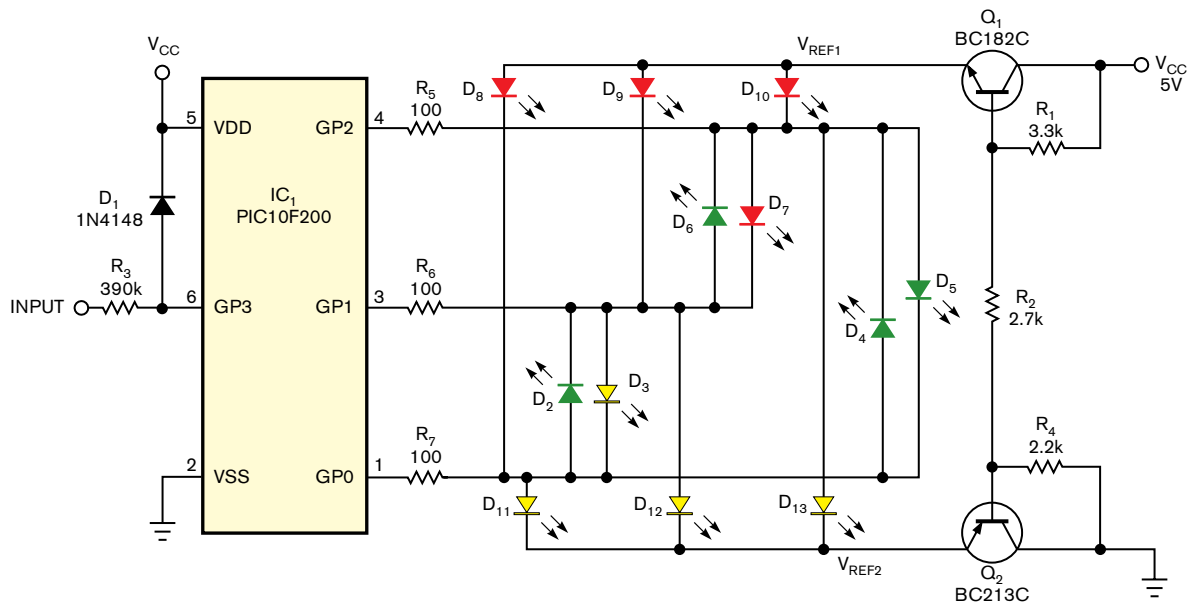




NOTE: LEDs ARE PANASONIC SSG LN224 SERIES (RED), LN324 SERIES (GREEN), AND LN424 SERIES (YELLOW).

Figure 1 A PIC microprocessor and a 12-LED bar-graph display form a simple tachometer circuit. (The decoupling capacitors are not shown.)