

A grayscale photograph of a modern, single-story office building with a large glass facade. The building has a prominent sign that reads "LINEAR" and "WORLD HEADQUARTERS". The address "720" is visible on a vertical sign. In the foreground, there is a landscaped area with low-lying plants and a paved road. Two cars are parked in the distance.

**Buck-Boost Converter
Achieving up to 97% Efficiency
at 12V/5A from 4-32V Input**


Linear Technology Corporation

Where are the V_{in} , $\min < V_o < V_{in}$, $\max$ Applications


- **Automotive:**
 - $V_{in}=8-15V$, $V_o=12V$
- **Telecom:**
 - $V_{in}=36-72V$, $V_o=48V$
- **Portable Equipments**
 - 1-4 cell Li-ion powered



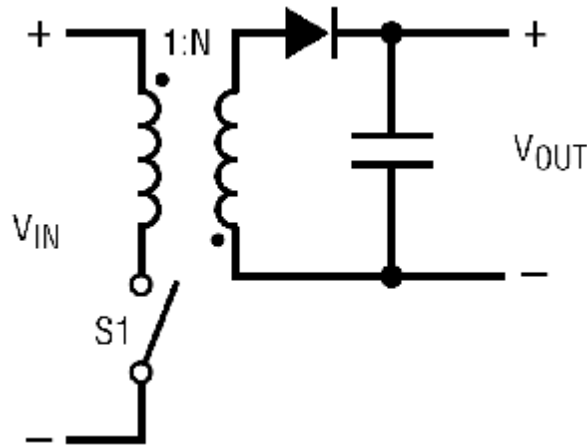Common Topologies for Buck-Boost Function



Flyback

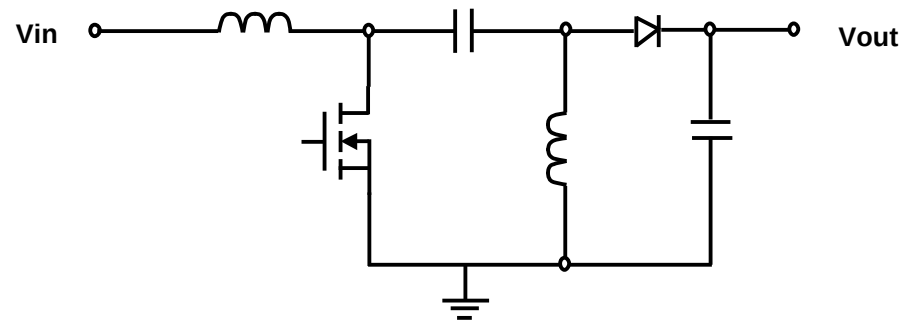


SEPIC

- 2 inductors or a transformer
- High current stresses on switch
- Max achieved efficiency 90-92%

LTC3780-based Single Inductor Buck-Boost Converter

4-SWITCH BUCK-BOOST
TOPOLOGY YIELDS HIGH
EFFICIENCY AT HIGH POWER

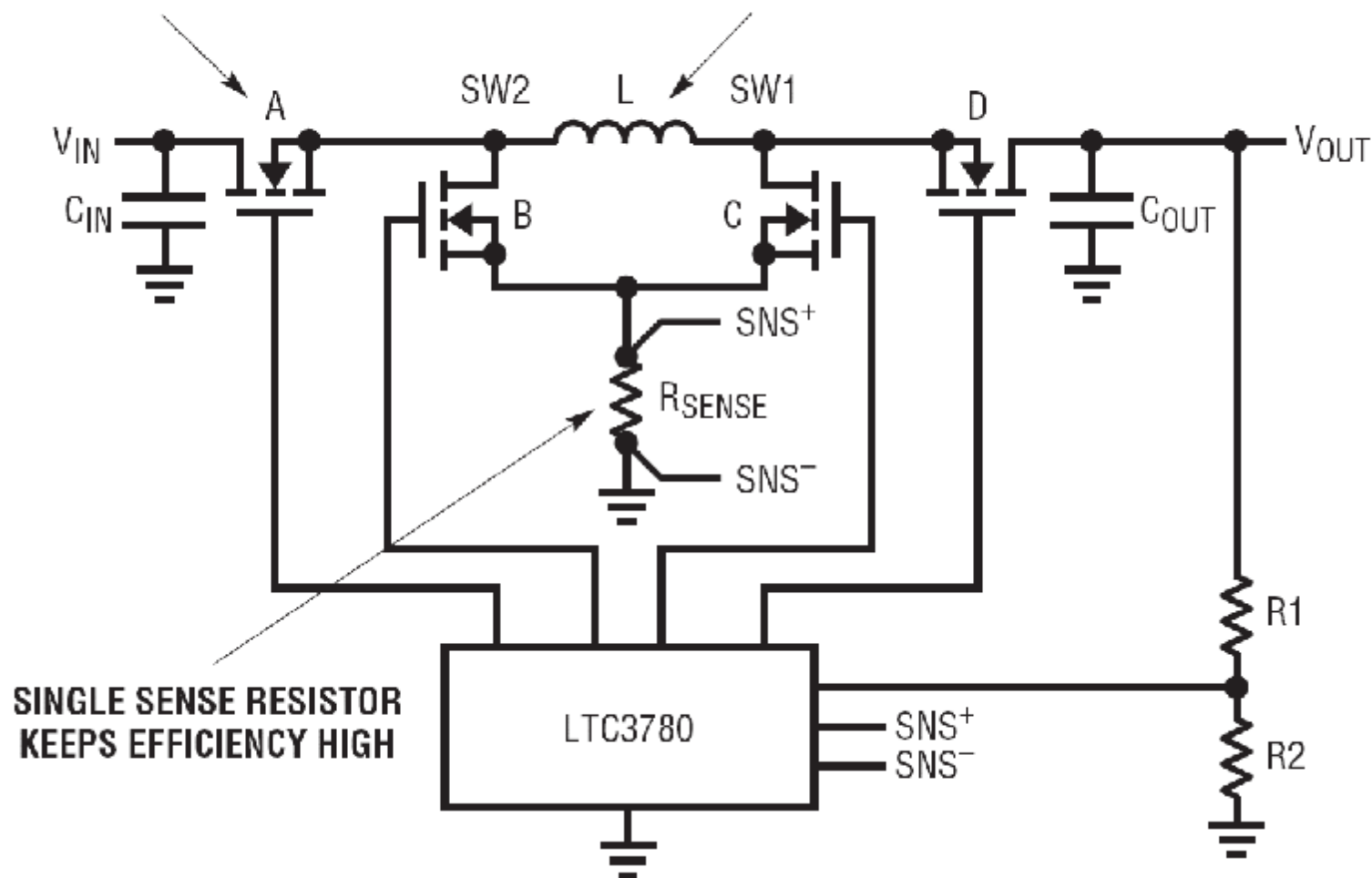ONLY ONE INDUCTOR SIMPLIFIES
LAYOUT AND SAVES SPACE




SINGLE SENSE RESISTOR
KEEPS EFFICIENCY HIGH


What does the Buck-Boost Achieve?

- Up to 97% efficiency at 12V/5A
- High light load efficiency
- Wide input range 8:1 (4V to 32V)
- Small single inductor
- Small converter size (2.5 in² PCB area)
- 1% output voltage accuracy
- Excellent load/line transient responses
- Internal LDO for MOSFET drive
- Over voltage/current protection
- Soft-start


The 12V/5A Buck-Boost Converter

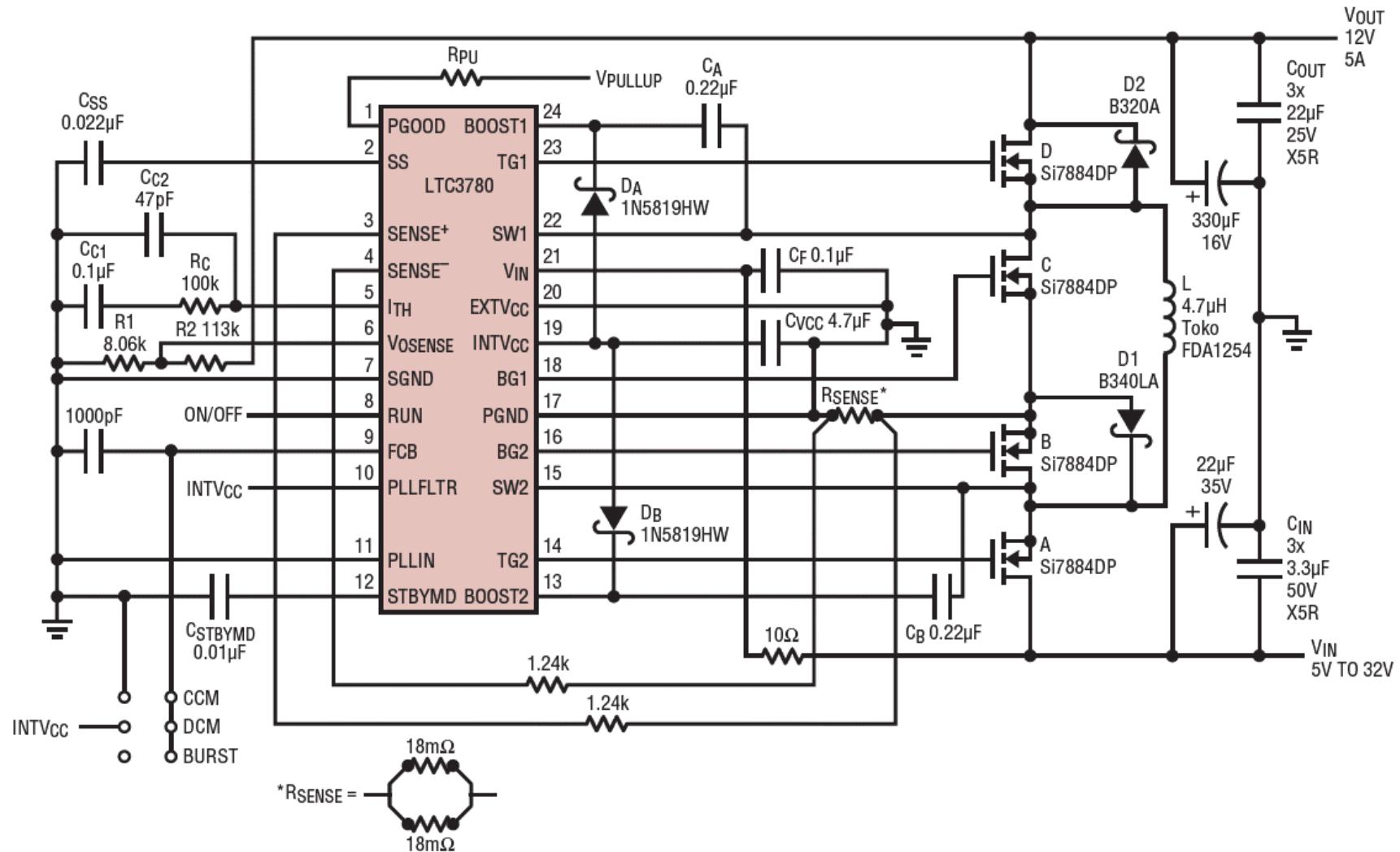


Size and Efficiency

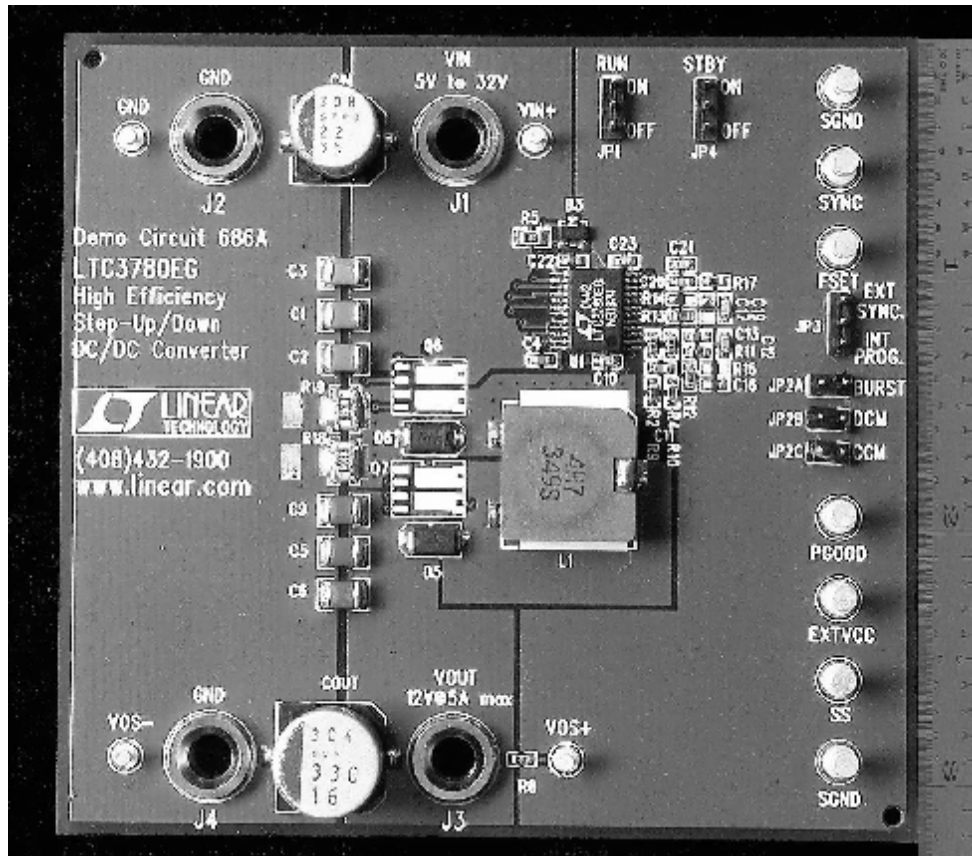

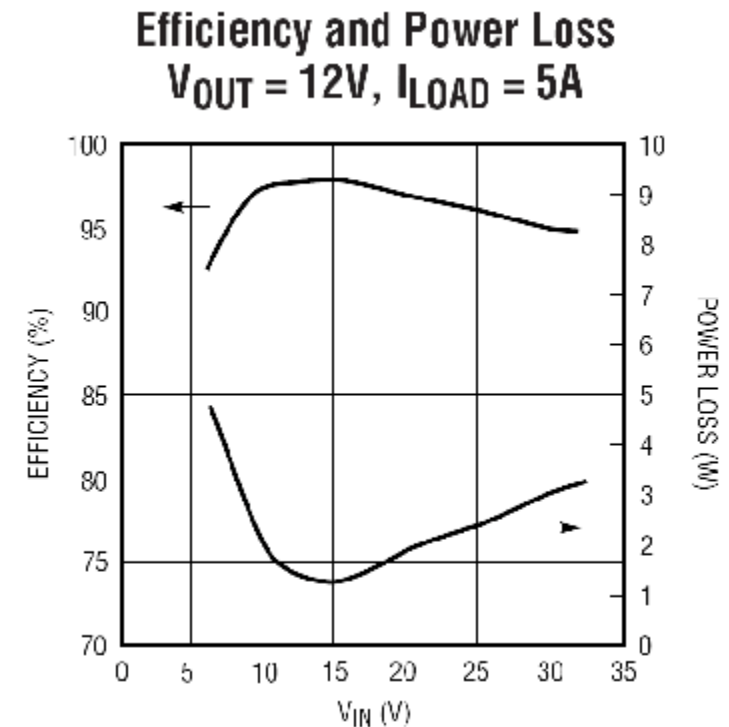
- $<2.5 \text{ in}^2$ total PCB area
- 97% Efficiency at 12V/5A




Load and Line Transient Responses

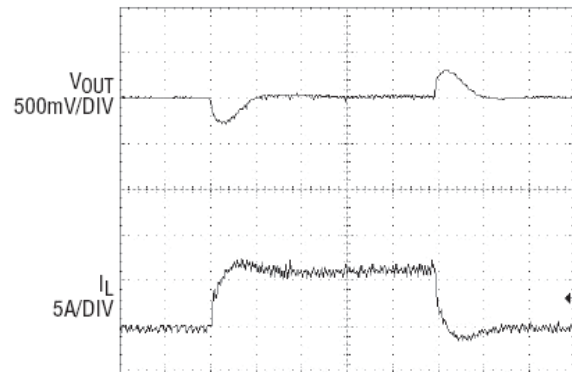

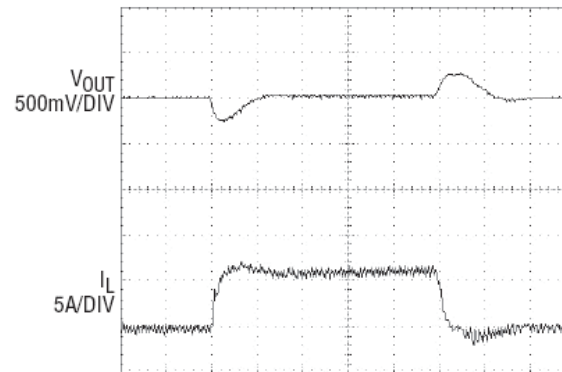$V_{IN} = 12V$
 $V_{OUT} = 12V$
 LOAD STEP: 0A TO 5A
 CONTINUOUS MODE




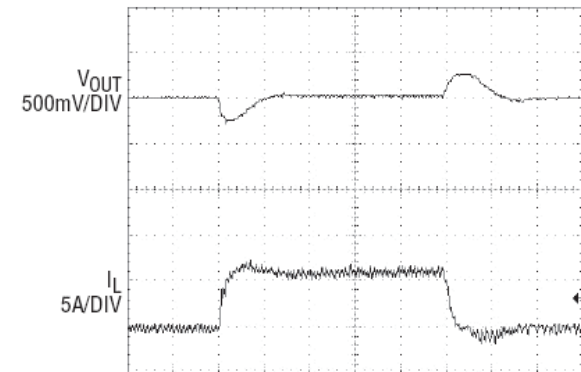$V_{IN} = 12V$
 $V_{OUT} = 12V$
 LOAD STEP: 0A TO 5A
 DISCONTINUOUS CURRENT MODE




$V_{IN} = 12V$
 $V_{OUT} = 12V$
 LOAD STEP: 0A TO 5A
 BURST MODE OPERATION

Line Transient

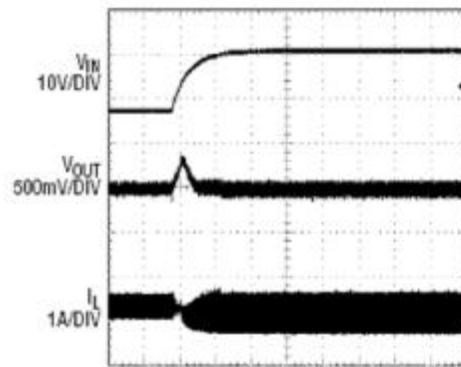



$V_{OUT} = 12V$
 $I_{LOAD} = 1A$
 V_{IN} STEP: 7V TO 20V
 CONTINUOUS MODE

Line Transient

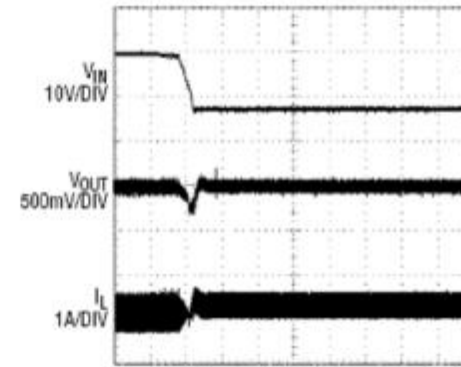

$V_{OUT} = 12V$
 $I_{LOAD} = 1A$
 V_{IN} STEP: 20V TO 7V
 CONTINUOUS MODE

SEPIC vs. Buck-Boost

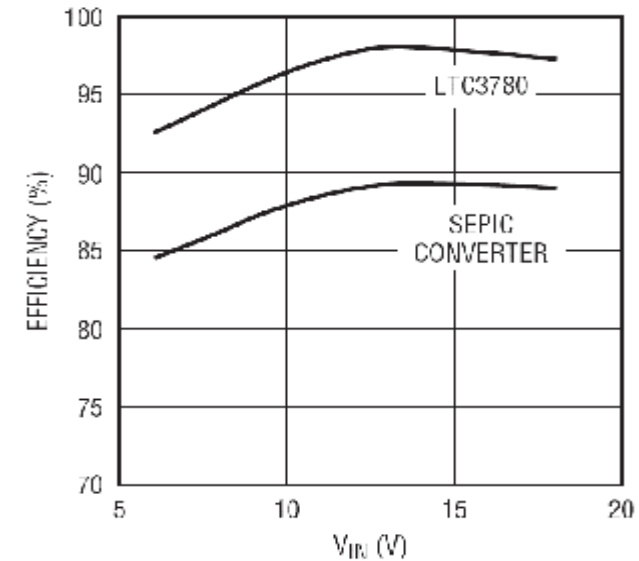
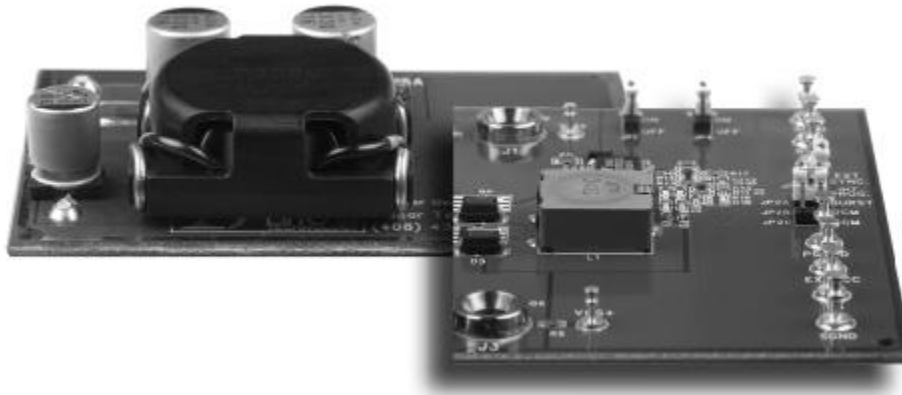


- 2X inductor foot print and height
- Max 90% efficiency vs. 97%

How Does LTC3780 Achieve these?

More Details


How Does LTC3780 Achieve these?

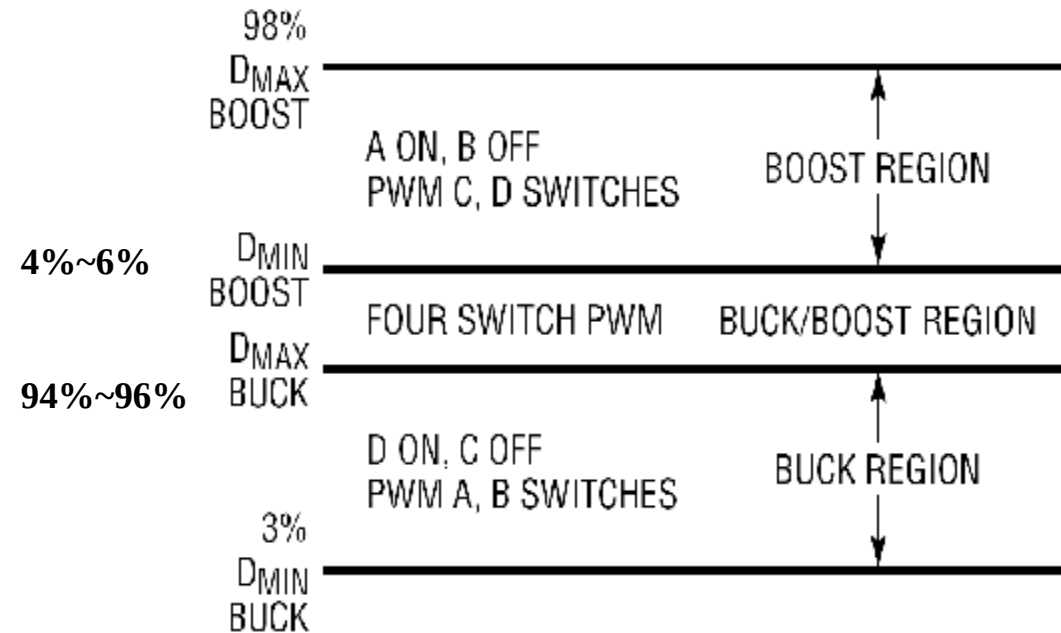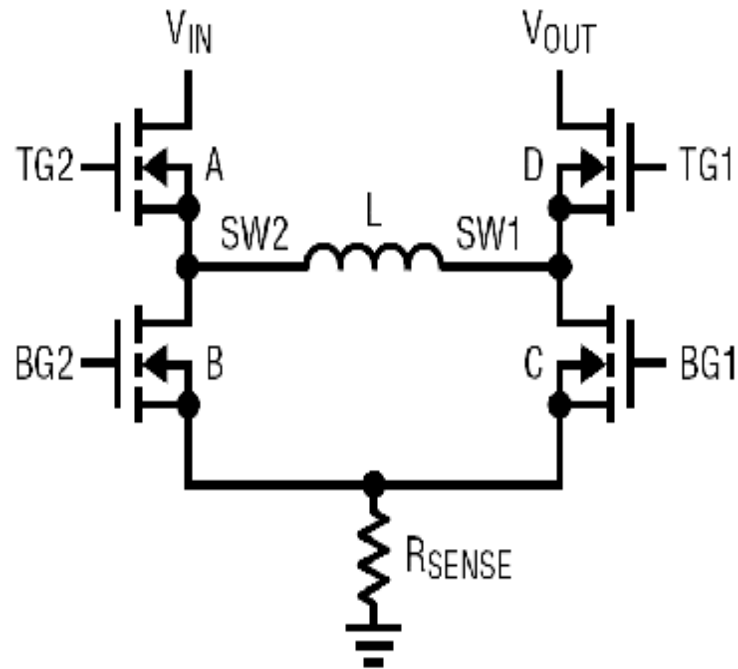

- $D_{\text{min-BOOST}} = D_{\text{BUCK-BOOST}}$
- $D_{\text{max_BUCK}} = (1 - D_{\text{BUCK-BOOST}})$
- $D_{\text{BUCK-BOOST}} = 200\text{ns} \cdot F_s$

Constant Frequency Buck and Boost Operation


Buck Mode ($V_{in} > V_o$)

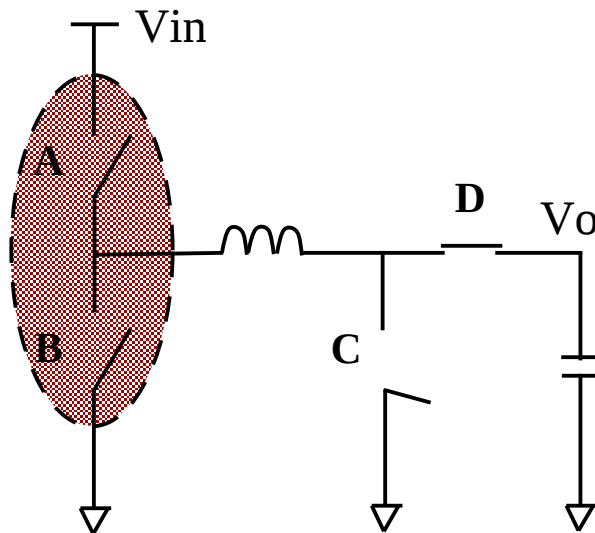

- **Valley Current Control**

(D always on, C always off
A and B controlled as buck switch
D shut off at zero load)

Boost Mode ($V_{in} < V_o$)

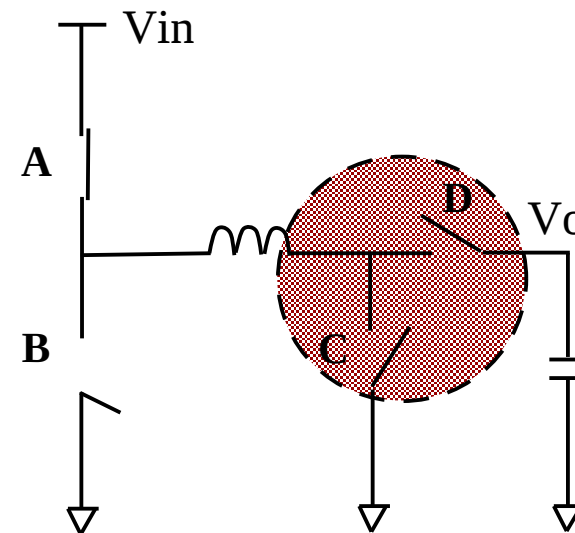


- **Peak Current Control**

(A always on, B always off
C and D controlled as boost switch
D shut off at zero load)


Valley Current Control vs. Peak Current Control

- **Valley-Current Control (Buck)**

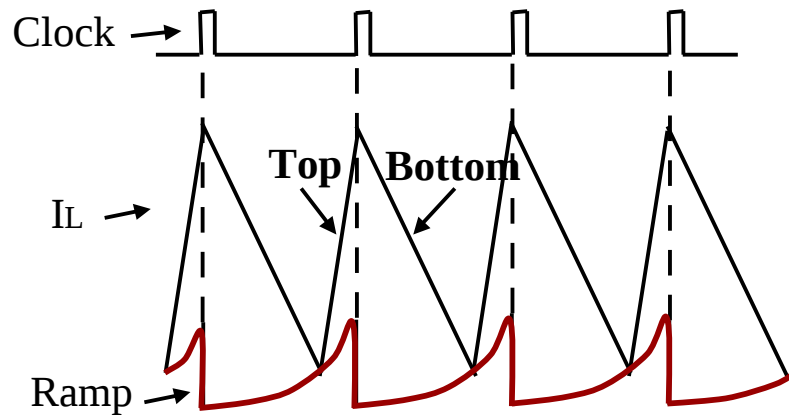


- **$D < 0.5$** ;
- **Ramp** needed;
- **Clock** turn on bottom FETs;

- **Peak-Current Control (Boost)**

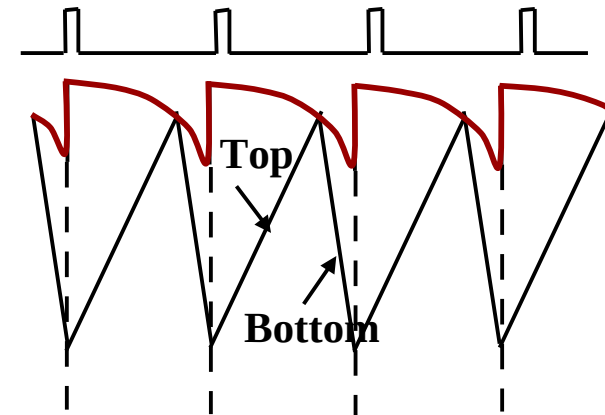

- **$D > 0.5$** ;
- **Ramp** needed;
- **Clock** turn on top FETs;

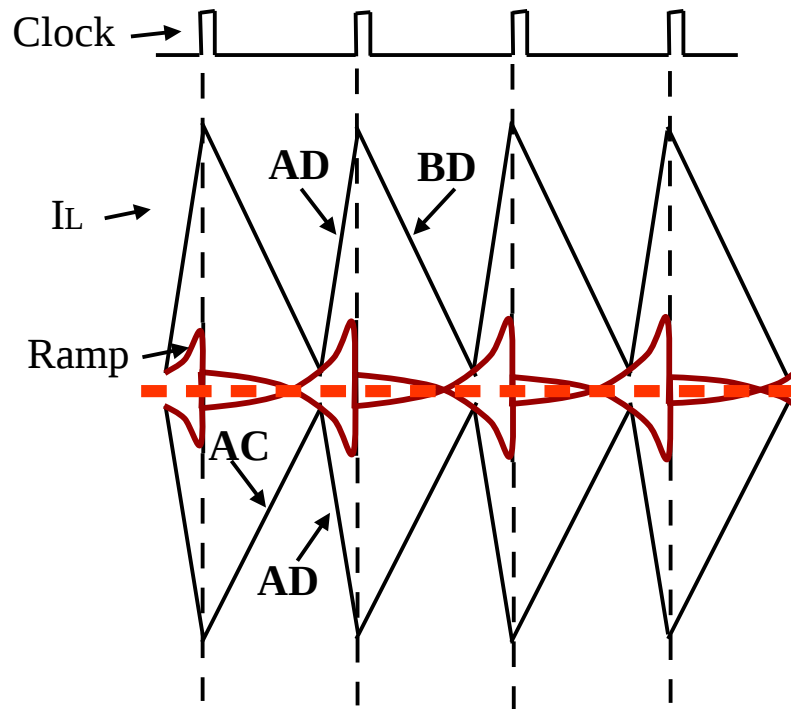Valley-Peak Current Mode Control Transitions




- **Valley-Current Control (Buck)**


$V_{in} > V_o$, switch AD and BD

- **Peak-Current Control (Boost)**

$V_{in} < V_o$, switch AC and AD

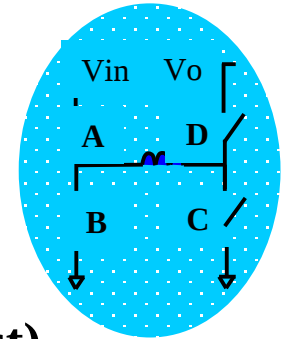


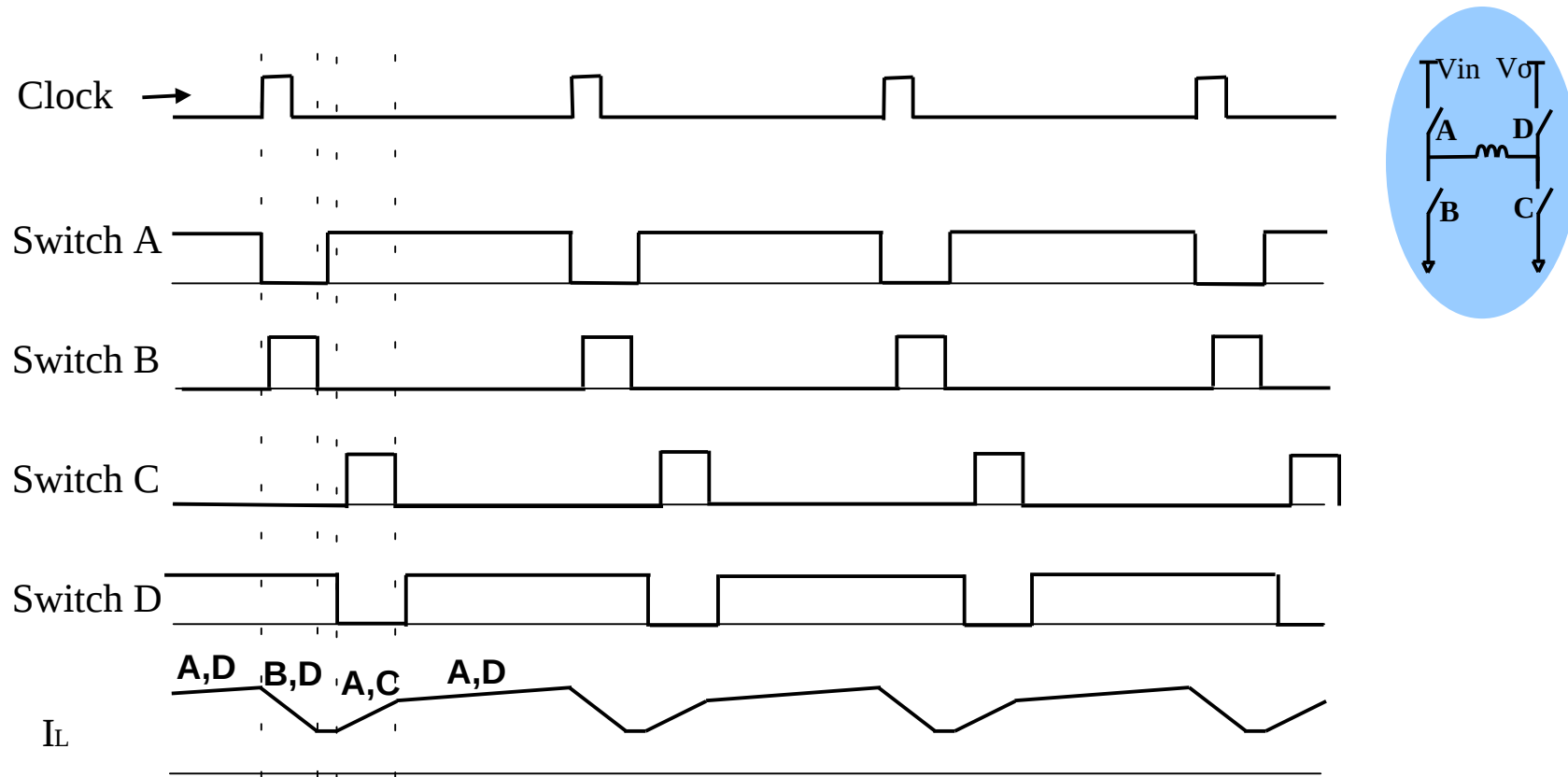Operation During Transition ($V_{in}^3 V_o$)



Cycle start with switch B & D turn On

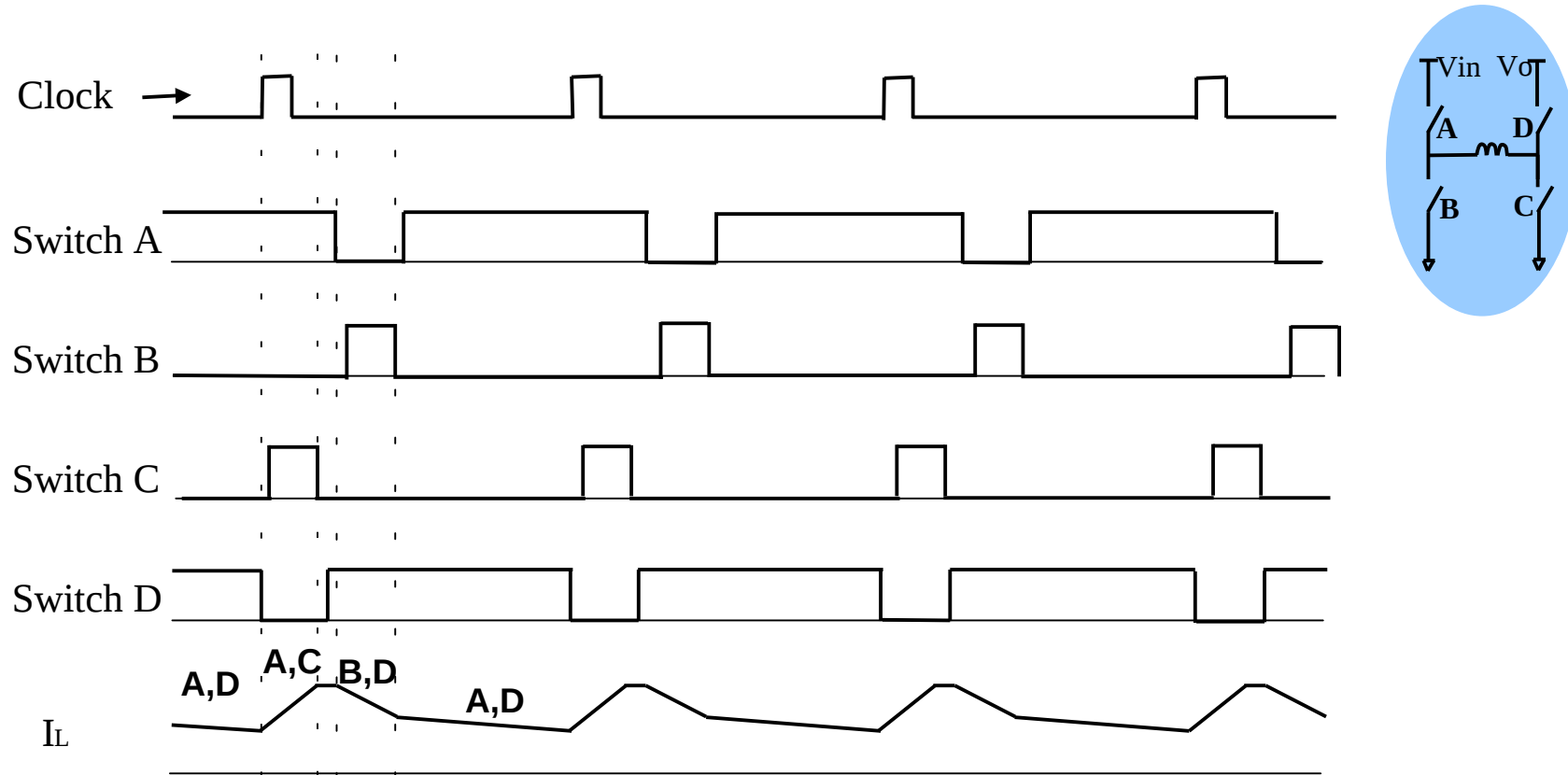Operation During Transition ($V_{in} \neq V_o$)



Cycle start with switch A & C turn On

For the battery powered device

Light load efficiency is critical

What does LTC3780 have?

3 operation modes





Achieving Light Load Efficiency

Multi Operation Modes


FCB Pin	BUCK Mode	BOOST Mode
0V to 0.75V	Force continuous mode	Force continuous mode
0.85 to 5.0	Skip cycle mode	Burst mode
> 5.3	DCM with constant freq	DCM with constant freq

Continuous Conduction Mode


($V_{FCB} = 0$, $V_{OUT} = 12V$)

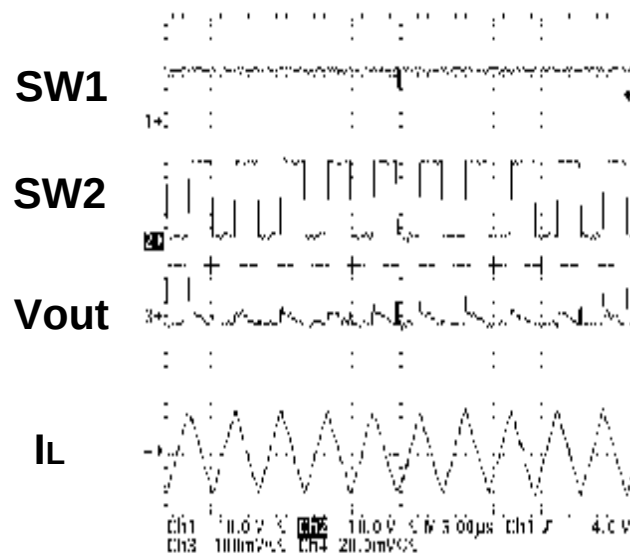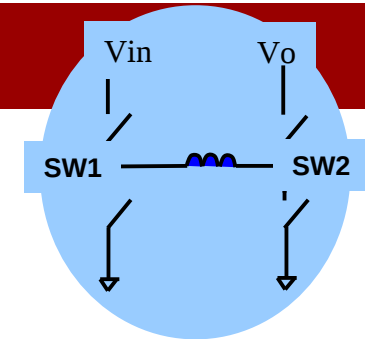

$V_{IN} = 6V$

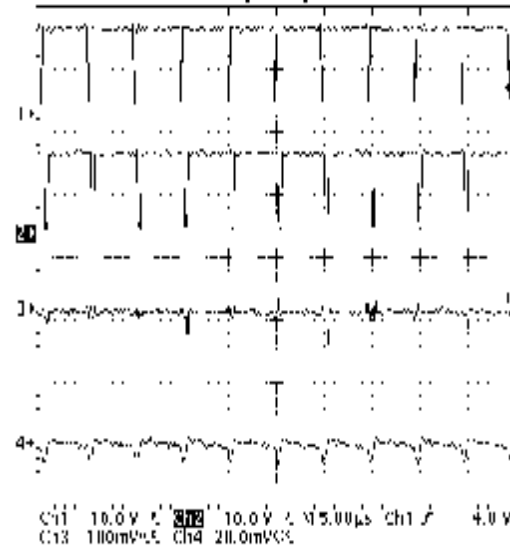



$V_{IN} = 12V$

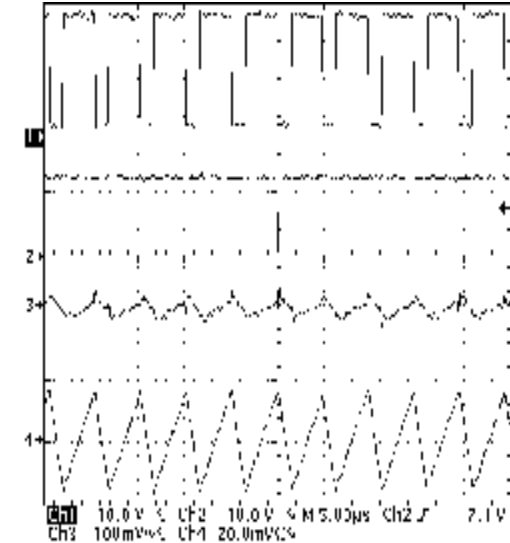


$V_{IN} = 18V$

Burst, SC Mode


(V_{FCB} floating, $V_{OUT} = 12V$)

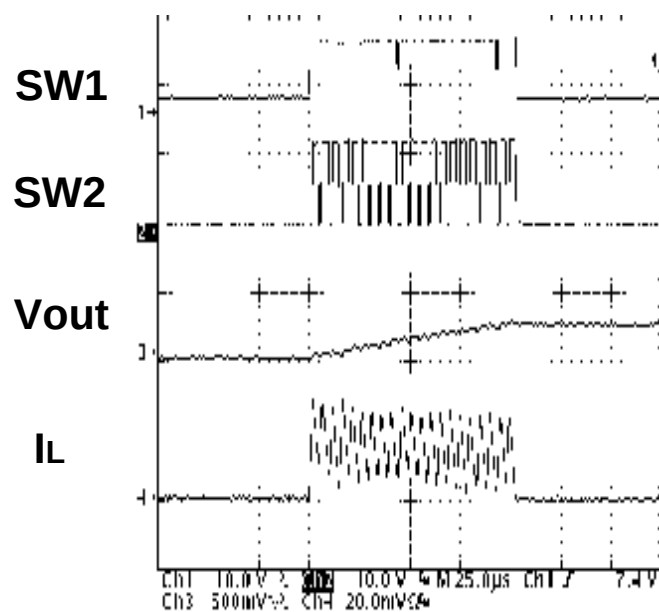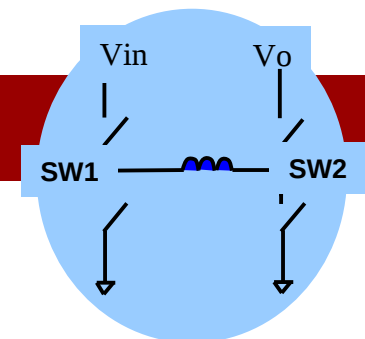

$V_{IN} = 6V$

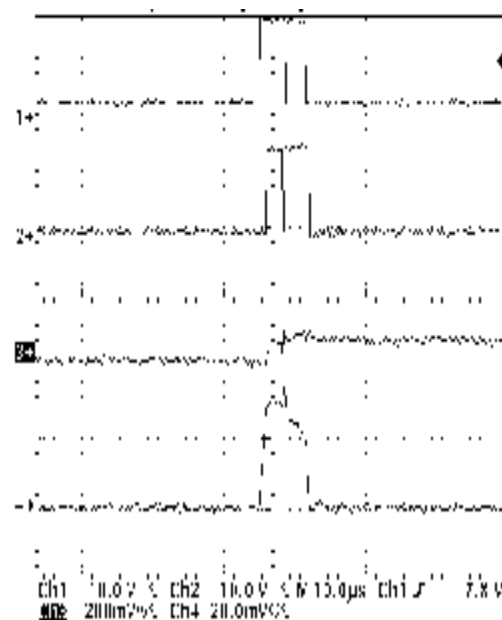


$V_{IN} = 12V$

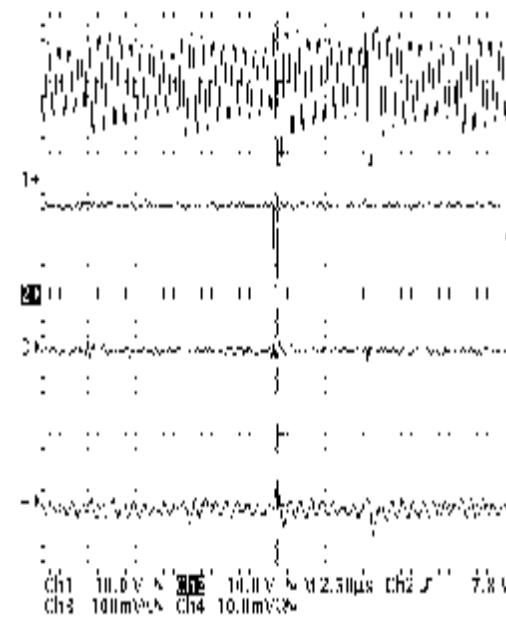

$V_{IN} = 18V$

DCM Mode

($V_{FCB} = 6V$, $V_{OUT} = 12V$)

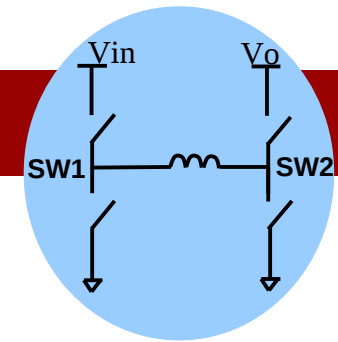


SW1


SW2

Vout


IL

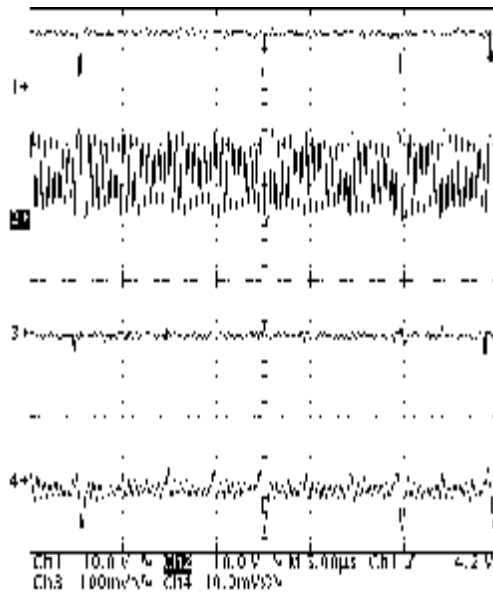

$V_{IN}=6V$

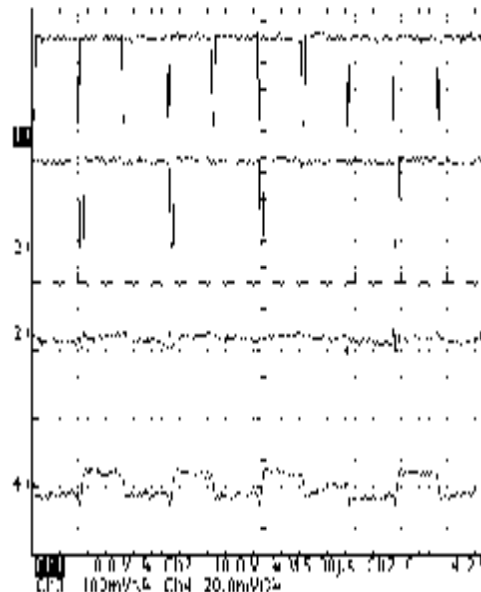


$V_{IN}=12V$

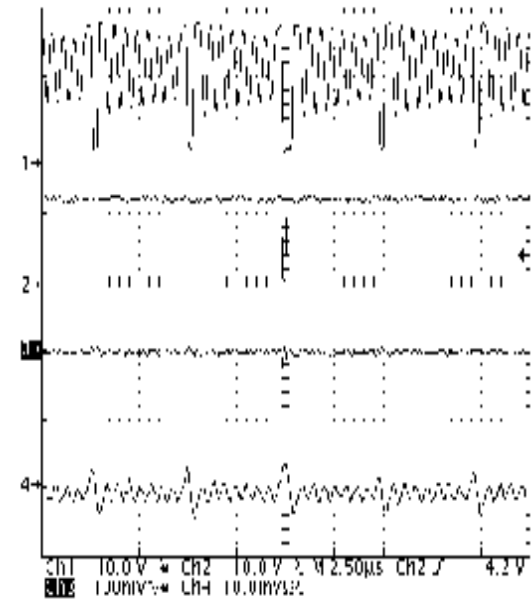


$V_{IN}=18V$

Efficiency at Different Operation Modes


($V_{OUT} = 12V$, $F_s = 200kHz$)

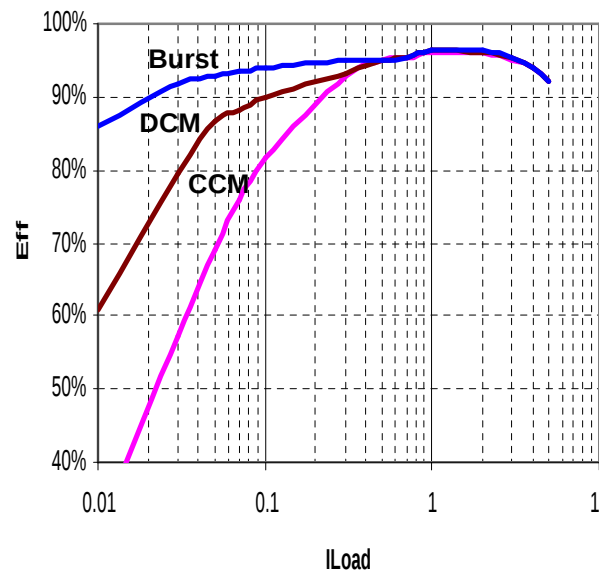

$V_{IN} = 6V$


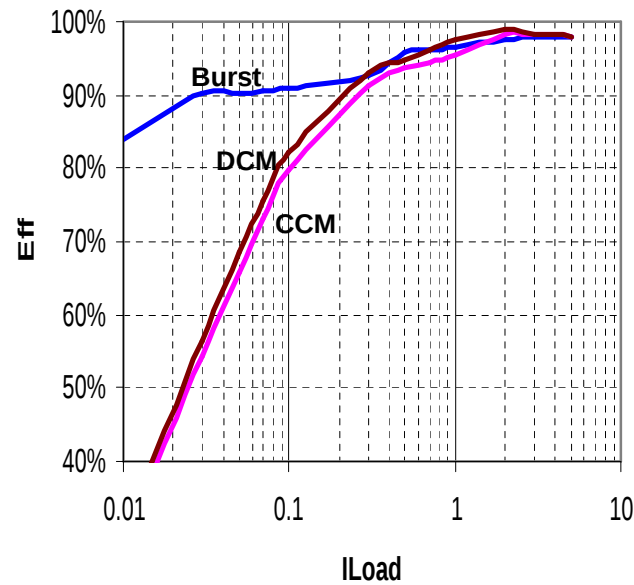


$V_{IN} = 12V$

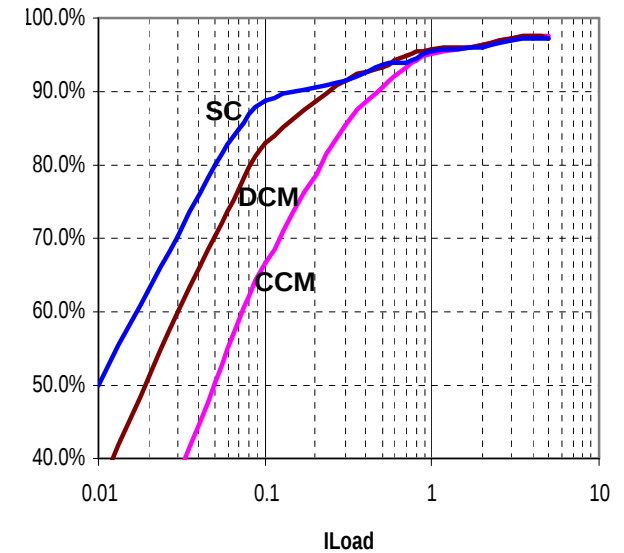

$V_{IN} = 18V$

Extending the Operation Voltage Range

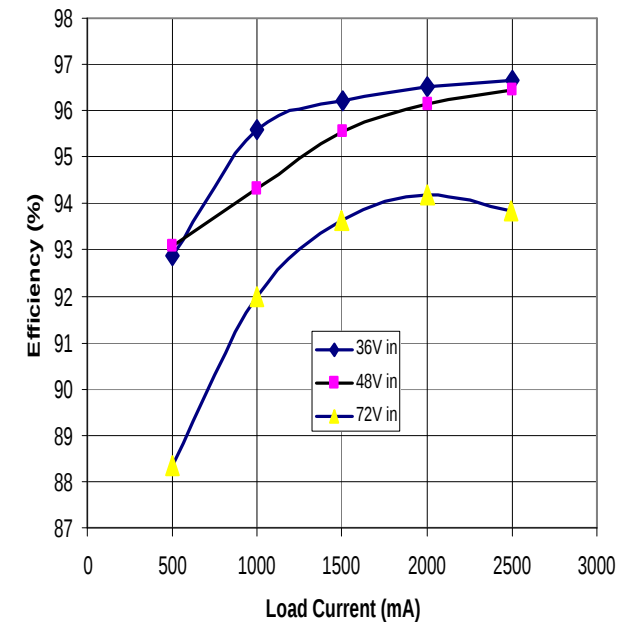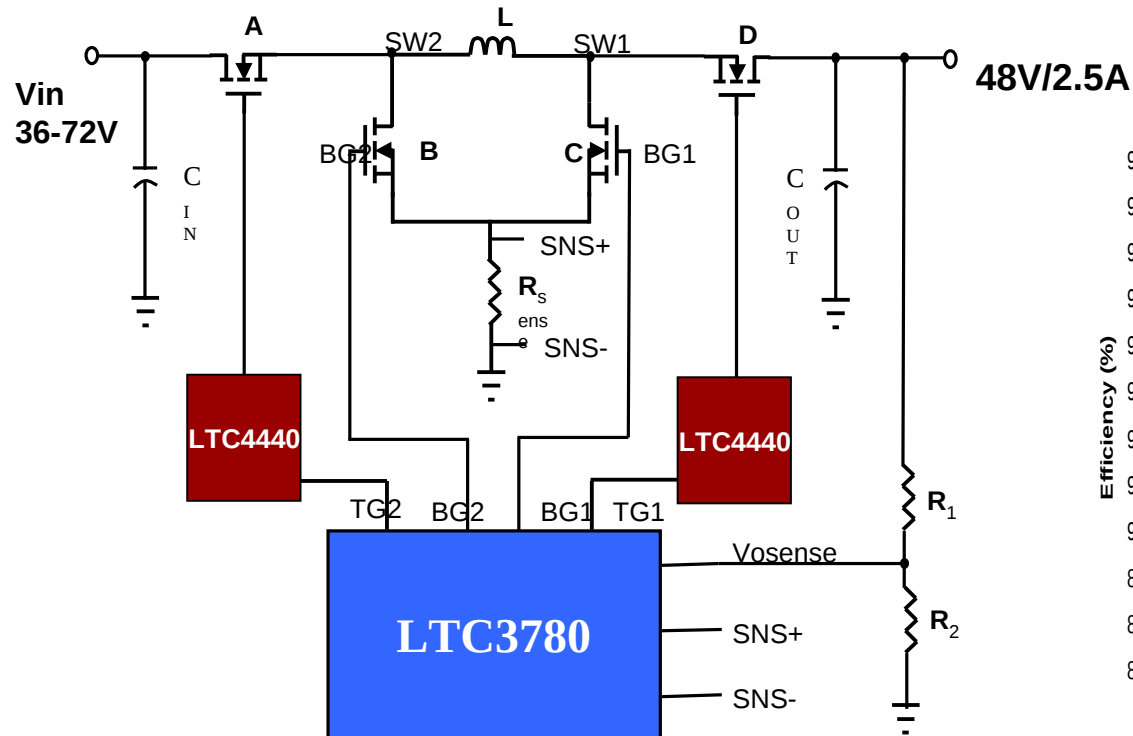


Efficiency exceeds 92% most of time

Max efficiency 96.5%

Summary

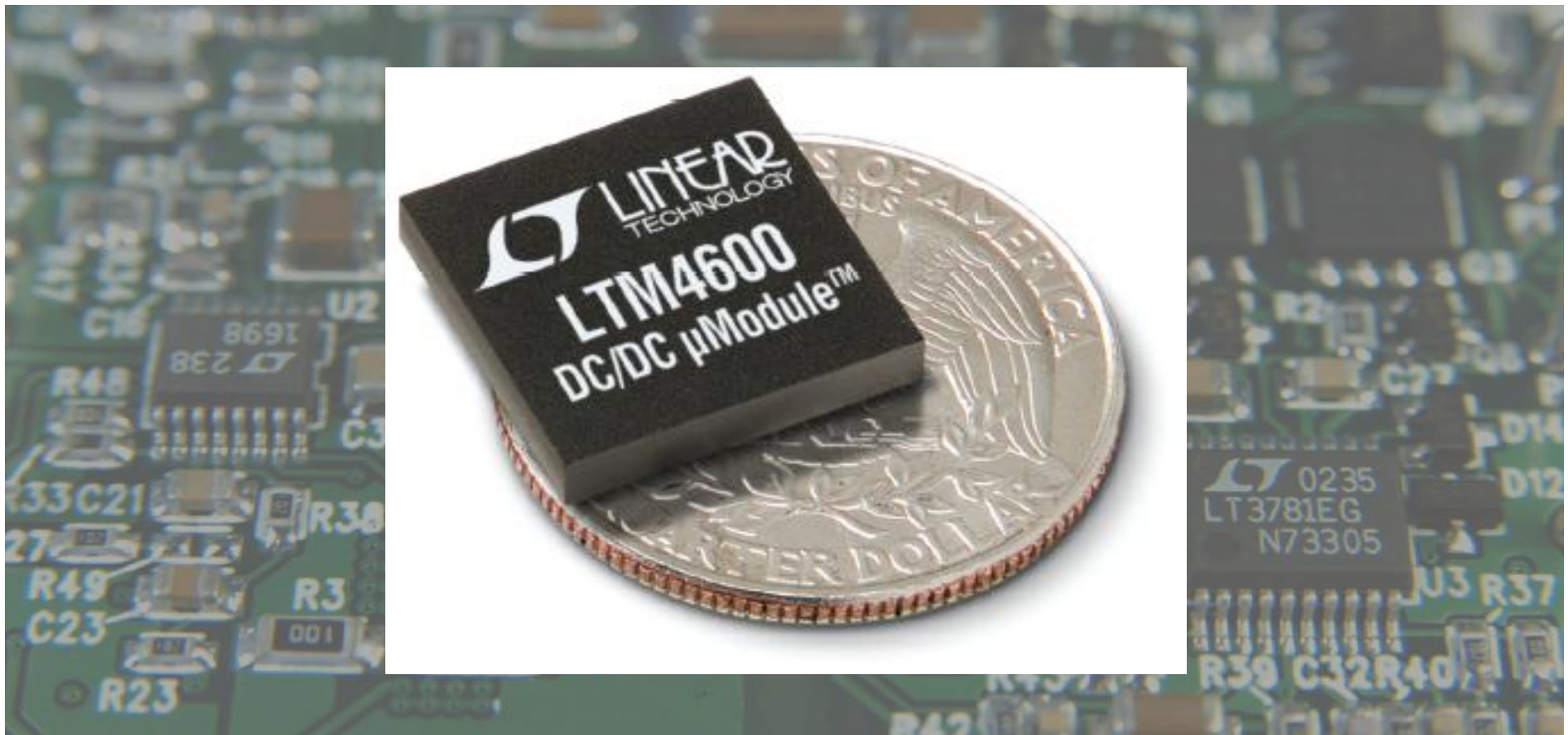- **LTC3780 based Buck-Boost Converter achieves over 97% for 12V/5A output, 5-8% better than a comparable SEPIC converter.**
- **It has wide input range (8:1)**
- **It has all the desirable features in a DC/DC converter**
- **With external driver(s), the operation voltage range can be greatly extended**
- **An excellent converter for automotive, telecom, and portable applications**





LTM[®]4600

10A Step Down DC/DC μModule[™]

LTM4600 μ Module


- μ Module™:

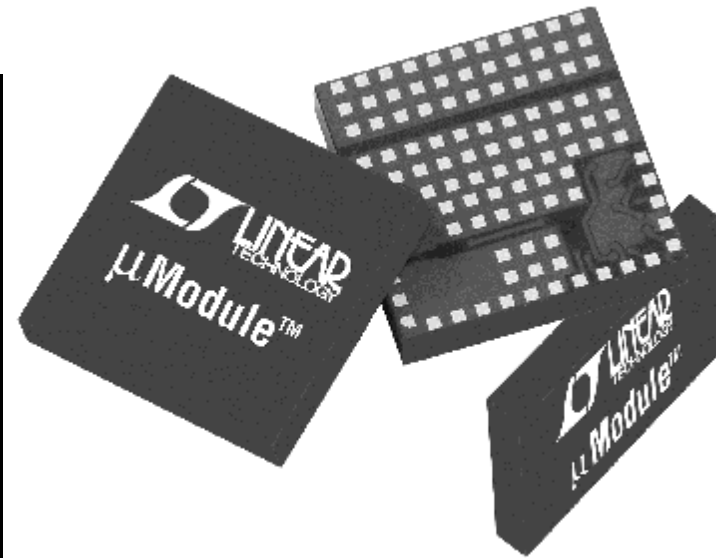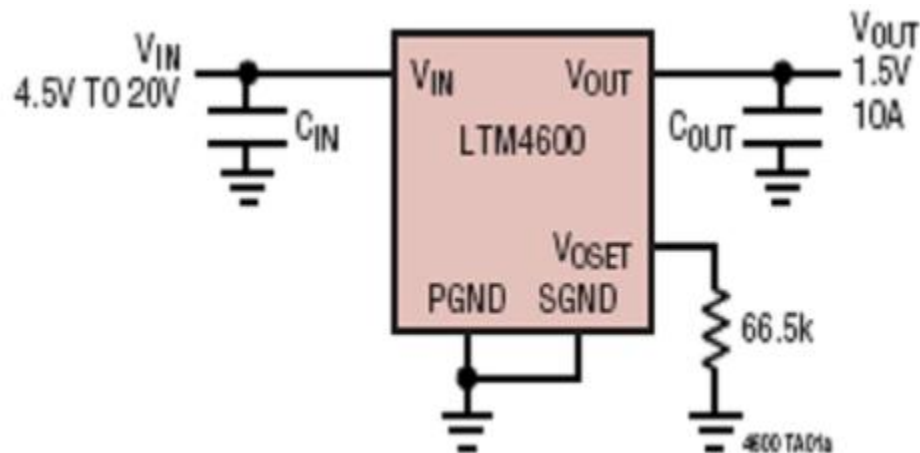

- Complete step down switch mode power supply
- As easy to design in as a linear regulator

LTM4600 Complete, Quick & Ready

- Discrete Design

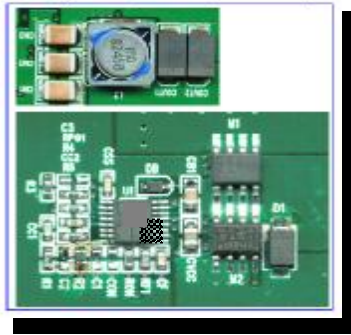

20+ Components +
Design
Simulation
Layout
Debug

Expert Power Supply Designer

Purchase +
Assembly
Debug

Time-to-Market, Effort, \$\$




- LTM4600 μ Module



- 40%-50% smaller solution
- Significant reduction in input/output capacitor size
- High power density
- Easy to use

LTM4600 What's Inside?

Ö All Linear Technology Silicon

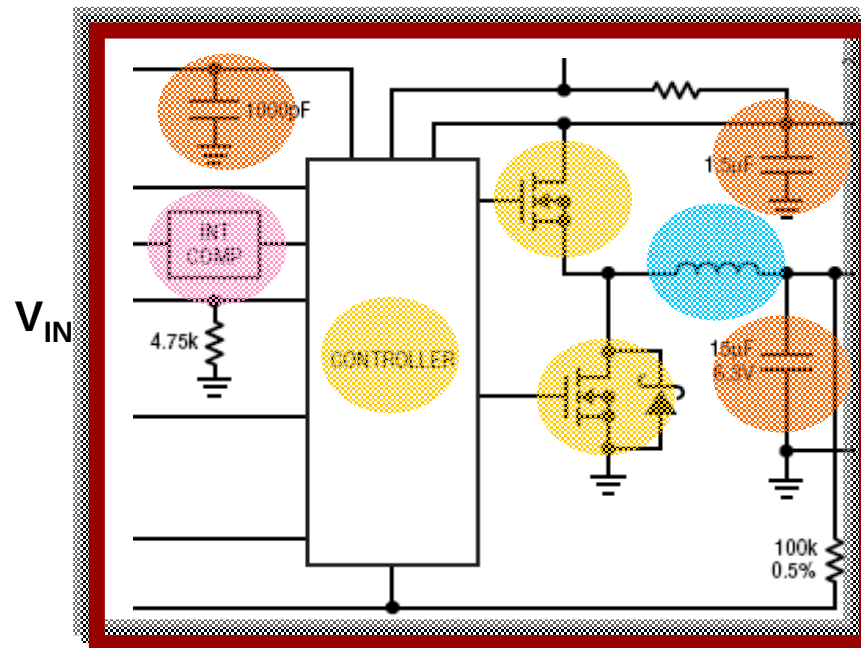

Simplified Block Diagram

- Linear Technology's DC/DC **Controller** & power **MOSFETs**
 - On-board **Inductor**
 - On-board bypass **Capacitors**
 - On-board **Compensation**
- F=800kHz**


LTM4600 10A Step Down DC/DC Converter

- **Features**

- Vin: 4.5V to 20V (28V for HV product)
- Vout: 0.6V to 5V, adjustable with single resistor
- -40° C to +85° C ambient operating temperature range
- Up to 92% efficiency
- 1.5% output regulation over temperature
- Ultra-fast transient response
- Integrated fault protection (OV/OC/UV)
- Integrated soft start
 - Adjustable with capacitor
- 15mm x 15mm x 2.8mm


Land Grid Array (LGA) package

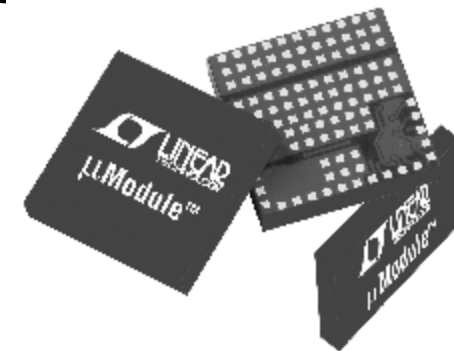$\theta_{JA} = 15^{\circ} \text{ C/W}$ (4 layer PCB)



LTM4600 More Power?


- **Parallel 2 LTM4600 for 20A output**

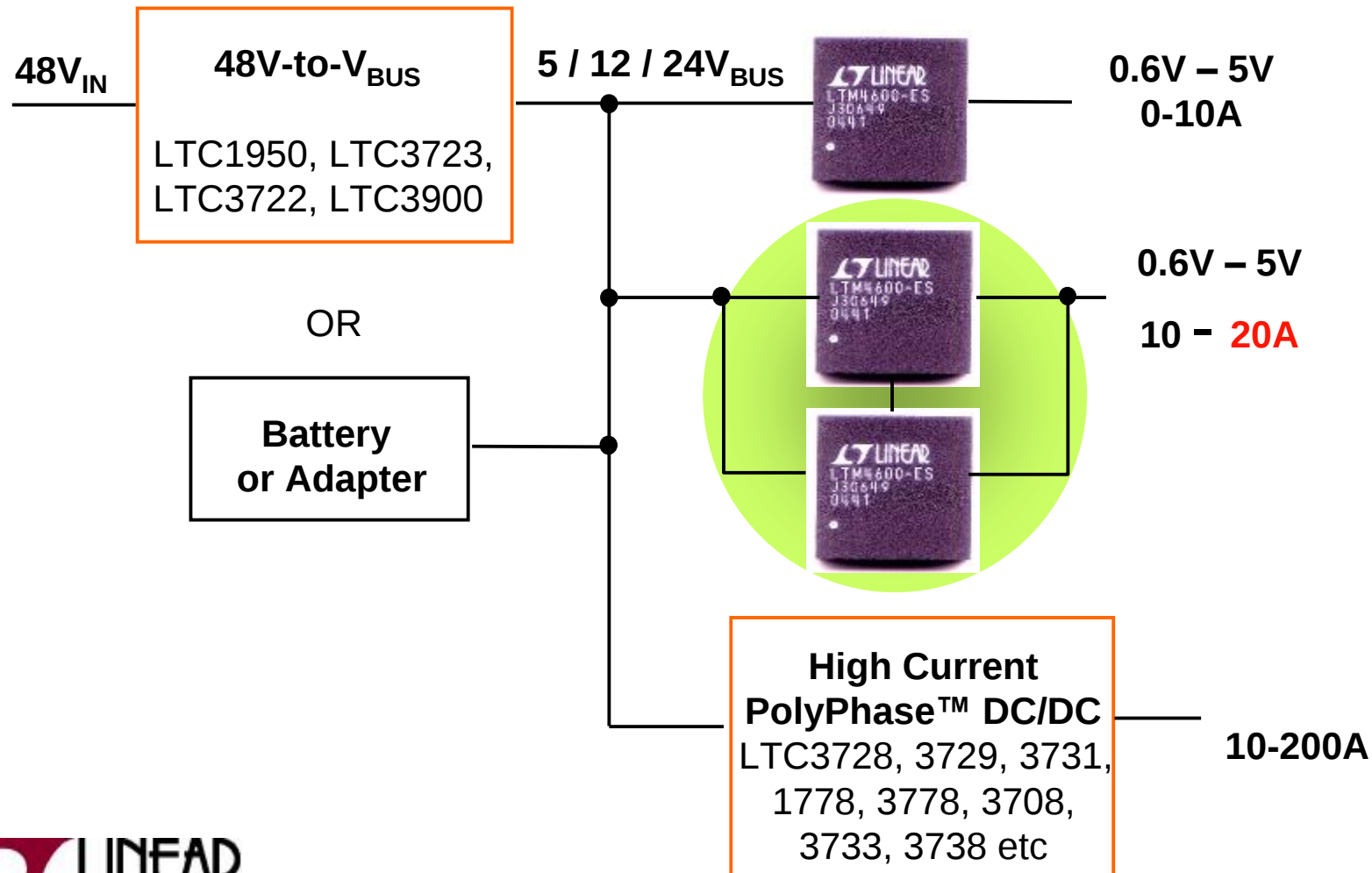

Questions and Discussion

Thank you for your time and interest
in **Linear Technology!**

Instant 10A Power Supply

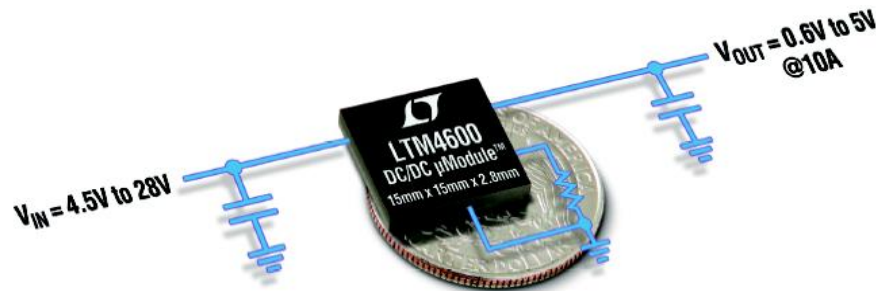

Complete, Quick & Ready.

Performance Driven.