



Lecture 5

CSE 140L

Instructor: C.K. Cheng

Oct. 26, 2005


Courtesy of Jianhua Liu




Agenda

- D flip-flops in Xilinx
- Introduction to Lab 2 assignment
 - Shifter register
 - Asynchronous counter
 - Synchronous counter
 - Gray Counter
 - Pseudo random sequencer
- A complete example of 4-bit binary counter design

FDCE

 

 
So it's a D flip-flop with Clear and Enable signals, and Clear has priority over Enable.



Inputs				Outputs
CLR	CE	D	C	Q
1	X	X	X	0
0	0	X	X	No Chg
0	1	1	↑	1
0	1	0	↑	0

FDPE

 
- D flip-flop with **P**reset and **E**nable



Inputs				Outputs
PRE	CE	D	C	Q
1	X	X	X	1
0	0	X	X	No Chg
0	1	0	↑	0
0	1	1	↑	1




■ T flip-flop with Clear and Enable

 

Inputs				Outputs
CLR	CE	T	C	Q
1	X	X	X	0
0	0	X	X	No Chg
0	1	0	X	No Chg
0	1	1	↑	Toggle

Shift Register

- What's that for?

 

1

1	1	0	1
---	---	---	---




1	1	0	1
---	---	---	---



8:03pm

Shift Register

 

Din

1

0

1

1

D0

0

1

0

1

1

D1

0

0

1

0

1

D2

0

0

0

1

0

D3

0

0


0

0


1

We want

Shift Register

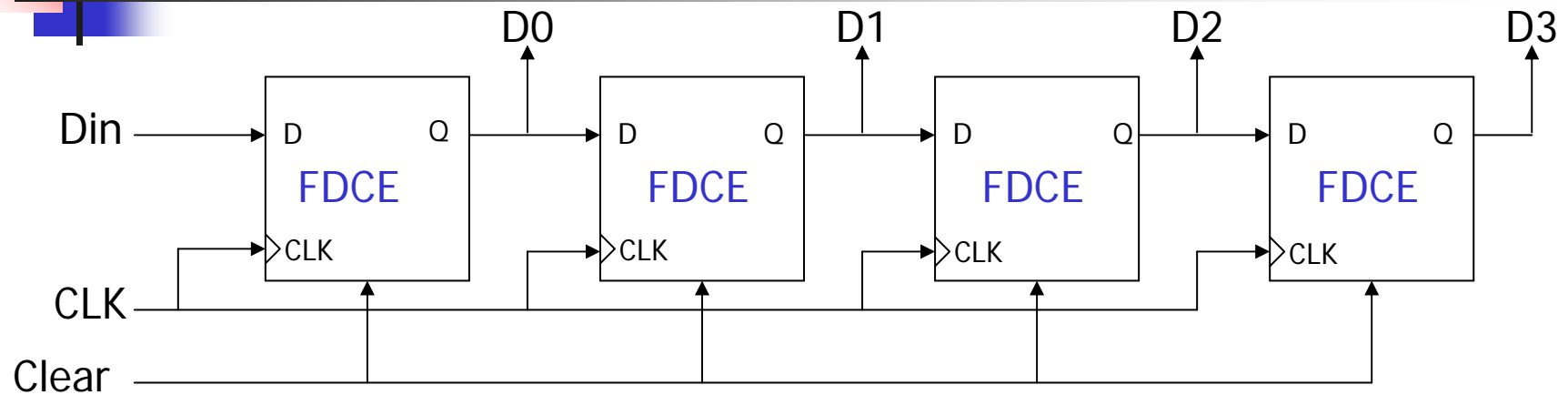

Verification

 



- [illegible]




Counter Styles


- Synchronous counter
 - All flip-flops are governed by a universal global clock signal
- Asynchronous counter
 - No universal global clock signal;
 - Less area
 - You have more flexibility in designing FSMs
 - Less power
 - Eliminates simultaneous D flip-flop switching during clock transitions
 - High speed
 - In terms of throughput
 - But ...hard to design and error prone
 - Complicate protocol for inter-module communication
 - Timing!

Asynchronous Counter

Design

 

Verification

 




Synchronous counter

- Binary counter
 - We'll see a design example of this
- Johnson counter
- Gray counter

Johnson Counter

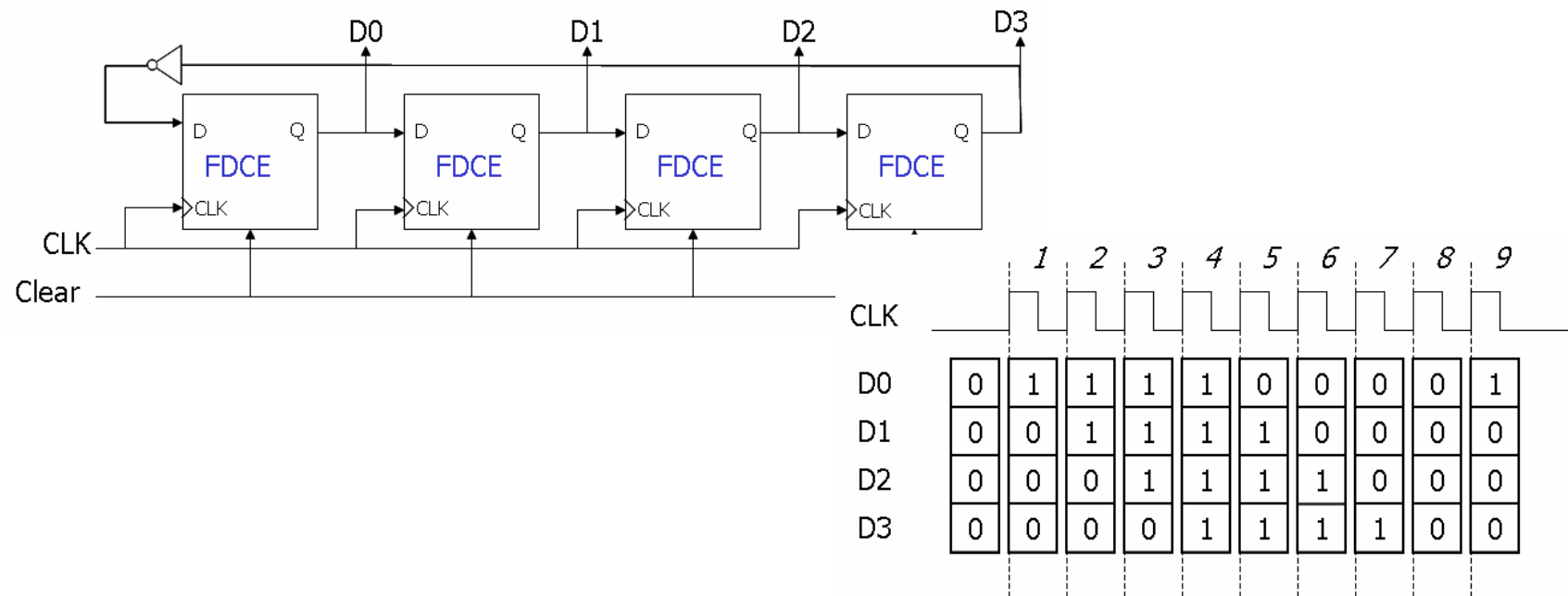- Last output inverted and feed back to the first input.
- also called Mobius counter because it resembles the famous Mobius band.






- [illegible]



Pseudo Random Sequencer

- A pseudo random sequencer generates a sequence of pseudo random bits.
- Pseudo means it's not complete random, it's actually a cyclic bit sequence with a large period.
- Usually implemented using Linear Feedback shifter Register (LFSR).

Random Sequencer

 

- The length of the cycle depends on
 - The feedback network
 - The initial state

