

POWER-SUPPLY FAILURE ALARM

M.K. CHANDRA MOULEESWARAN




Most of the power-supply failure indicator circuits need a separate power-supply for themselves. But the alarm circuit presented here needs no additional supply source. It employs an electrolytic capacitor to store adequate charge, to feed power to the alarm circuit which sounds an alarm for a reasonable duration when the mains supply fails.

During the presence of mains power supply, the rectified mains voltage is stepped down to a required low level. A zener is used to limit the filtered voltage to 15-volt level. Mains presence is indicated by an LED. The low-level DC is used for charging capacitor C3 and reverse biasing switching transistor T1. Thus, transistor T1 remains cut-off as long as the mains supply is present. As soon as the mains power fails, the charge stored in the capacitor acts as a power-supply source for

transistor T1. Since, in the absence of mains supply, the base of transistor is pulled 'low' via resistor R8, it conducts

the components are not critical. If the alarm circuit is powered from any external DC power-supply source, the mains-supply section up to points 'P' and 'M' can be omitted from the circuit. Following points may be noted:

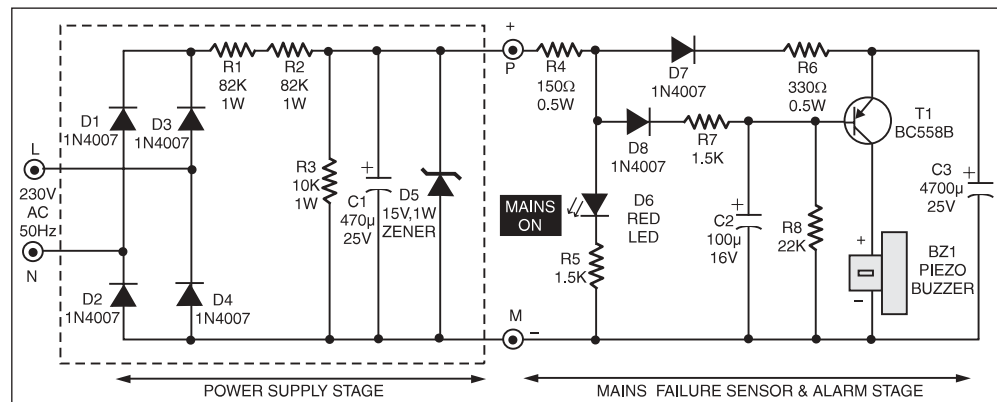1. At a higher DC voltage level, transistor T1 (BC558) may pass some collector-to-emitter leakage current, causing a continuous murmuring sound from the



and sounds the buzzer (alarm) to give a warning of the power-failure.

With the value of C3 as shown, a good-quality buzzer would sound for about a minute. By increasing or decreasing the value of capacitor C3, this time can be altered to serve one's need.

Assembly is quite easy. The values of

buzzer. In that case, replace it with some low-gain transistor.

2. Piezo buzzer must be a continuous tone version, with built-in oscillator.

To save space, one may use five small-sized 1000µF capacitors (in parallel) in place of bulky high-value capacitor C3.