

Electrical Engineering Technology¹

EET 107

Introduction to Circuit Analysis

35


Professor Robert Herrick

Electrical Engineering Technology

Switched RC Transient

- ◆ **Inverse Solution**
- ◆ **Multiple RC – Thévenin Model**

RC Circuit - *Sudden DC Change*

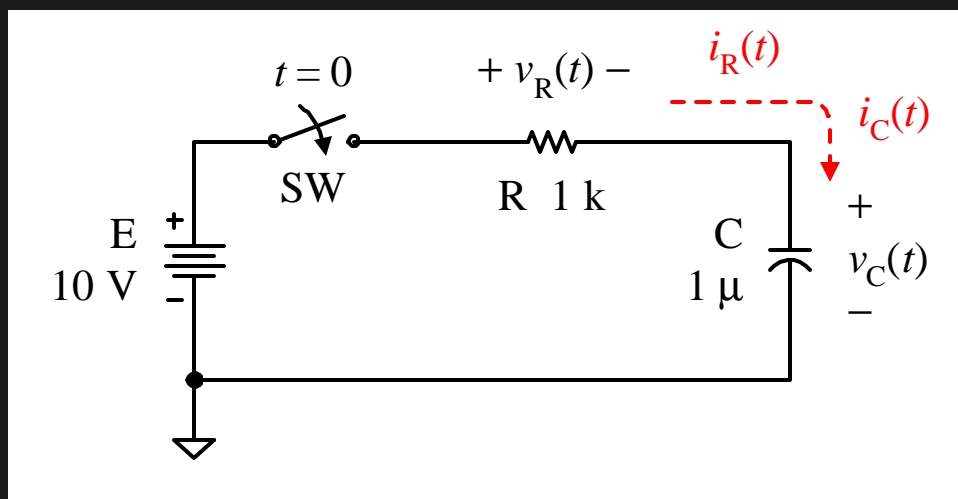

$t = 0^-$

Just before switching

$t = 0$

INITIAL - sudden dc change

$0 < t < 5\tau$

TRANSIENT


$t = 5\tau$

Capacitor 99% charged

$t \rightarrow \infty$

STEADY STATE – final dc

RC Transient DC Circuit

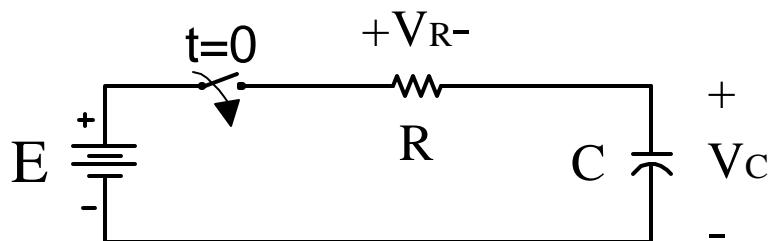

init = initial ($t = 0$)

ss = steady state ($t = \infty$)

$$v_C(t) \quad i_C(t) \quad v_R(t) \quad i_R(t)$$


$$v_x(t) = V_{ss} + (V_{init} - V_{ss}) e^{-t/\tau}$$

$$i_x(t) = I_{ss} + (I_{init} - I_{ss}) e^{-t/\tau}$$

RC Transient DC Circuit

Analyze circuit and find:

- τ
- Initial value
- Steady state value

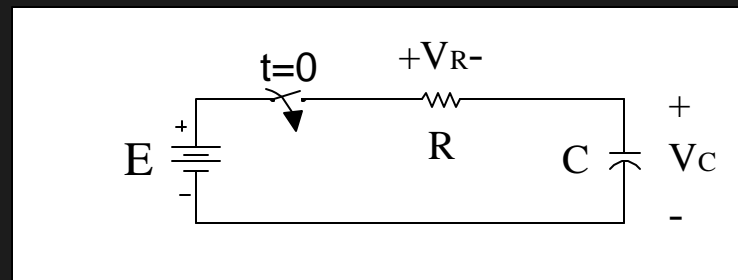

Then substitute:

$$v_x(t) = V_{ss} + (V_{init} - V_{ss}) e^{-t/\tau}$$

RC Circuit – *uncharged capacitor*

$$v_C(t) = V_{ss} + (V_{init} - V_{ss}) e^{-t/\tau}$$

Example: $\tau = RC = 10\text{ms}$
uncharged $V_{init} = 0\text{V}$
 $V_{ss} = 10\text{V}$

$$v_C(t) = 10\text{V} + (0\text{V} - 10\text{V}) e^{-t/10\text{ms}}$$

$$v_C(t) = 10\text{V} - 10\text{V} e^{-t/10\text{ms}}$$

RC Circuit – *charged capacitor*

$$v_C(t) = V_{ss} + (V_{init} - V_{ss}) e^{-t/\tau}$$

Example: $\tau = RC = 10\text{ms}$
charged $V_{init} = 3\text{V}$
 $V_{ss} = 10\text{V}$

$$v_C(t) = 10\text{V} + (3\text{V} - 10\text{V}) e^{-t/10\text{ms}}$$

$$v_C(t) = 10\text{V} - 7\text{V} e^{-t/10\text{ms}}$$

8 RC Transient Circuit Analysis

1. Establish *capacitor voltage* before switch thrown
2. Evaluate *time constant* after switch thrown
3. Initial model of *capacitor* and evaluate circuit
4. Steady state model of *capacitor* and evaluate circuit
5. Apply universal RC equations
6. Sketch resulting equations

Capacitor Models – Know These

CAPACITOR - stores *VOLTAGE*

INITIALLY - Uncharged cap



INITIALLY - charged cap


E_O initial voltage



STEADY STATE - fully charged cap




1. Example - *before switch closed*

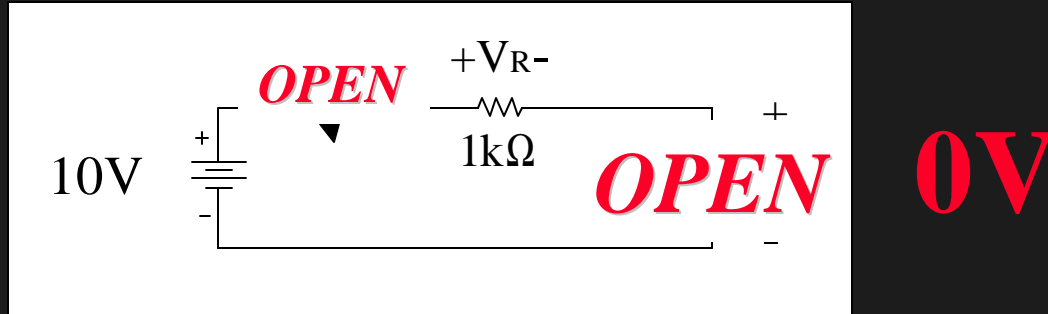

$$t = 0^-$$

- switch open for a long time is assumed
- steady state capacitor \rightarrow **OPEN**
- $V_C = 0V$

2. Example - *time constant*

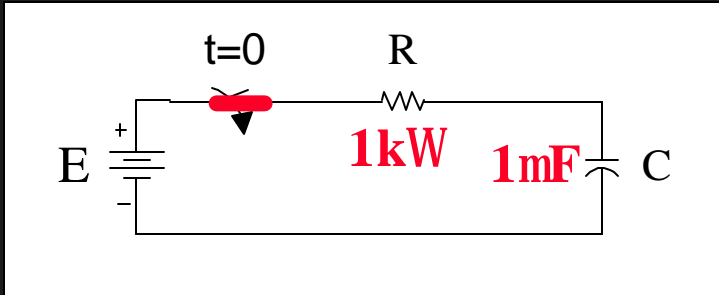

**Switch
closed**

RC Time Constant when switch closed


- $\tau = RC = 1k\Omega \times 1\mu F = 1ms$

Cap 63% charged after switch closed

- $5\tau = 5 \times 1ms = 5ms$

Cap 99.3% charged after switch closed

3. Example - *initial circuit*

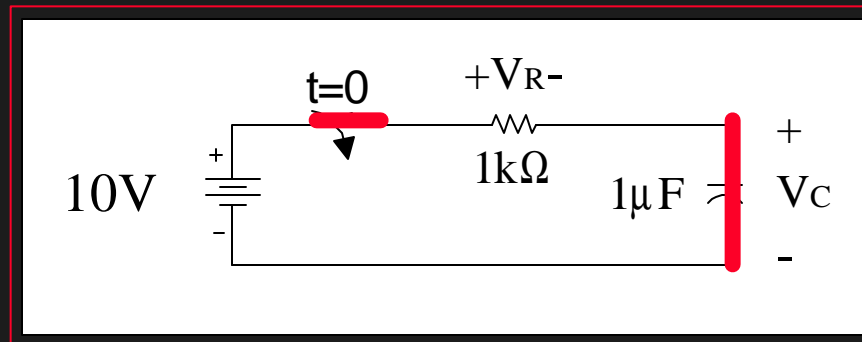


0V from $t = 0^-$

$t = 0$

- $V_C = 0V$ *uncharged cap model*
- Capacitor acts like a **SHORT**
- $V_R = 10V$ and $I_R = I_C = 10mA$

4. Example - *steady state circuit*

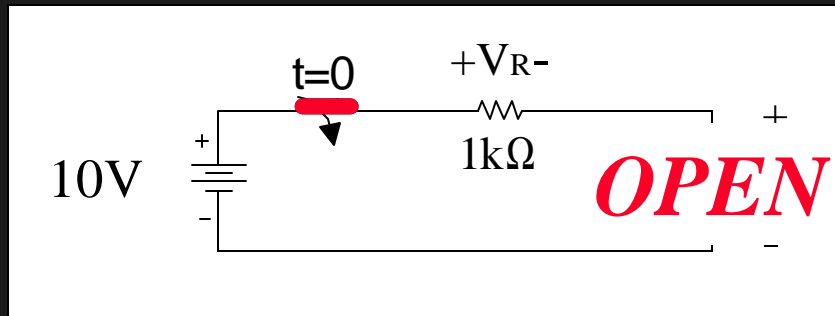


10V

$t \gg 5\tau$

- capacitor acts like an open: *model as OPEN*
- $V_C = 10V$ *capacitor fully charged*
- $V_R = 0V$
- $I_C = I_R = 0mA$

5. Example - capacitor voltage equation

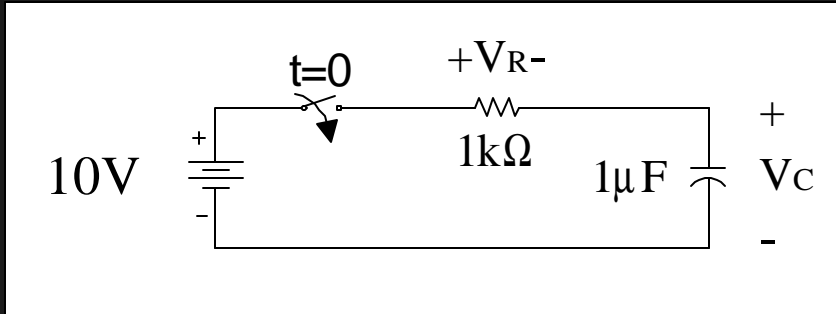

Capacitor Voltage

$$t = 1\text{ms}$$

$$V_{\text{init}} = 0\text{V}$$

$$V_{\text{ss}} = 10\text{V}$$

Complete capacitor voltage expression

$$v_C(t) = V_{\text{ss}} + (V_{\text{init}} - V_{\text{ss}}) e^{-t/\tau}$$

$$v_C(t) = 10\text{V} + (0\text{V} - 10\text{V}) e^{-t/1\text{ms}}$$

$$v_C(t) = 10\text{V} - 10\text{V} e^{-t/1\text{ms}}$$

5. Example - *capacitor voltage equation*

$$v_C(t) = 10V - 10V e^{-t/1ms}$$

Alternate form by factoring out 10V

$$v_C(t) = 10V (1 - e^{-t/1ms})$$

5. Example - *capacitor voltage equation*

Evaluating capacitor voltage - t in units of ms

$$v_C(t) = 10V - 10V e^{-t/1\text{ms}}$$

$$v_C(0) = 10V - 10V e^{-0/1\text{ms}} = 0V$$

$$v_C(1\text{ms}) = 10V - 10V e^{-1\text{ms}/1\text{ms}} = 6.32V$$

$$v_C(2\text{ms}) = 10V - 10V e^{-2\text{ms}/1\text{ms}} = 8.65V$$

• • •

$$v_C(5\text{ms}) = 10V - 10V e^{-5\text{ms}/1\text{ms}} = 9.93V$$

5. Example - *capacitor voltage equation*

Evaluating capacitor voltage - t in units of τ

$$v_C(t) = 10V - 10V e^{-t/\tau}$$

$$v_C(0) = 10V - 10V e^{-0/\tau} = \underline{0V}$$

$$v_C(1\tau) = 10V - 10V e^{-1\tau/\tau} = \underline{6.32V}$$

$$v_C(2\tau) = 10V - 10V e^{-2\tau/\tau} = \underline{8.65V}$$

• • •


$$v_C(5\tau) = 10V - 10V e^{-5\tau/\tau} = \underline{9.93V}$$

6. Example - capacitor voltage sketch


$$v_C(t) = 10V - 10V e^{-t/\tau}$$

$$\begin{aligned} \tau &= 1\text{ms} \\ V_{\text{init}} &= 0V \\ V_{\text{ss}} &= 10V \end{aligned}$$

<u>t</u>		<u>$v_C(t)$</u>
0		0.0V
1τ	1ms	6.3V
2τ	2ms	8.7V
3τ	3ms	9.5V
4τ	4ms	9.8V
5τ	5ms	9.9V

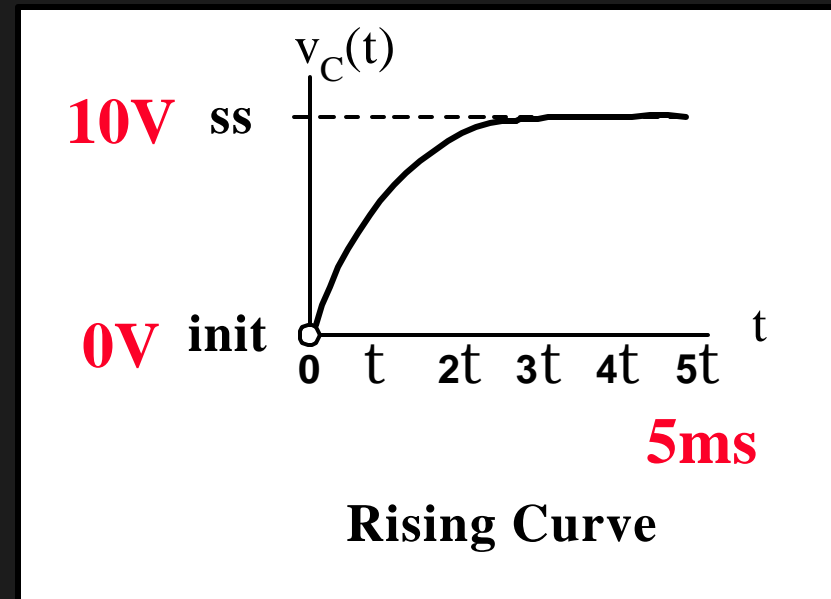

5. Example - capacitor current equation

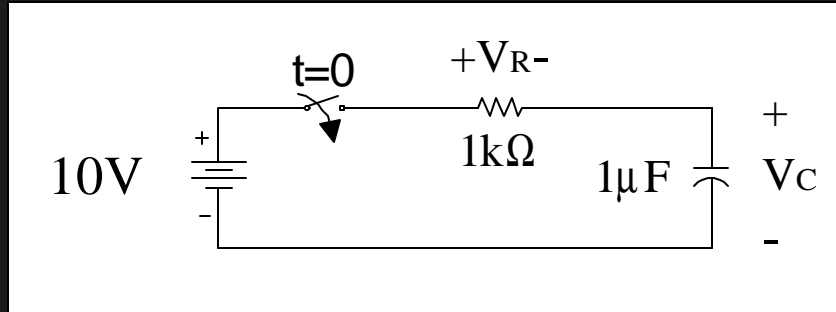

Capacitor current

$t = 1\text{ms}$

$I_{\text{init}} = 10\text{mA}$

$I_{\text{ss}} = 0\text{mA}$

Complete cap current expression

$$i_C(t) = I_{\text{ss}} + (I_{\text{init}} - I_{\text{ss}}) e^{-t/\tau}$$

$$i_C(t) = 0\text{mA} + (10\text{mA} - 0\text{mA}) e^{-t/1\text{ms}}$$

$$i_C(t) = 10\text{mA} e^{-t/1\text{ms}}$$

6. Example - capacitor current sketch


$$i_C(t) = 10\text{mA} e^{-t/\tau}$$

$$\tau = 1\text{ms}$$


$$I_{\text{init}} = 10\text{mA}$$

$$I_{\text{ss}} = 0\text{mA}$$

t		$i_C(t)$
0		10.0mA
1τ	1ms	3.7mA
2τ	2ms	1.3mA
3τ	3ms	0.5mA
4τ	4ms	0.2mA
5τ	5ms	0.1mA

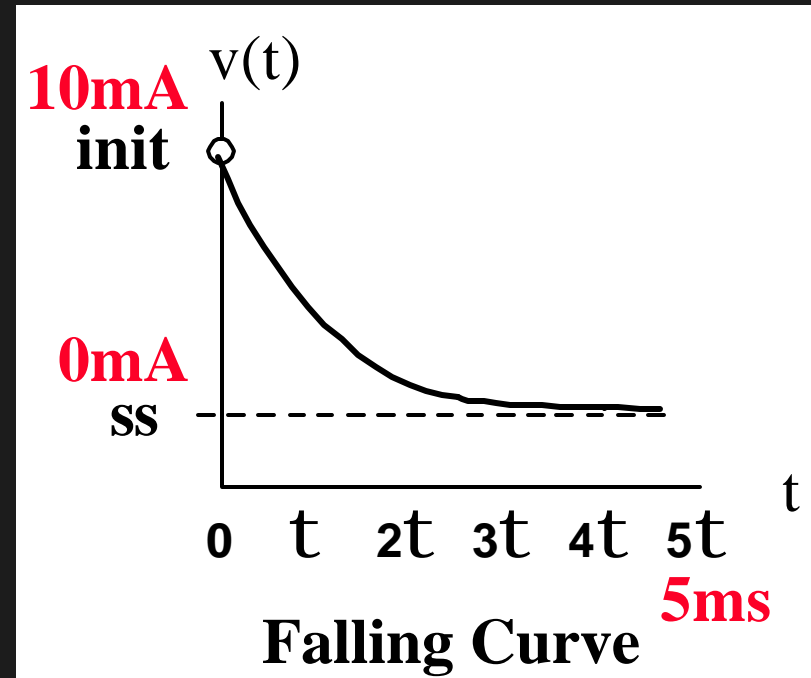

5. Example - *resistor current equation*

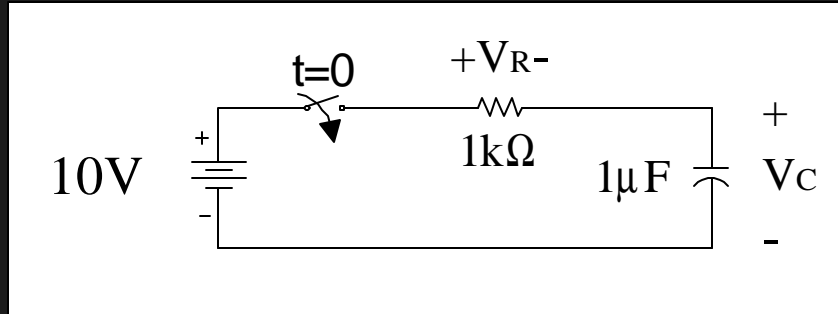

Resistor current

$t = 1\text{ms}$

$I_{\text{init}} = 10\text{mA}$


$I_{\text{ss}} = 0\text{mA}$

Note: quick solution, same as the capacitor current

$$i_R(t) = i_C(t) = 10\text{mA} e^{-t/1\text{ms}}$$

Same sketch

5. Example - *resistor voltage equation*

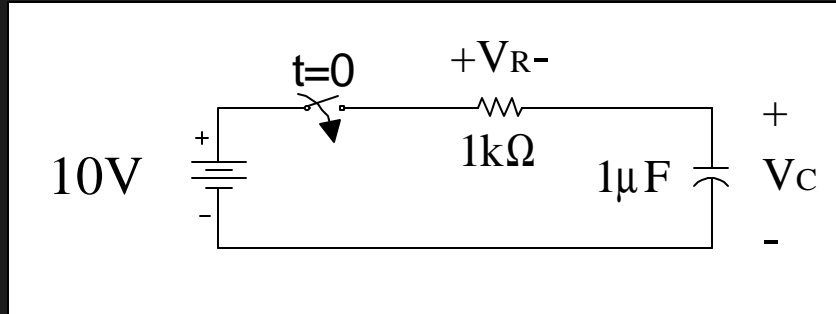

Resistor voltage

$t = 1\text{ms}$

$V_{\text{init}} = 10\text{V}$

$V_{\text{ss}} = 0\text{V}$

Quick solution: *Ohm's Law*

$$i_R(t) = 10\text{mA} e^{-t/1\text{ms}}$$

$$v_R(t) = 1\text{k}\Omega \times 10\text{mA} e^{-t/1\text{ms}}$$

$$\mathbf{v_R(t) = 10V e^{-t/1ms}}$$

6. Example - *resistor voltage sketch*


$$v_R(t) = 10V e^{-t/\tau}$$

$$\tau = 1ms$$

$$V_{init} = 10V$$

$$V_{ss} = 0V$$

<u>t</u>		<u>$V_R(t)$</u>
0		10.0V
1τ	1ms	3.7V
2τ	2ms	1.3V
3τ	3ms	0.5V
4τ	4ms	0.2V
5τ	5ms	0.1V

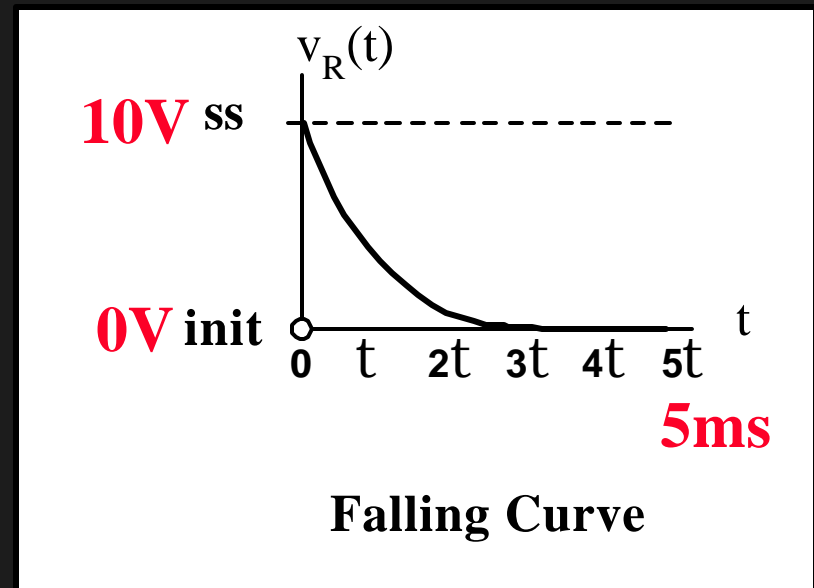


Resistor Sketches

Resistor voltage and current sketch must have the same shape.


Ohm's Law $v(t) = R i(t)$

Related by a constant !

What if Charged Cap - *initial circuit*

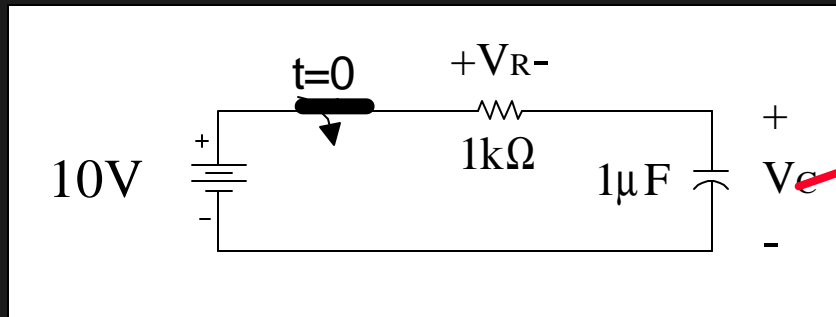

4V

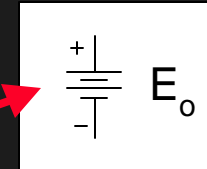

**Model if
charged cap**

$t = 0$ *Initial Circuit*

- What if cap was previously charged to 4V
- Initial model of cap would be a 4V supply
- $V_R = 10\text{V} - 4\text{V} = 6\text{V}$
- $I_R = I_C = 6\text{V}/1\text{k}\Omega = 6\text{mA}$

Electrical Engineering Technology

◆ **Switched RC Transient**

 **Inverse Solution**

◆ **Multiple RC – Thévenin Model**

RC Circuit - *universal equation*

$$v_C(t) = V_{ss} + (V_{init} - V_{ss}) e^{-t/\tau}$$

Example

$$\tau = 10\text{ms}$$

$$V_{init} = -4\text{V}$$

$$V_{ss} = 10\text{V}$$

$$v_C(t) = 10\text{V} + (-4\text{V} - 10\text{V}) e^{-t/10\text{ms}}$$

$$v_C(t) = 10\text{V} - 14\text{V} e^{-t/10\text{ms}}$$

RC Circuit - *universal equation*

Evaluate $v(t)$ at $t = 18\mu\text{s}$


Plug in a time and find a voltage.

$$v_C(\mathbf{18ms}) = 10V - 14V e^{-\mathbf{18ms}/10\mu\text{s}}$$

$$v_C(\mathbf{18ms}) = 7.686V$$

RC Circuit - capacitor voltage sketch

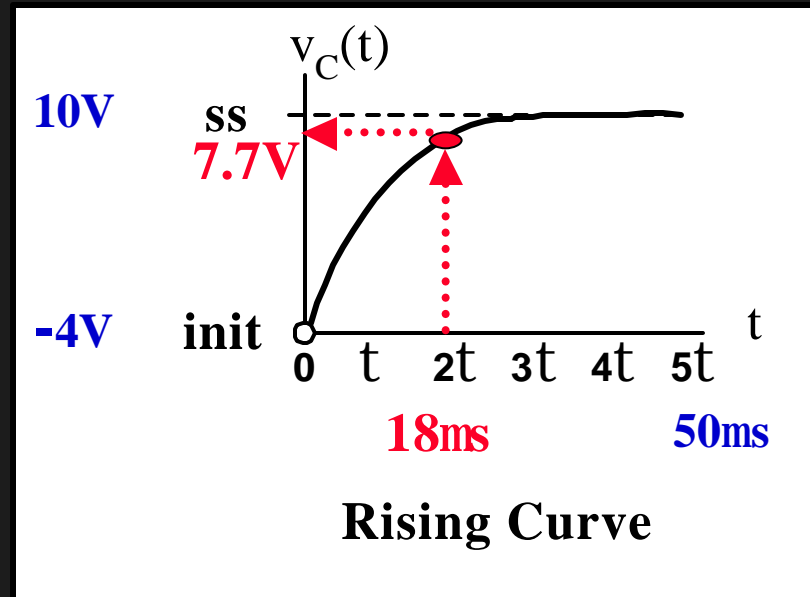
At $t = 18\text{ms}$, $V_C = 7.686\text{V}$



$t = 10\text{ms}$

RC Circuit - *capacitor voltage sketch*

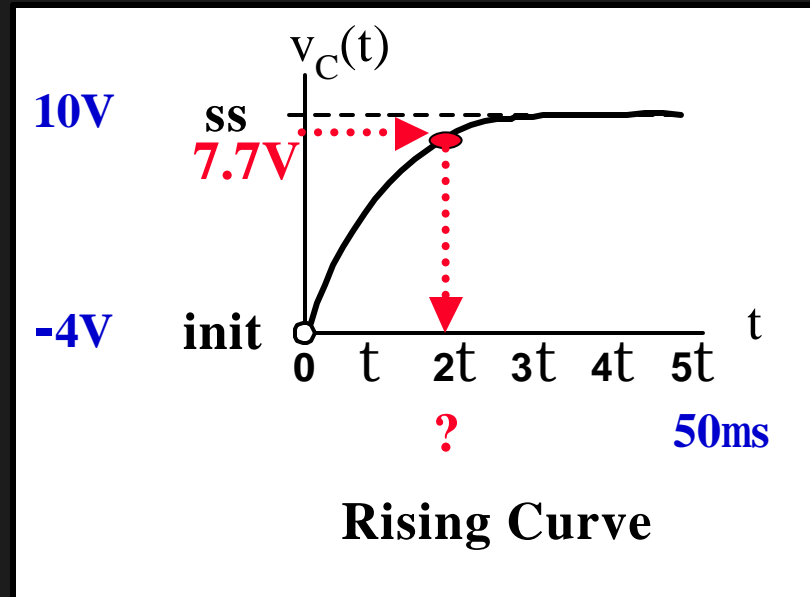Given a voltage, find the corresponding time.



$$t = 10\text{ms}$$

RC Circuit - *universal equation*

How much time “ t ” does it take to charge to a particular voltage ?

For example, how much time “ t ” is needed to charge the capacitor to 3V ?

RC Circuit - *universal equation*

$$v_C(t) = \underline{3V}$$

$$t = ?$$

$$\underline{3V} = 10V - 14V e^{-t/10\mu s}$$

$$-7V = -14V e^{-t/10\mu s}$$

$$0.5 = e^{-t/10\mu s}$$

RC Circuit - *universal equation*

$$\mathbf{Ln} (0.5) = \mathbf{Ln} (e^{-t/10\mu s})$$

↙ exponent pops out


$$-0.693 = -t / 10\mu s$$

$$t = 0.693 \times 10\mu s = \underline{\underline{6.93ms}}$$

RC Circuit - capacitor voltage sketch

How much time is required to charge the capacitor to 3V?

$$t = 6.93\text{ms}$$

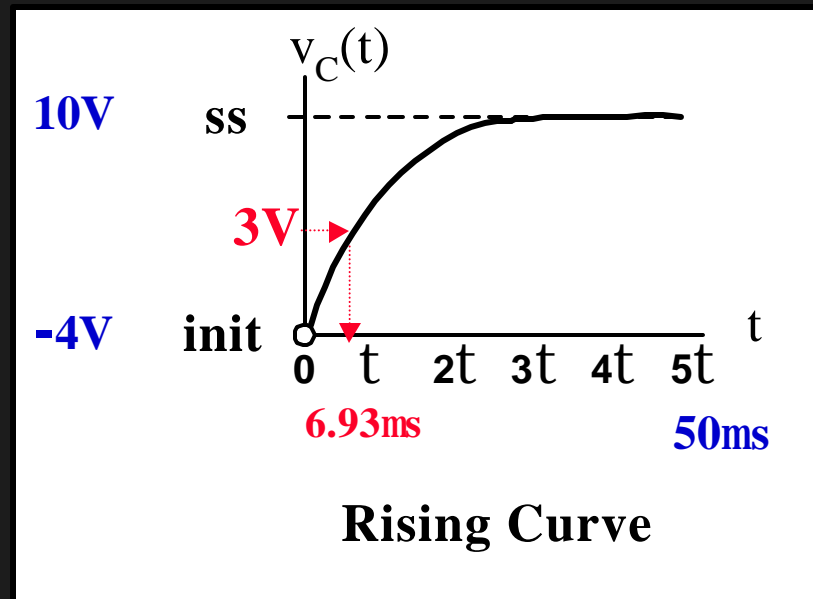

$$t = 10\text{ms}$$


Electrical Engineering Technology

◆ **Switched RC Transient**

◆ **Inverse Solution**

 **Multiple RC – Thévenin Model**


Multiple RC – simplify to Thévenin

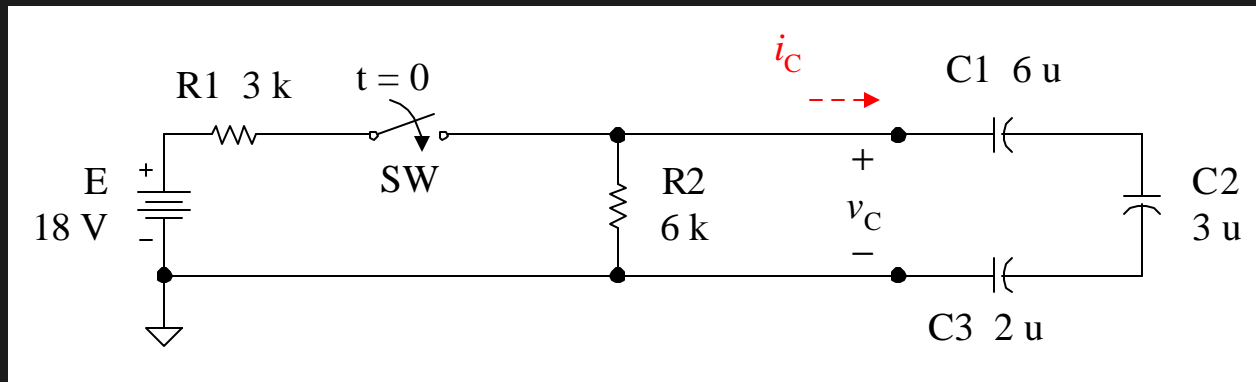


Thévenin model

Charging circuit

Total Capacitance

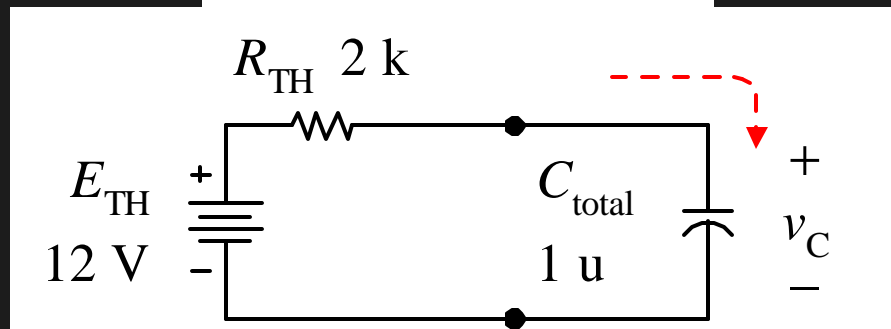


Textbook Example 14-5

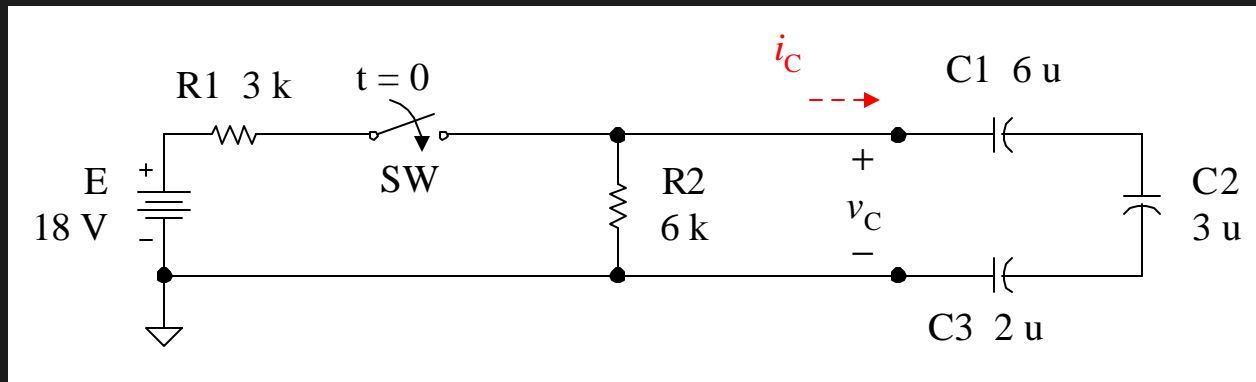

- Uncharged capacitors before switch closed
- Close switch for 4 ms then reopened
- Draw $v_C(t)$ and $i_C(t)$


Textbook Example 14-5

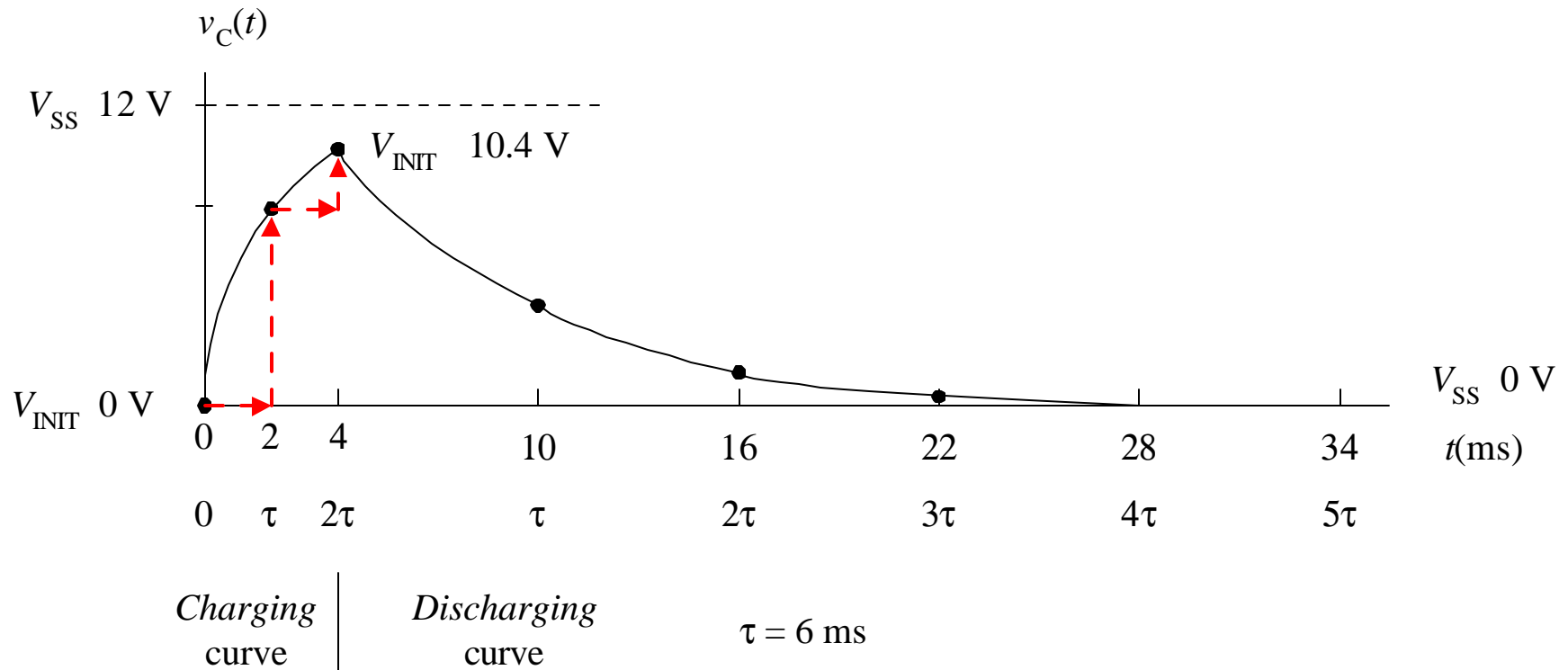

$t = 2\text{ ms}$

$t = 6\text{ ms}$


Textbook Example 14-5

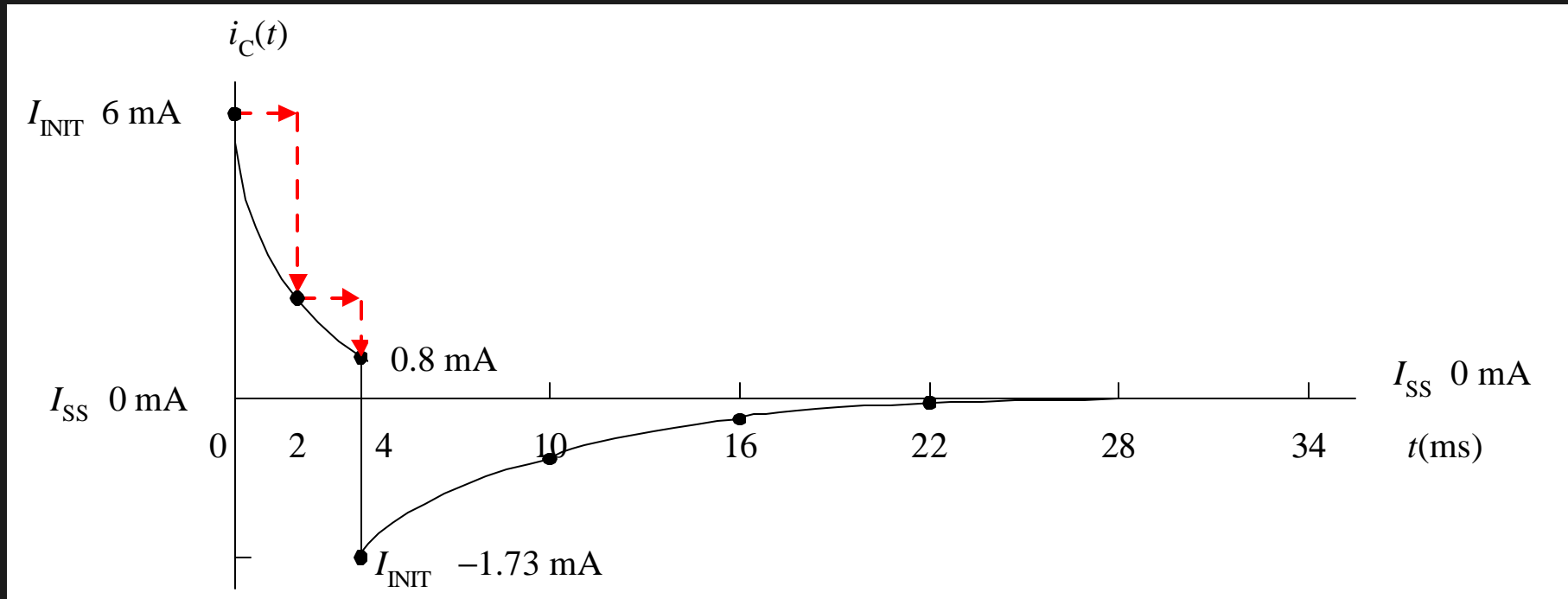

$t = 2 \text{ ms}$

$t = 6 \text{ ms}$


Textbook Example 14-5

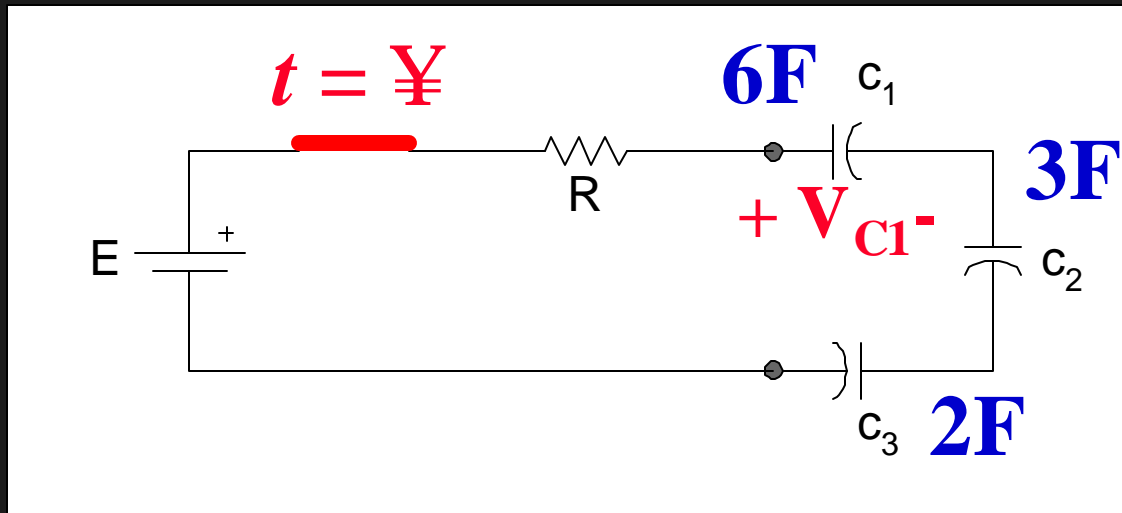

Larger C


Smaller X_C

Less voltage drop

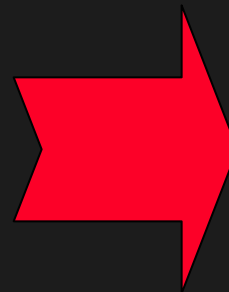

6F drops least voltage

Capacitance - VDR in Steady State

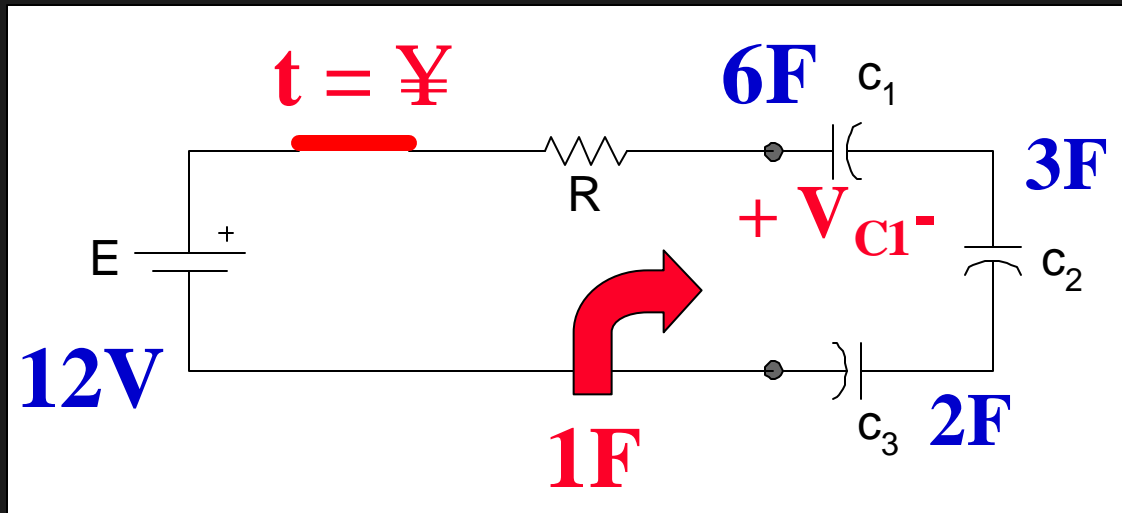

$R \rightarrow 1/C$

VDR steady state

$$V_{C1} = \frac{C_T}{C_1} E = \frac{1F}{6F} 12V = 2V$$

Electrical Engineering Technology

- ◆ **Switched RC Transient**
- ◆ **Inverse Solution**
- ◆ **Multiple RC – Thévenin Model**