



Figure 1 You can drive a single-coil latching relay without an H-bridge circuit, greatly simplifying hardware design and making the most of the low-power-consumption features inherent to latching relays in portable-system applications.