



Microstrip calculations

For $\epsilon_r = 10.2$

For Z_0 in ranges $\leq 44 - 2\epsilon_r$ ie $Z_0 \leq 23.6\Omega$

$$\frac{W}{h} = \frac{2}{\pi} \left\{ B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left[\ln(B - 1) + 0.293 - \frac{0.517}{\epsilon_r} \right] \right\}$$

$$\text{Where } B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}}$$

$$B = \frac{377\pi}{2 * 25\sqrt{10.2}} = 7.41 \quad \text{For } Z_0 = 25\Omega$$

$$\frac{W}{h} = \frac{2}{\pi} \left\{ 7.41 - 1 - \ln(2 * 7.41 - 1) + \frac{10.2 - 1}{2 * 10.2} \left[\ln(7.41 - 1) + 0.293 - \frac{0.517}{10.2} \right] \right\}$$

$$\frac{W}{h} = 1.81 \quad \therefore \text{for a dielectric thickness of 0.635mm width of track} = 1.2\text{mm}$$

For $Z_0 \geq 44 - 2\epsilon_r$ ie $Z_0 \geq 23.6\Omega$

$$\frac{W}{h} = \frac{8e^n}{e^{2n} - 2}$$

$$\text{Where } n = \sqrt{\frac{\epsilon_r + 1}{2}} \cdot \frac{Z_0}{60} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(0.226 + \frac{0.12}{\epsilon_r} \right)$$

For $Z_0 \geq 44 - 2\epsilon_r$ Impedance required = 50Ω

$$44 - 2\epsilon_r = 23.6\Omega$$

$$\frac{W}{h} = \frac{8e^{2.167}}{e^{2*2.167} - 2} = 0.94$$

$$\text{Where } n = \sqrt{\frac{10.2 + 1}{2}} \cdot \frac{50}{60} + \frac{10.2 - 1}{10.2 + 1} \left(0.226 + \frac{0.12}{10.2} \right) = 2.167$$

Using this calculated value of $W/h = 0.94$ it is possible to calculate the line width required to give us a 50Ω line.



$$h = 0.635 \text{ therefore } W = 0.635 * 0.94 = 0.59\text{mm}$$

Using this calculated value of $W/h = 0.94$ it is possible to calculate the effective dielectric constant:-

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(1 + 10 \cdot \frac{h}{W} \right)^{-a.b}$$

$$\text{where } b = 0.564 \left(\frac{\epsilon_r - 0.9}{\epsilon_r + 3} \right)^{0.053}$$

$$\text{and } a = 1 + \left(\frac{1}{49} \right) \ln \left[\frac{(W/h)^4 + (W/52h)^2}{(W/h)^4 + 0.432} \right] + \left(\frac{1}{18.7} \right) \ln(1 + (W/18.1h)^3)$$

$$\therefore b = 0.553 \quad \text{and} \quad a = 0.9911 \quad \therefore ab = 0.548$$

$$\epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(1 + 10 \cdot \frac{h}{W} \right)^{-a.b} \quad \epsilon_{eff} = \frac{10.2 + 1}{2} + \frac{10.2 - 1}{2} \left(1 + 10 * \frac{1}{0.94} \right)^{-0.548}$$

$$\epsilon_{eff} = 6.80$$


Length of transmission line can now be calculated:-

Length of 'n' degrees Transmission Line

$$\lambda_{air} = \frac{c}{f} = \frac{3E8}{5E9} = 0.06\text{m} \quad \lambda_{microstrip} = \frac{\lambda}{\epsilon_{eff}} = \frac{0.06}{\sqrt{6.80}} = 0.023\text{m}$$

$$\therefore \text{Length} = \frac{\text{nn degrees required}}{360} * 0.023 =$$

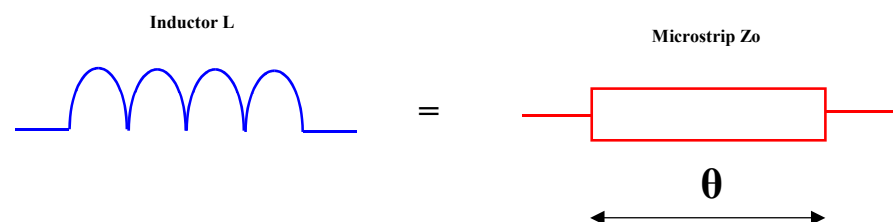Calculation of micro-strip series inductor






$$\omega_L = Z_0 \sin \theta$$

$$\text{Where } \theta < 90^\circ \left(90^\circ = \frac{\lambda_{op}}{4} \right)$$

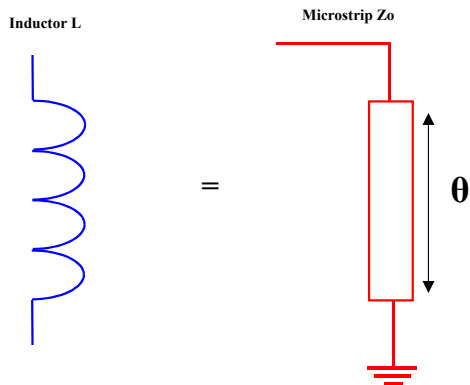
Calculation of micro-strip shunt inductor



$$\omega_L = Z_0 \tan \theta$$

$$\text{Where } \theta < 90^\circ \left(90^\circ = \frac{\lambda_{op}}{4} \right)$$

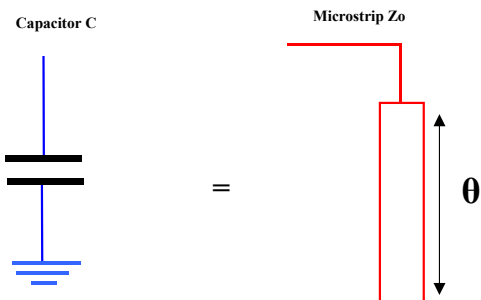Calculation of micro-strip shunt capacitor



$$\omega C = \frac{\tan \theta}{Z_0}$$

$$\text{Where } \theta < 90^\circ \left(90^\circ = \frac{\lambda_{op}}{4} \right)$$

Series C are realised using chip capacitors, Inter-digital capacitors or gaps in tracks.