

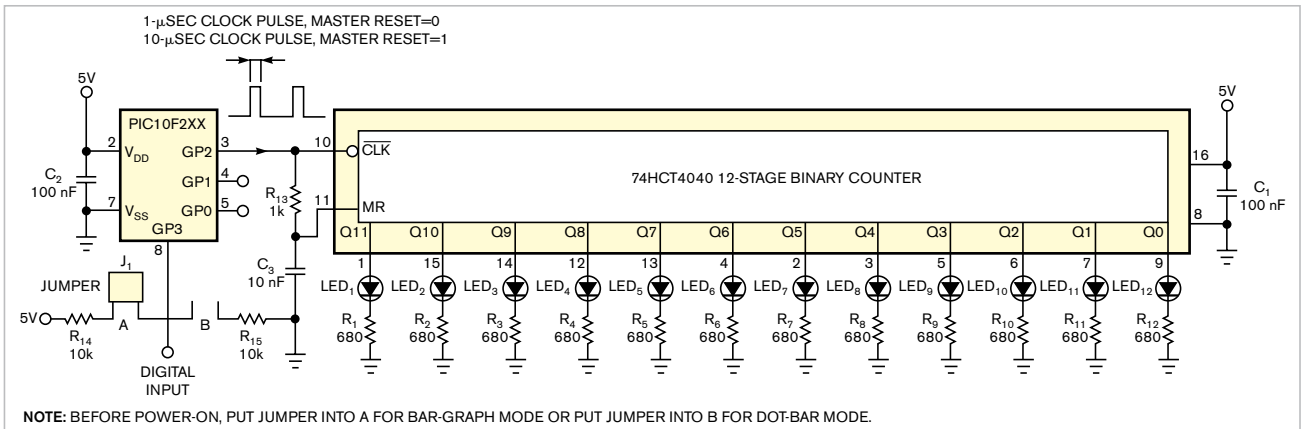


Figure 1 A 12-LED dot-bar/bar-graph display uses a 12-stage binary counter.