Alternate Class AB Amplifier Design

This Class AB amplifier (Figure 1) has an integral common emitter bipolar amplifier (see Q4). The CE amplifier replaces the bipolar main amplifier in the previous design, i.e. Vs in this circuit is the output of the preamp. This produces a more compact and less expensive design since there are fewer components.

0. t

For designs with high open circuit gain, the overall voltage gain of the Class AB stage is determined by the feedback resistors R7 (R_A) and R5 (R_B). So $A_V = -R_B/R_A$.

This audio amplifier has three aspects which need to be explained: (a) the VBE amplifier, (b) bootstrapping for increased gain, (c) feedback for output stability.



Figure 1. Alternate Class AB Amplifier Schematic

page 2 of 14

Amplifier Features

The VBE Multiplier

A V_{BE} multiplier, sometimes called an amplified diode, (Figure 2) is used to provide a tunable voltage between the bases of the Darlingtons X1 and X2. The purpose of this voltage is to bias the bases of the two Darlingtons, keeping them in a "slightly" ON state - a quiescent current of about 20 mA is desirable. Tuning is obtained through the use of potentiometer XRV1. The quiescent current minimizes the zero crossing distortion associated with the power stage emitter followers. Since VBE is a function of temperature, Q3 should be mounted on the same heat sink as X1 and X2 to minimize voltage drift.



Figure 2. Vbe Multiplier

The value of the bias should be about 4 x $V_{BE} \approx 2.8V$, enough to forward bias each of the four base-emitter junctions in the pair of Darlingtons.

Operation

Assume a current I flows down out of node 2. Assume the gain of Q3 is high, so

page 3 of 14

 $I_{b,3}$ can be ignored. A current I' = I - I_E flows through R1 and R2.

$$V_{R1} = I' R1$$

 $V_{R2} = I' R2 = \frac{R2}{R1} V_{BE3}$
 $V(2,3) = V_{R1} + V_{R2} = \left(1 + \frac{R2}{R1}\right) V_{BE3}$

Thus the voltage drop is a multiple of V_{BE3} , and is not restricted to being an integral multiple.

By placing a potentiometer at the base of Q3 we can adjust the bias to accommodate tolerance variations between Darlingtons. A capacitor can be used between nodes 2 and 3 to bypass ac signals so that the VBE multiplier provides a simple dc bias.

Example 1

Design a VBE multiplier to provide a 3.0 V bias. Assume I = 2.5 mA, B = 100, and $V_{BE} = 0.7$ V.

$$V = \left(1 + \frac{R2}{R1}\right) V_{BE3}$$
$$\frac{R2}{R1} = \frac{V}{V_{BE3}} - 1 = \frac{3.0V}{0.7V} - 1 = 3.29$$

Let the resistors have standard values $R2 = 3.3 k\Omega$, $R1 = 1.0 k\Omega$. Or we could let R2 be a 2.7 $k\Omega$ fixed resistor and a 1 $k\Omega$ potentiometer in series. This would allow bias adjustment from 2.59 V to 3.29 V.

*** 07/15/97 00:36:17 *** Evaluation PSpice (July 1993) *** DC Simulation of VBE Multiplier

page 4 of 14

**** CIRCUIT DESCRIPTION

*Spice extraction from McLogic R2 2 1 3.3k R1 1 0 1.0k Q3 2 1 0 Q2N2222 I4 0 2 2.5mA .lib eval.lib

*** 07/15/97 00:36:17 *** Evaluation PSpice (July 1993) ***

DC Simulation of VBE Multiplier

*** BJT MODEL PARAMETERS

Q2N2222 NPN 14.340000E-15 IS BF 255.9 NF 1 VAF 74.03 .2847 IKF 14.340000E-15 ISE NE 1.307 BR 6.092 NR 1 10 RB RBM 10 RC 1 CJE 22.010000E-12 MJE .377 CJC 7.306000E-12 MJC .3416 TF 411.100000E-12 XTF 3 1.7 VTF .6 ITF 46.910000E-09 TR XTB 1.5

*** 07/15/97 00:36:17 *** Evaluation PSpice (July 1993) ***

DC Simulation of VBE Multiplier

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE		VOLTAGE	NODE		VOLTAGE
(1)	0.6609	(2)	2.8794

Note that since the 2N2222 transistor does not have the ideal V_{BE} of 0.7 V, the voltage drop across the V_{BE} multiplier is not exactly 3.0 V.

page 5 of 14

Note that in Example 1 the calculation produced the ratio of R2 to R1. How do you choose unique values? To get a better feel for the range of appropriate values, look at the ac resistance of the VBE multiplier:

$$r=\frac{R2}{\beta}+\left(1+\frac{R2}{R1}\right)\!r_{e}$$
 , where $r_{e}=\frac{0.025\,V}{I_{c}}$

This can be derived from the ac equivalent circuit of the VBE multiplier. To produce a nearly pure dc voltage drop of a given value you would want R2 small, β large and I_c large.

Example 2

Calculate the ac resistance of the VBE multiplier in the previous example.

$$I_{E} = I - I' = 2.5 \text{mA} - \frac{0.7 \text{V}}{1.0 \text{k}\Omega} = 1.8 \text{mA}$$

$$r_{e} = \frac{0.025 \text{V}}{1.8 \text{mA}} = 13.9 \Omega$$

$$r = \frac{3.3 \text{k}\Omega}{100} + \left(1 + \frac{3.3}{1.0}\right) 13.9 = 33.0 \Omega + 59.8 \Omega = 92.8 \Omega$$

If this value of r is too high you could lower R2 (and R1), raise I, or add a capacitor between nodes 2 and 3 with an impedance much less than r at the frequencies of interest.

Bootstrapping

[Reference: Transistor Circuit Techniques - Discrete and integrated, 3rd ed., G.J. Ritchie, Chapman and Hall, London, 1993]

Bootstrapping is a method of increasing the open loop [no feedback] gain of an

page 6 of 14

amplifier. In this amplifier, capacitor C4 is the bootstrap capacitor. The higher the open loop gain, the more accurately the equation $A_V = -R_B/R_A$ will predict the closed loop [with feedback] gain. Consider the circuit below, where Q1 is used in a common emitter amplifier and Q2 is an emitter follower (common collector amplifier).



Figure 3. Bootstrapping Example

If the ac voltage at the collector of Q1 is v, then voltage Av is present at the emitter of Q2 and also at the common terminals of R3 and R4, assuming that the impedance of C4 is very small at the frequencies of interest.

The gain A of the common emitter amplifier is

$$A = \frac{R}{r_{e2} + R}$$
, where R = RE II R3, and $R_{e2} = \frac{0.025 V}{I_{c2}}$

The voltage across resistor R4 is v - Av = (1 - A) v.

So for ac signals, the resistance of R4 appears to be R4' = R4 / (1 - A), which is much

page 7 of 14

higher than R4 since A is typically just slightly less than 1 for the emitter follower.

Since R4' is the collector resistance for the common emitter stage, the gain of the CE stage will become

$$A_{V} = -\frac{R4' \operatorname{IIr}_{in(follower)}}{r_{e1}}, \text{ where } r_{in(follower)} = r_{\pi} + (1+\beta)R \approx \beta R$$

Without the bootstrapping, the gain would be

$$A_{V} = -\frac{(R3 + R4) \text{ II } r_{in(follower)}}{r_{e1}}$$

a value much less than that seen if C4 is used.

. . . .

Example 3. Bootstrapping

Design a CE/CC amplifier pair. Compare the voltage gains with and without bootstrapping.

Assumptions and Design Parameters

Vcc = 12 V Ic for each transistor is 2.5 mA β for each transistor is 100 RL = 1 k Ω Use 2N2222 for simulations

See appendix for detailed component calculations and PSpice files

page 8 of 14





Without bootstrapping (Figure 4), the voltage gain is

$$\begin{split} A_v &= -\frac{\text{RC II}\left(\beta \times \text{RE2}\right)}{r_{e1}} \times \frac{\text{RE2}}{\text{RE2} + r_{e2}}, \text{ where } r_{ei} = \frac{V_t}{I_{ci}} = \frac{25\text{mV}}{I_{ci}} \\ A_v &= -\frac{1.6\text{k}\Omega\,\text{II}\,290\text{k}\Omega}{10\Omega} \times \frac{2.9\text{k}\Omega}{2.9\text{k}\Omega + 10\Omega} \\ A_v &= -159 \times \frac{2900}{2910} = -158.6 \\ A_v \left(\text{PSpice}\right) = -129 \end{split}$$

B x RE2 represents the input resistance of the common collector amplifier, and is the load for the common emitter amp.

With bootstrapping (Figure 5), the collector resistor of the common emitter is split into two pieces and the bootstrap capacitor C4 is

page 9 of 14

added. The impedance of C4 should be small in the audio frequency band.



Figure 5. Common emitter, common collector amplifiers with bootstrapping. RC was split in half and capacitor C4 added. The amplitude of the sine wave input was reduced in anticipation of higher gain.

The voltage gain of the amplifier pair is A_{v} , and the voltage gain of the common collector stage is A.

$$\begin{split} A_v &= -\frac{RC2' \, \text{II} \, r_{in} \, (\text{follower})}{r_{e1}} \times A \\ \text{where } r_{ei} &= \frac{V_t}{I_{ci}} = \frac{25 \text{mV}}{I_{ci}}, \ A = \frac{R}{R + r_{e2}}, \\ R &= RE2 \, \text{II} \, \text{RC1}, \ \text{and} \ r_{in} \, (\text{follower}) = \beta R \end{split}$$

page 10 of 14

$$\begin{aligned} \mathsf{R} &= \mathsf{RE2} \: || \: \mathsf{RC1} = 2.9 \mathsf{k}\Omega \: || \: 800\Omega = 627\Omega \\ \mathsf{r}_{e2} &= \frac{25\mathsf{mV}}{2.5\mathsf{mA}} = 10\Omega \\ \mathsf{A} &= \frac{\mathsf{R}}{\mathsf{R} + \mathsf{r}_{e2}} = \frac{627\Omega}{637\Omega} = 0.984 \\ \mathsf{RC2'} &= \frac{\mathsf{RC2}}{1 - \mathsf{A}} = \frac{800\Omega}{1 - 0.984} = 50\mathsf{k}\Omega \\ \mathsf{A}_{v} &= -\frac{50\mathsf{k}\Omega \: || \: 62.7\mathsf{k}\Omega}{10\Omega} \times 0.984 \\ \mathsf{A}_{v} &= -2782 \times 0.984 = -2737 \\ \mathsf{A}_{v} \: (\mathsf{PSpice}) = -1300 \end{aligned}$$

While we can show a large increase in gain (factor of nearly 20) from the no bootstrap case, the calculation and simulation do not match. The reason for this is not yet known.

Appendix

Amplifier Calculations

$$Ic = 2.5 \text{ mA}, B = 100, RL = 1k\Omega, Vcc = 12 \text{ V}.$$

Let the voltage at the base of Q1, V_B, be about Vcc/3 or 4 V for good output swing Then at the emitter of Q1, V_E = 4 - V_{BE} = 3.3 V. Let I_E = I_C to simplify calculations.

$$RE1 = \frac{V_E}{I_E} = \frac{3.3V}{2.5mA} = 1.32k\Omega$$

Let the current through the divider consisting of R1 and R2 be about ten times the Q1 base current, or about $0.1I_F$ when $\beta = 100$.

$$R1+R2 = \frac{12V}{0.25mA} = 48k\Omega$$
$$\frac{R2}{R1+R2}V_{cc} = 4V$$
$$R2 = \frac{4V}{V_{cc}}(R1+R2) = \frac{4V}{12V}48k\Omega = 16k\Omega$$
$$R1 = 32k\Omega$$

Let the drop across Q1's collector resistor be about Vcc/3.

$$RC = \frac{V_{cc} - V_{c}}{I_{c}} = \frac{4V}{2.5mA} = 1.6k\Omega$$

The dc bias at the base of Q2 should be 8 V. The emitter voltage should be 7.3 V.

page 12 of 14

$$\mathsf{RE2} = \frac{7.3\mathsf{V}}{2.5\mathsf{mA}} = 2.9\mathsf{k}\Omega$$

PSpice Input Files

```
CE/CC Amplifier - no bootstrapping
* nominal gain = -160
* Spice extraction from McLogic
C1
       1 b1 91uF
C2
       e2 Vout 33uF
       Vcc cl 1.6k
RC
       el 0 1.32k
RE1
RE2
       e2 0 2.9k
       Vin 0 sin(OV 10mV 1kHz)
Vin
       Vcc 0 12V
VCC
       c1 b1 e1 02N2222
01
       el 0 1000uF
CE
R1
       Vcc bl 32k
R2
       bl 0 16k
       Vout 0 1k
RL
02
       Vcc c1 e2 Q2N2222
       Vin 1 100
Rs
* Pull the transistor models from the eval library
.lib eval.lib
.probe
* Run simulation for 2 cycles, 200 points minimum
.tran 0.02ms 2ms 0 10us
* Show the output voltage in the dialog box as sim runs
.watch tran V([Vout])
.end
*************
Bootstrapped CC/CE amplifier
```

```
* Nominal gain = -2700
```

* Spice extraction from McLogic

C1 1 b1 91uF

page 13 of 14

C2e2 Vout 33uF RC1 Vcc 2 800 2 cl RC2 800 el 0 1.32k RE1 Vin 0 sin(OV 1mV 1kHz) Vin Vcc 0 12V VCC Q1 c1 b1 e1 Q2N2222 CE el 0 1000uF R1 Vcc bl 32k R2 bl 0 16k RL Vout 0 1k 02 Vcc c1 e2 Q2N2222 RE2 e2 0 2.9k Vin 1 100 Rs 2 e2 4000uF C4 * Pull the transistor models from the eval library .lib eval.lib .probe * Run simulation for 2 cycles, 200 points minimum .tran 0.02ms 2ms 0 10us * Show the output voltage in the dialog box as sim runs

.watch tran V([Vout])

.end