Don Lancaster's **Tech Musings**

May, 1999

et's take a look at something so old and so simple that it just may be new for you. At any rate, this one still makes a seldom-seen and a really fine little homebrew project...

Twinkle Lights

The NE-2 neon lamp is by far your number one electronic component of all time. Yeah, this device is more or less way into retirement, owing to the high voltages and the restricted light output. But you can still get them for a dime or so each at *Radio Shack* and elsewhere. Nothing else even comes remotely close to its versatility or its elegant simplicity.

In its prime, that good old NE-2 served as everything from...

panel lamps electronic organs surge protectors voltage regulators polarity finders ac-dc voltmeters display decorations proximity devices and-or logic flash triggers strobe lights computer memories flame monitors lamp dimmers touch sensors signal sources flip-flop latches frequency dividers "hot chassis" checkers audio oscillators vacuum tube testers radiation detectors

...and an awful lot more.

The NE-2 is just a small glass tube having a tiny amount of low pressure neon gas in it. Two simple pins act as terminals. At voltages below 55 volts or so, your neon lamp is more or less an open circuit. Above this value, the tube "turns on" and starts to conduct, emitting a distinctive orange light.

When conduction starts, the NE-2 becomes a *negative* resistance. This

happens as more current ionizes more gas in the plasma and *lowers* the drop across the terminals. Typically to 45 volts or so. This destructive behavior *must* get externally current limited. Usually with a high value resistor of 100K or more. Conduction continues so long as a current source remains. When and if your current drops down to zero, the neon lamp turns off.

Figure 1-a shows us the standard NE-2 pilot light circuit. Connect this one to 110 volts ac and both pins will light up to that characteristic neon orange. Once again, external current limiting *must* be provided, or a NE-2 will self destruct. A variation on this circuit is the standard hardware store "circuit tester". Both lamp pins light on ac, but only the positive one does on dc. Thus, you have a simple ac-dc and polarity detector.

Another long forgotten trick with the circuit checker is the *hot chassis* detector. Some consumer electronics

Tachometer design basics "knotty neon" lighting rope New PIC breadboard source Some boat anchor resources Ancient twinkle lights circuit

> connects one side of the line cord to an internal chassis. Supposedly, the polarized prongs of the power cord prevent the wrong side from getting connected, but mistakes do happen.

> A severe shock hazard can exist when you try to service hot chassis gear. To find out for sure, just hold one terminal of a neon tester in your hand and then touch the other to the chassis. If the lamp weakly lights, reverse the power cord or take other suitable precautions.

No shock should be felt.

Figure 1-b shows us a simple neon lamp *relaxation oscillator*. That two meg resistor by itself cannot provide enough current to light the neon lamp in this circuit. So, the lamp remains off and the capacitor starts charging. When the capacitor voltage gets up to 55 volts, the neon lamp turns on and flashes brightly.

The capacitor then gets discharged to the lamp's turnoff point, and the


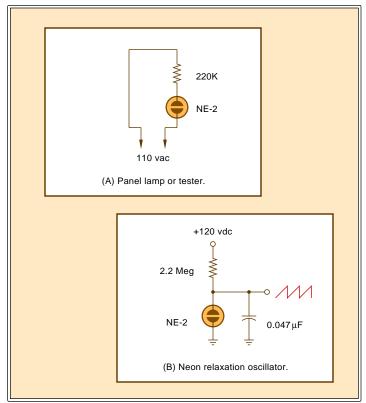



Fig. 1 - TWO NEON LAMP CIRCUITS.

136.1

Tech Musings

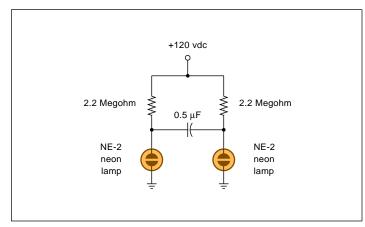

bulb.

 

cycle repeats. The lamp flashes at a frequency determined by the RC time constant and the thresholds involved.

A sawtooth-like exponantial wave will appear across the capacitor and can get sensed and used as an audio or other signal source.

Neon circuits are also micropower because only a very few microamps are needed from your dc supply.

In Figure 2, a pair of neon lamps gets used as an alternating flasher. This was once known as an *astable multivibrator*. The cap first charges right-to-left and then left-to-right as the alternate lamps conduct. The secret to startup involves small stray capacitances inherently around each Figure three gives you a cute neon *twinkle light* effect. I have used this many times for dance decorations.

Long ago and far away.

The sequence ends up pretty much random. Owing to the differences in lamp thresholds. Hence your twinkle lights or "little stars". At any given time, one (or rarely two) lamps are lit and provide capacitor charging paths. As the caps charge, the threshold for another lamp is exceeded and it fires. Because of a *commutation* effect, any other lamp turning on should turn off any already lit ones.

For relaxation oscillators to work, the resistors and supply voltage must

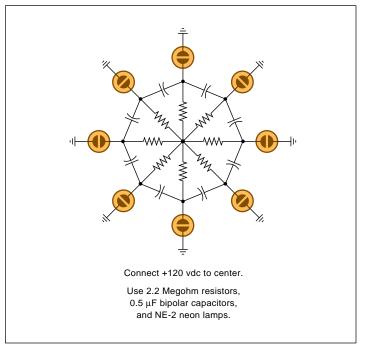


Fig.3 – "TWINKLE LIGHTS" for a dance, show, or display.

all get chosen to lie on the negative resistance portion of the NE-2 curve. This usually happens over a rather wide value range. Some cut-and-try may be needed for anything fancy. Resistors in the one to four meg range are usually a good starting point.

What gets really mind-blowing is that I still know of no way to do the same thing using LED's that can end up remotely as simple, as cheap, or as low in power.

Much more on elegant simplicity apears in ELESIMP.PDF Found on my *www.tinaja.com* website.

Tachometer Fundamentals

A *tachometer* is an instrument to measure the speed of a rotating shaft. The results are often shown in RPM, short for *Revolutions per Minute*.

Tachs might be digital or analog. Generally, digital is more accurate but can be *much* harder to read and interpret. Especially during changes. Since there are lots of subtle gotchas to tach design, I thought we might go over some fundamentals. Digital tach design can often be split into *sensing*, *conditioning*, *algorithmic conversion*, and *display*...

Sensing– Sensing involves generating one or more pulses per revolution. In a "sensorless" sensing, speed signals are extracted and conditioned directly from the motor's back emf. This has to be tightly integrated into the exact motor and controller in use.

In "sensored" sensing, a device is placed on or near the motor shaft to generate one or more electric pulses per shaft revolution.

Sensored sensing most often gets done magnetically or optically.

Mag sensing is usually done with magnets and *Hall Effect* devices. Or alternately by using ferrous gear teeth and variable reluctance coils. With infrared optics, a bladed vane could interrupt a LED-photodetector pair. Or ir light could be bounced off reflective shaft portions.

A third route of very questionable reliability is to use direct mechanical contacts in a commutator setup. Or a physical gear or roller.

Note that speed can be determined using a single sensor. But when *both* speed and direction are needed, then

May, 1999

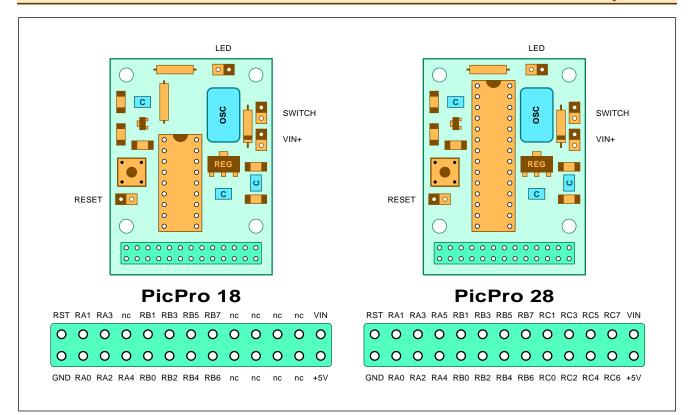


Fig. 4 – THESE PICPRO BREADBOARDS from Technical Works simplify PIC design and interface.

a pair of *quadrature* sensors must be used. These are arranged so that one is in the *middle* of its sensing activity while the other is at its *edge*. A dual flip-flop or a computer logic circuit can extract both speed and direction. As could a somewhat trivial software algorithm. Actual position could get found by adding up, or *integrating* all your speed pulses.

Honeywell and Allegro Electronics are major suppliers for low cost Hall sensors. The optoelectronic providers will include Hewlett-Packard, Texas Instruments, Toshiba, Siemens, and QT Optoelectronics.

Conditioning– This just consists of making sure that each sensed pulse ends up as a single clean event. It can be done using hardware, software, or a mixture of both.

Algorithmic conversion– This step usually has to solve several interface problems. It might include numeric translations and reaching acceptable measurement speeds.

At 600 rpm with a single pulse per revolution, you'll have 10 pulses per second. The "10" result from a direct one second measurement needs to be multiplied by "60" to provide a "600" display. Other scaling factors need to be considered when more than one pulse per revolution is involved, or in automotive applications where each cylinder fires only once for every two revolutions. Note that certain newer cars may fire their cylinders *twice* to eliminate a distributor. Once for real and once at a uselessly wrong time.

Watch this detail.

Scaling can be done with hardware or software. These days, a software scaling using a PIC or other micro is the preferred choice.

Again, at 600 rpm using a single pulse per revolution, you'll have 10 pulses per second. Six seconds would be required to achieve a ten percent accurate measurement. Much longer times would be required for higher accuracy, especially at lower speeds.

One obvious solution to response times is to have more sensed pulses per revolution. A second solution is to use a phase lock loop (such as a CMOS 4046) to "multiply" your input pulse repetition rates by a reasonable selected numeric value.

Such a multiplication might also perform the required scaling as well.

However, there is an inherent lag in any pll circuit which might cause the display to unacceptably fall behind real time speed changes.

An often optimum workaround is to measure the time period *between* the sensed pulses instead of counting their frequency. This is known as the *EPUT* method, as in *events per unit time*. Your once horrendous nasty involved here is that a 1/x calculation is required. If your chosen micro has no division instructions, alternates such as a table lookup or a repeated subtraction can be used. Scaling can also be provided internal to your 1/xcalculation process.

Another algorithmic consideration is your update time. For continuous updates tend to jump around and can be incredibly difficult to interpret or follow. Something near two to four updates per second is often a good choice that optimizes human factors. It's also a very good idea to take the average of as many measurements as practical before displaying them. It is sometimes optimum to round all the display values off to the nearest 100 revolutions per minute.

In certain circumstances, it is best

Tech Musings

SOME USEFUL TACHOMETER RESOURC

Abbeon Cal 123 Gray Ave Santa Barbara CA 93101 (805) 966-0810

Allegro Microsystems Box 15036 Worcester MA 01605 (508) 853-5000

Asian Sources 1020 Church St Evanston IL 60201 (847) 475-1900

Barbara Arnold Sales 3704 Carlisle Ct Modesto CA 95356 (800) 335-4852

Circuit Cellar Ink 4 Park St #20 Vernon CT 06066 (203) 875-2751

Scott Edwards 964 Cactus Wren Lane Sierra Vista AZ 85635 (520) 459-4802 Electromatic Equipment 600 Oakland Avenue Cedarhurst NY 11516 (800) 645-4330

Hewlett-Packard PO Box 10301 Palo Alto CA 94303 (415) 857-1501

Honeywell Microswitch 3660 Technology Dr Minneapolis MN 55418 (800) 345-6770

Measurement & Control 2994 W Liberty Ave Pittsburgh PA 15216 (412) 343-9666

Microchip Technology 2355 W Chandler Blvd Chandler AZ 85224 (602) 786-7200

Frank Murphy Mfg PO Box 470248 Tulsa OK 74147 (918) 627-3550 Omega Engineering One Omega Dr Stamford CT 06907 (800) 826-6342

Parallax 3805 Atherton Rd #102 Rocklin CA 95765 (916) 624-8333

QT Optoelectronics 610 N Mary Ave Sunnyvale CA 94086 (408) 720-1440

Red Lion Controls 20 Willow Springs Circle York PA 17402 (717) 767-6511

Reddington Counters 130 Addison Rd Windsor CT 06095 (860) 688-6205

Sensors 174 Concord St Peterborough NH 03458 (603) 924-9631 Siemens Components 2191 Laurelwood Rd Santa Clara CA 95054 (408) 980-4500

Sunshine Instruments 1810 Grant Avenue Philadelphia PA 19115 (800) 343-1199

TES Electronics 57 Jen-Ai Road SEc 2 Taipei, TAIWAN 886-2-2393-9142

Texas Instruments PO Box 655303 Dallas TX 75380 (800) 336-5236

Toshiba 1220 Midas Wy Sunnyvale CA 94086 (800) 321-1718

Veeder Root 125 Powder Forest Dr Simsbury CT 06070 (860) 651-2700

to provide for *both* an analog and a digital speed display. Use digital for accuracy, and analog to interpret any sudden changes.

Display– A PIC or other micro can be used for input conditioning, scaling, and algorithmic conversion. This will often drive a LCD or LED display. A LCD display might typically carry its own very specialized controller chip strapped onto its back.

Some Resources

I've gathered together some tach info for you as this month's resource sidebar. Your best starting points are usually the *Sensors* or *Measurements* & *Control* trade journals. Lab tachs are resold by *Omega Engineering*, by *Abbeon Cal*, and others.

Three examples of handheld tachs include that *TouchTach* by *Barbara Arnold Sales*, that Shimpo DT-105 from *Sunshine Instruments*, and the *RM-1500* from *TES Electronic*

Ready-to-use digital tach panel instruments are widely available. A pair of useful sources includes *Red Lion* and *Reddington*. Check out the latter's *Eagle* Model 53.

One obvious starting point for any custom tachometer is to use the *Basic Stamp* from *Parallax* combined with

that LCD display module from *Scott Edwards Electronics*. Later these can be replaced with a custom PIC or a baby PIC design and cheaper display. *Microchip Technology* is your main PIC supplier. Alternate solutions are offered by *Circuit Cellar*, as well as in most of those "hobby projects" kit product lines.

But unless you are up to something special, the commercial high volume modules are likely to be a better and cheaper solution than homebrew.

PIC Development Boards

Speaking of PIC's, Brad Mock of his *Technical Works* has just come up with something which has long been needed. Some small printed circuit breadboards that hold your choice of

NEED HELP?

Phone or email all your US Tech Musings questions to:

> Don Lancaster Synergetics Box 809-EN Thatcher, AZ, 85552 (520) 428-4073

US email: *don@tinaja.com* Web page: *www.tinaja.com* popular PIC chips, along with all the necessary regulator, oscillator, reset circuitry, and related goodies. Unlike the *Basic Stamp* from *Parallax*, these conveniently let you work directly in ultra fast PIC machine language. Two current models are for the 18 and 28 pin PIC chips.

Other sizes are in the works.

The list prices will be \$17.95. His special introductory price of \$14.95 is available for readers of this column. Figure four shows you several more details on these *PicPro* devices. Lots more PIC info can be downloaded at *www.tinaja.com/picup01.html*

New Tech Lit

From Texas Instruments, a Radio Frequency Solutions and their Video Solutions for PC Platforms mailers. From Maxim, the latest release of a Data Catalog CD. The new reference library CD from Hitachi about their SuperH RISC Engines

There is a new freebie catalog out from *Home Automation Systems*. And *Home Automator* magazine remains your first choice for useful help in this field. A home automation tutorial is at www.tinaja.com/resbn01.html

I came across two interesting new books this month. First, do check out *When Things Start to Think* by Neil



May, 1999

NAMES AND NUMBERS

Hitachi

2000 Sierra Point Pkwy Brisbane CA 94005 (415) 589-8300

Home Automation Systems 17171 Daimler Street Irvine CA 92614 (800) 367-9836

Home Automator 2258 Sandy Lane Mebane NC 27302 (910) 578-9519

Live Wire Enterprises PO Box 670081 Flushing NY 11367 (718) 544-4400

Maxim

120 San Gabriel Dr Sunnyvale CA 94086 (800) 998-8800

P-O-P & Sign Design 7400 Skokie Blvd Skokie IL 60077 (708) 675-7400

Gershenfeld. This text is mostly on ongoing projects by the MIT Media Lab. Neil makes heavy predictions for the widespread use of low cost distributed intelligence. Everything from erasable digital paper to smart shoes. This title meshes nicely with *The Age of Intelligent Machines* that we looked at last month.

There is also a superb *Planetary Astronomy* text by a Ronald Schorn. This appears to be a highly readable and a definitive history of our solar system discoveries. As written by a NASA insider. Lots of references and a detailed and annotated bibliography are nicely included.

More on these titles can be found at *www.tinaja.com/amlink01.html* A very useful data base for astronomy teaching materials can be gotten from *www.aas.org/~education/index1.html*

An intriguing *Knotty Neon* lighting and display material is now available. These are basically knottable "ropes" of electrolumnescent light. There's ten colors with lengths up to 600 feet. The colors are somewhat adjustable by changing your applied frequency from a 12 volt ac control unit driven by a wall wart.

Supplier is *Live Wire Enterprises*. I was unable to locate their website. They are mentioned at *www.led.com*

Point of Purchase 6225 Barfield Rd #200

Atlanta GA 30328 (404) 252-8831

Sign Business 1008 Depot Hill Office Pk Broomfield CO 80020 (303) 469-0424

SignCraft PO Box 06031 Ft Myers FL 33906 (813) 939-4644

Synergetics Box 809 Thatcher AZ 85552 (520) 428-4073

Technical Works PO Box 3692 Albany GA 31706 (912) 787-3000

Texas Instruments PO Box 655303 Dallas TX 75380 (800) 336-5236

and at www.lightsearch.com

Trade journals that target this sort of neat stuff include *Signcraft*, *Sign Business*, *POP* and *Sign Design*, and *Point* of *Purchase*.

There sure is a bunch of interest in *boat anchors* these days. Pieces of ancient military surplus comm or test gear that are outrageously huge and heavy. They sure do not make them like this any more. I will try to do an in-depth survey sometime.

But for now, check into that link farm at *nashville.net/~badger/millist* Or to find "straight from the horse's whatever" info, try out FM 24-24 at *www.gordon.army.mil/doctrine/2424*

Plus, of course, good old Surplus Al at mh105.infi.net/~surplsal/

Speaking of boat anchors, I just do happen to have a stunning buy on a neat-o 60 kilowatt load bank. AC or DC, single or three phase, 12 to 440 volts. You use this one for generator testing, student power lab loads, or wind energy research. It also makes toast. Nope, there is no way you can call this one a white elephant. It is a perfectly normal gray elephant color.

And size.

Email me at *don@tinaja.com* or go to *www.tinaja.com/bargte01.html*

For all the fundamentals of digital integrated circuits, be sure to check

DON LANCASTER

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. \$28.50

RESEARCH INFOPACKS

Don's instant cash-and-carry flat rate consulting service. Ask any reasonable technical question for a detailed analysis and complete report. See www.tinaja.com/info01 for specifics. \$79.00

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. **THE** two books for digital integrated circuit fundamentals. About as hands-on as you can get. **\$28.50** each.

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. **\$18.50**

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. \$119.50

LOTS OF OTHER GOODIES

Tech Musings V or VI	\$24.50
Ask the Guru I or II or III	\$24.50
Hardware Hacker II, III or IV	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell.	\$29.50
PostScript Video & secrets	\$29.50
PostScript Reference II	\$34.50
DestCarlet Tetericite (0 a shi s sh	
PostScript Tutorial/Cookbook	\$22.50
PostScript by Example	\$32.50
Understanding PS Programming	\$29.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking in DoctScrint	\$22.50
Thinking in PostScript	
LaserWriter Reference	\$19.50
Type 1 Font Format	\$16.50
Acrobat Reference	\$24.50
	\$380.00
Technical Insider Secrets	FREE

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. \$39.50

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set shows you Don's tested and proven real-world alternatives. **28.50**

BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. **\$24.50**

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. \$24.50

FREE SAMPLES

Check Don's Guru's Lair at http://www.linaja.com for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resouces, too. Tech help, hot links to cool sites, consultants. email: don@tinaja.com FREE US VOICE HELPLINE VISA/MC

SYNERGETICS Box 809-EN Thatcher, AZ 85552 (520) 428-4073

Tech Musings

into my *TTL* and *CMOS Cookbooks*. Either by themselves or as part of my bargain priced *Lancaster Classics Library*. See my nearby *Synergetics* ad for full details.

And for all your book needs, see *www.tinaja.com/amlink01.html*

The latest website additions to my

Guru's Lair found at *www.tinaja.com* do include a tutorial on *Supraluminal Dowsing for Brown's Gas in Roswell.* Your key secret, of course, is to be sure to use an overunity water-fueled black helicopter.

Our *Consultant's Network* is newly expanded and greatly improved up at

www.tinaja.com/consul01.html And lots of surplus bargains are found at www.tinaja.com/barg01.html

As usual, most of these mentioned items should show up in our *Names* & *Numbers* or *Tachometer Resources* sidebars. Check here before calling our US technical helpline. \blacklozenge

