

Some Equations Useful in AC Power Calculations

Notation: All **bold-face** letters represent **complex** numbers.

RMS Value of a Sinusoid

$$V_{\text{rms}} = V_p / \sqrt{2}$$

$$I_{\text{rms}} = I_p / \sqrt{2}$$

Impedance

$$\mathbf{Z} = R + j X = |\mathbf{Z}| \angle \theta$$

$$|\mathbf{Z}| = (R^2 + X^2)^{1/2}$$

$$\theta = \tan^{-1}(X/R)$$

Note: θ is the angle of the load impedance (We have suppressed the subscript z.)

Ohm's Law in Frequency Domain

$$\mathbf{V} = \mathbf{I} \mathbf{Z}$$

$$V_p = I_p |\mathbf{Z}|$$

$$V_{\text{rms}} = V / \sqrt{2}$$

$$I_{\text{rms}} = I / \sqrt{2}$$

$$V_{\text{rms}} = I_{\text{rms}} |\mathbf{Z}|$$

$$\theta_v - \theta_i = \theta$$

$$\theta > 0 \text{ when } X > 0 \text{ (Inductive impedance)}$$

$$\theta < 0 \text{ when } X < 0 \text{ (Capacitive impedance)}$$

Average Power (W)

$$P = V_{\text{rms}} I_{\text{rms}} \cos \theta = I_{\text{rms}}^2 R = (V_{\text{rms}}^2 \cos \theta) / |\mathbf{Z}|$$

Power Factor

$$\text{pf} = \cos \theta = R / (R^2 + X^2)^{1/2}, \quad 1 \geq \text{pf} \geq 0.$$

If $\theta > 0$ (inductive impedance), $\theta_i < \theta_v$, pf lagging

If $\theta < 0$ (capacitive impedance), $\theta_i > \theta_v$, pf leading

If $\theta = 0$ for purely resistive load and the pf is unity

Reactive Power (VAR)

$$Q = V_{\text{rms}} I_{\text{rms}} \sin \theta = I_{\text{rms}}^2 X$$

Apparent Power (VA)

$$S = V_{\text{rms}} I_{\text{rms}} = I_{\text{rms}}^2 |\mathbf{Z}| = V_{\text{rms}}^2 / |\mathbf{Z}|$$

Complex Power (VA)

$$\mathbf{S} = V_{\text{rms}} (\mathbf{I}_{\text{rms}})^* = V_{\text{rms}} I_{\text{rms}} \angle \theta = P + j Q = I_{\text{rms}}^2 \mathbf{Z} = (V_{\text{rms}})^2 / \mathbf{Z}^*$$